



# **FUNDAMENTALS OF ELECTRIC CIRCUITS**

## **Part 1: DC CIRCUITS**



### **Chapter 2: Basic laws**

**I. Introduction.**

**II. Ohm's law.**

**III. Nodes, branches and loops.**

**IV. Kirchhoff's laws.**

**V. Series resistors and voltage division.**

**VI. Parallel resistors and current division.**

**VII. Wye – Delta transformations**



# Chapter 2: Basic laws





## I. Introduction

- In order to determine the values of current, voltage, and power in an electric circuit, we should understand some fundamental laws.
- This chapter presents:
  - ❖ Ohm's law, Kirchhoff's laws
  - ❖ Some techniques commonly applied in circuit design and analysis:
    - ☐ Combining resistors in series and parallel
    - ☐ Voltage division
    - ☐ Current division
    - ☐ Delta – Wye and Wye – Delta transformations
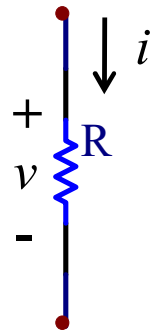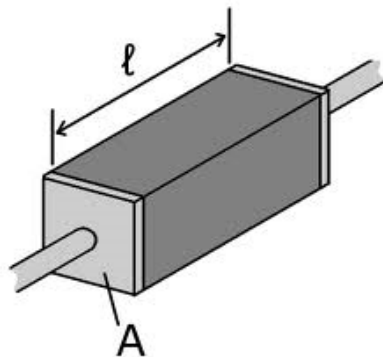
## II. Ohm's law

- In general, material have a characteristic behavior of resisting the flow of electric charge.
- *Resistance* ( $R$ ) is known as the ability to resist current.



$$R = \rho \frac{l}{A}$$

$\rho$ : resistivity of the material [ $\Omega\text{m}$ ]

$l$ : length of material [m]

$A$ : cross sectional area [ $\text{m}^2$ ]

- **Ohm's law:** The voltage  $v$  across a resistor is directly proportional to the current  $i$  flowing through the resistor.

$$v = Ri$$

- The resistance  $R$  of an element denotes its ability to resist the flow of electric current; it is measured in Ohms [ $\Omega$ ]

$$R = \frac{v}{i} \rightarrow 1\Omega = 1 \frac{V}{A}$$




## Chapter 2: Basic laws



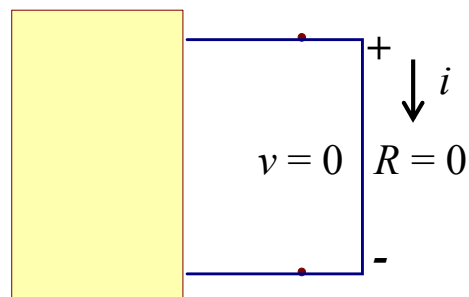
### II. Ohm's law

- There are two extreme possible values of  $R$ 
  - ❖ *Short circuit*: is a circuit element with resistance approaching zero (current could be anything).
  - ❖ *Open circuit*: is a circuit element with resistance approaching infinity (voltage could be anything).



$$R = 0 \rightarrow v = iR = 0$$

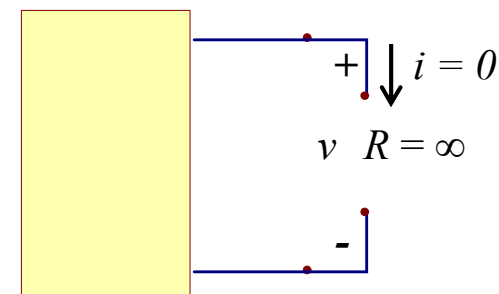

$$i = \lim_{R \rightarrow \infty} \frac{v}{R} = 0$$

## Chapter 2: Basic laws

### II. Ohm's law

#### ➤ Resistor classification:


##### ❖ Fixed resistors:



Wire wound  
(small resistance)




Composition (large  
resistance)

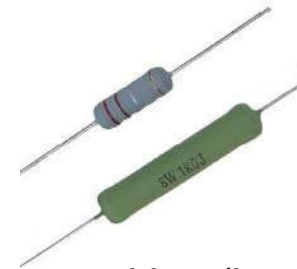


Symbol for  
fixed resistor


##### ❖ Variable resistors:

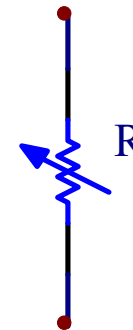

##### ❖ Linear resistor:

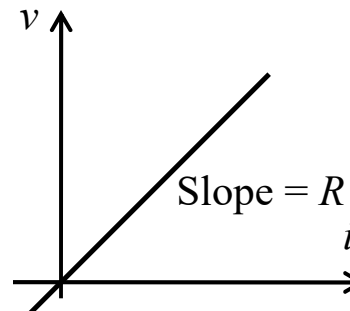
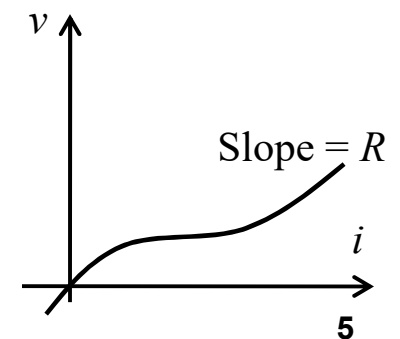
##### ❖ Nonlinear resistor: Do not consider





## Chapter 2: Basic laws



### II. Ohm's law

- *Conductance* is the ability of an element to conduct electric current, it is measured in Siemens [S]

$$G = \frac{1}{R} = \frac{i}{v} \quad 1\text{S} = 1\frac{\text{A}}{\text{V}}$$

- *Power dissipated by a resistor (conductance):*

$$p = vi = i^2 R = \frac{v^2}{R}$$

$$p = vi = v^2 G = \frac{i^2}{G}$$

→ a resistor always absorbs power from the circuit (*passive element*)



## Chapter 2: Basic laws




### III. Nodes, branches, and loops

- Since the elements of an electric circuit can be interconnected in several ways  
→ we need to understand some basic concepts of network topology.
- We regard a network as an interconnection of elements or devices, whereas a circuit is a network providing one or more closed paths
- We study the ***properties relating to the placement of element*** in the network and the ***geometric configuration of the network***.
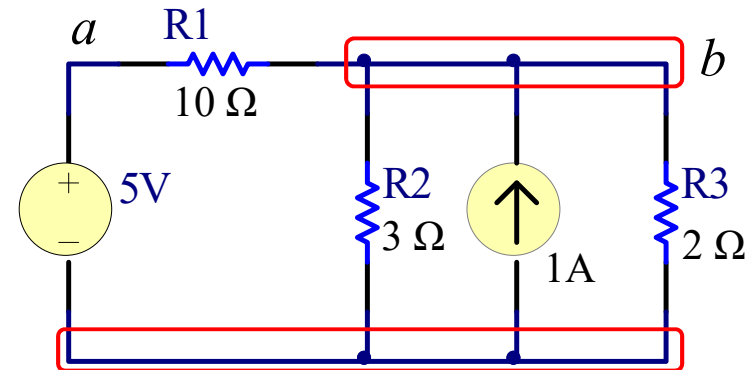
### III. Nodes, branches, and loops

- A **branch** ( $b$ ) represents a single element such as a voltage source or a resistor (represent any two terminal element).



*Ex:* The circuit has five branches: the 5-V voltage source, the 1-A current source, and three resistors.

- A **node** ( $n$ ) is the point of connection between two or more branches.

*Ex:* The circuit has three nodes:  $a$ ,  $b$ , and  $c$ .

- A **loop** is any closed path in a circuit, formed by starting at a node, passing through a set of nodes, and returning to the starting node without passing through any node more than once.


*Ex:*  $abca$  is a loop, containing the  $R1$ ,  $R2$  and voltage source.


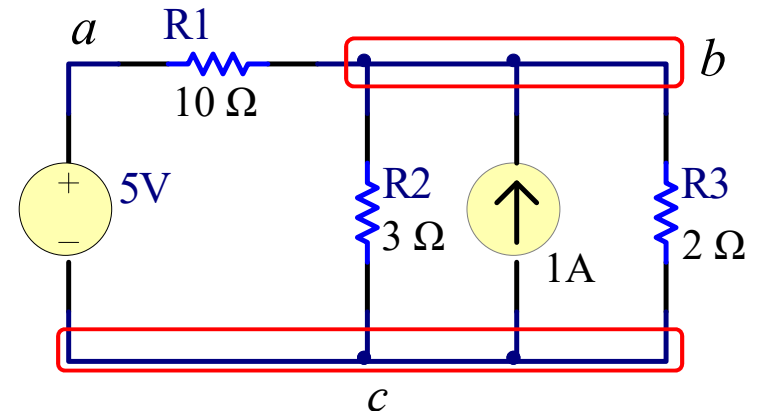
## III. Nodes, branches, and loops

- A loop is said to be **independent** if it contains a branch which is not in any other loop.

*Ex:* The circuit has totally six loops, but only three of them are independent.



- A network with  $b$  branches,  $n$  nodes, and  $l$  independent loops, has an equation:

$$b = l + n - 1$$

- Two or more elements are in **series** if they are cascaded or connected sequentially and consequently carry the same current.
- Two or more elements are in **parallel** if they are connected to the same two nodes and sequentially have the same voltage across them.

## Chapter 2: Basic laws



### IV. Kirchhoff's laws

- Kirchhoff's laws include: Kirchhoff's current law (KCL) and Kirchhoff's voltage law (KVL).
- Kirchhoff's laws, coupled with Ohm's law, make a sufficient and powerful set of tools for analyzing a large variety of electric circuits.
- **Kirchhoff's current law (KCL)** states that the algebraic sum of currents entering a node (or a closed boundary) is zero.


$$\sum_{n=1}^N i_n = 0$$

Convention:

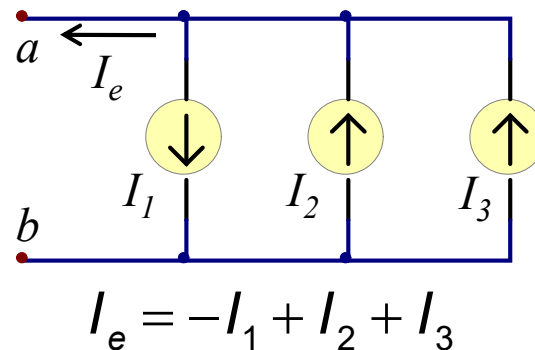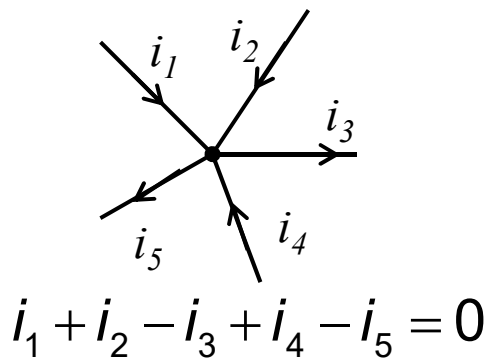- ❖ Current entering a node may be regarded as positive.
- ❖ Current leaving the node may be taken as negative.



Equivalent

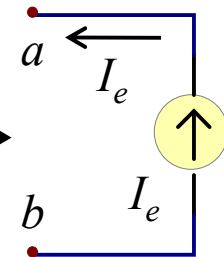

## IV. Kirchhoff's laws

- **Kirchhoff's voltage law (KVL)** states that the algebraic sum of all voltages around a closed path (or loop) is zero.

$$\sum_{m=1}^M v_m = 0$$

Ex1: Write KVL for this circuit.



- ❖ Start with any branch and go around the loop either clockwise or counterclockwise

$$-V_1 + V_2 + V_3 + V_4 + V_5 = 0$$

$$V_2 + V_3 + V_5 = V_1 - V_4$$

Ex2: When voltage sources are connected in series, KVL can be applied to obtain the total voltage.


$$V_{ab} = V_1 + V_2 - V_3$$

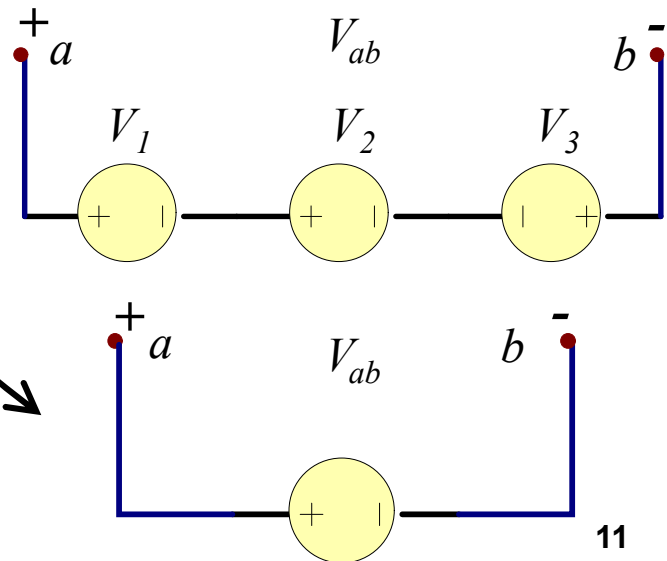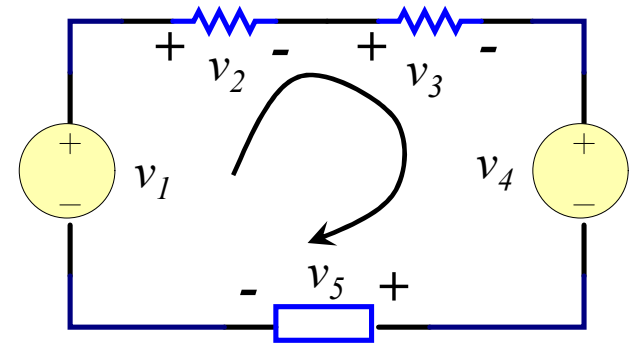
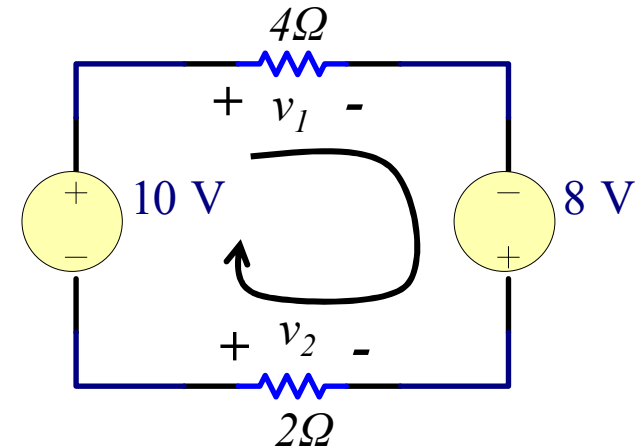
## IV. Kirchhoff's laws

Ex3: Find  $v_1$  and  $v_2$  in the circuit.

- ❖ Assume that current  $i$  flows through the loop as indicating in the Figure.




- ❖ From Ohm's law:  $v_1 = 4i$  ;  $v_2 = -2i$
- ❖ Applying KVL around the loop gives:  $v_1 - v_2 = 10 + 8 = 18$
- ❖ Substituting  $i$  in Ohm's law to KVL:  $6i = 18 \rightarrow i = 3A$
- ❖ Finally we have:  $v_1 = 4i = 12V$

$$v_2 = -2i = -6V$$
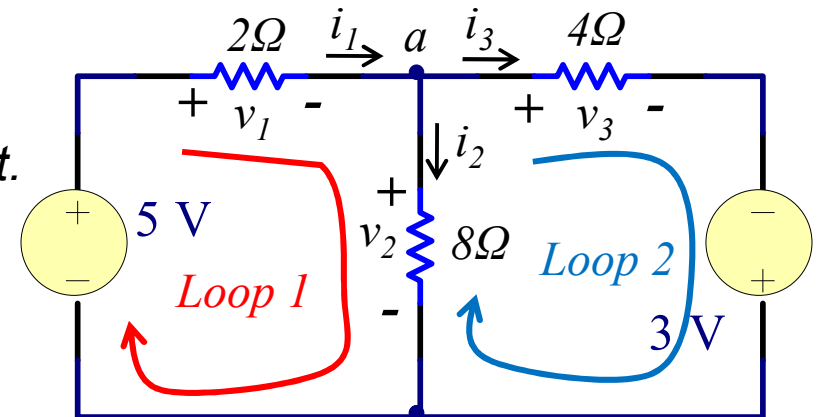
## IV. Kirchhoff's laws

Ex4: Find the currents and voltages in the circuit.



- ❖ From Ohm's law:

$$v_1 = 2i_1 \quad ; \quad v_2 = 8i_2 \quad ; \quad v_3 = 4i_3$$

- ❖ At node  $a$ , applying KCL gives:  $i_1 - i_2 - i_3 = 0$

- ❖ Applying KVL to loop 1 and loop 2: 
$$\begin{cases} v_1 + v_2 = 5 \\ -v_2 + v_3 = 3 \end{cases} \rightarrow \begin{cases} 2i_1 + 8i_2 = 5 \\ -8i_2 + 4i_3 = 3 \end{cases}$$

- ❖ Finally we have: 
$$\begin{cases} i_1 - i_2 - i_3 = 0 \\ 2i_1 + 8i_2 = 5 \\ -8i_2 + 4i_3 = 3 \end{cases} \rightarrow \begin{cases} i_1 = 1,5A \\ i_2 = 0,25A \\ i_3 = 1,25A \end{cases} \rightarrow \begin{cases} v_1 = 3V \\ v_2 = 2V \\ v_3 = 5V \end{cases}$$



## Chapter 2: Basic laws



### V. Series resistors and voltage division

- The **equivalent resistance** of any number of resistors connected in series is the sum of the individual resistances.

$$R_{eq} = R_1 + R_2 + \dots + R_N = \sum_{n=1}^N R_n$$

- **Voltage divider:** The voltage  $v$  is divided among the resistors in direct proportion to their resistances, the larger the resistance, the larger the voltage drop.

$$V_n = \frac{R_n}{R_1 + R_2 + \dots + R_N} v$$



## Chapter 2: Basic laws

### VI. Parallel resistors and current division

- The **equivalent resistance** of two parallel resistors is equal to the product of their resistances divided by their sum

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$$

- The **equivalent conductance** of resistors connected in parallel is the sum of their individual conductances.


$$G_{eq} = G_1 + G_2 + \dots + G_N = \sum_{n=1}^N G_n$$

- **Current divider:**


$$i_n = \frac{G_n}{G_1 + G_2 + \dots + G_N} i$$
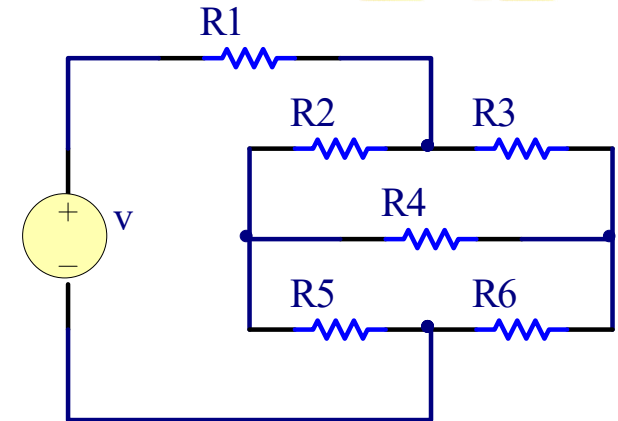
## VII. Wye – Delta transformations


- How do we combine resistors when they are neither in series nor in parallel ?
- **Delta to Wye conversion:**



*Bridge circuit*

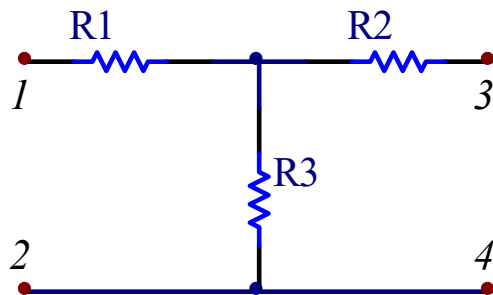

*Wye (Y) or T network*

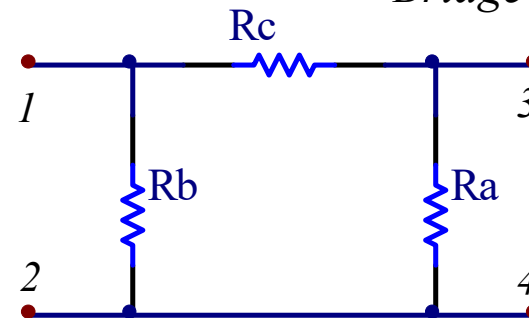


*Delta (Δ) or Π network*

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c} ; R_2 = \frac{R_c R_a}{R_a + R_b + R_c} ; R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$




## VII. Wye – Delta transformations

### ➤ Wye to Delta conversion:

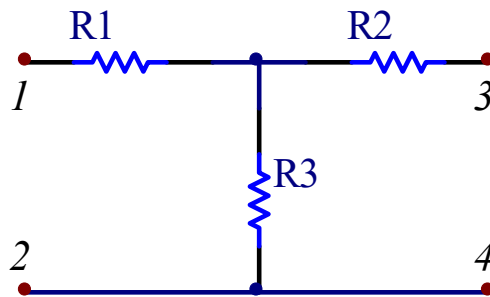

Wye (Y) or T network

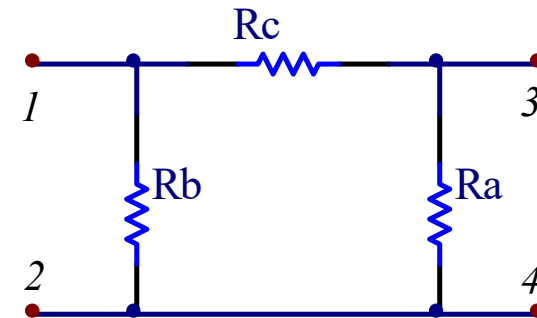

Delta (Δ) or Π network

$$R_a = R_2 + R_3 + \frac{R_2 R_3}{R_1} ; R_b = R_1 + R_3 + \frac{R_1 R_3}{R_2}$$

$$R_c = R_1 + R_2 + \frac{R_1 R_2}{R_3}$$

## VII. Wye – Delta transformations

Ex: For the bridge circuit, find  $R_{eq}$  and  $i$

- In this circuit, there are two Y networks:  $(R_2, R_4, R_6)$  and  $(R_3, R_5, R_6) \rightarrow$  transforming just one of them will simplify the circuit
- Applying the Y to  $\Delta$  transformation:

$$R_a = R_3 + R_5 + \frac{R_3 R_5}{R_6} = 85\Omega$$

$$R_b = R_5 + R_6 + \frac{R_5 R_6}{R_3} = 170\Omega$$

$$R_c = R_3 + R_6 + \frac{R_3 R_6}{R_5} = 34\Omega$$

- Combining all resistors, we obtain:

$$R_{eq} = R_1 + \left\{ \left[ (R_2 // R_c) + (R_4 // R_b) \right] // R_a \right\}$$

$$R_{eq} = 40\Omega$$

$$\rightarrow i = \frac{u_{ab}}{R_{eq}} = \frac{100}{40} = 2,5A$$

