



# FUNDAMENTALS OF ELECTRIC CIRCUITS

## Part 1: DC CIRCUITS



### Chapter 3: Methods of analysis

**I. Introduction.**

**II. Nodal analysis.**

**III. Mesh analysis.**

**VI. Nodal versus mesh analysis.**



# Chapter 3: Methods of analysis



## I. Introduction

- In chapter 2, we have studied the fundamental laws of circuit theory (Ohm's law and Kirchhoff's laws).
- This chapter will apply these laws to develop 02 powerful techniques for circuit analysis:
  - ❖ Nodal analysis: Base on KCL
  - ❖ Mesh analysis: Base on KVL
- With the 02 techniques, we can analyze almost any circuit by obtaining a set of simultaneous equations that are the solved to obtain the required values of current or voltage (power, energy)




# Chapter 3: Methods of analysis



## II. Nodal analysis

- Nodal analysis provides a general procedure for analyzing circuits using *node voltage as the circuit variables* → known as the *node – voltage method*.
- Choosing node voltages instead of element voltages is convenient and *reduces the number of equations*.

### II.1. Nodal analysis without voltage sources

- Assuming that circuits with  $n$  nodes do not contain voltage sources
  - ❖ Select *a node as the reference node (ground,  $v = 0$ )*.  Assign voltages  $v_1, v_2, \dots, v_{n-1}$  to the remaining  $n-1$  nodes. All voltages are referenced to the reference node.
  - ❖ Apply *KCL to each of the  $n-1$  non-reference nodes*. Use Ohm's law to *express the branch currents in terms of node voltages*.
  - ❖ Solve the resulting simultaneous equations to obtain the unknown node voltages.

## II.1. Nodal analysis without voltage sources

Ex 1: Find the currents in this circuit.


- Choose node 0 as a reference node ( $v_0 = 0$ ). Assign voltage of node 1 and node 2 with  $v_1$  and  $v_2$ , respectively.
- Applying KCL to each non-reference node:

- ❖ Add  $i_1$ ,  $i_2$ , and  $i_3$  as the currents on  $R_1$ ,  $R_2$ ,  $R_3$
- ❖ Applying KCL for node 1 and 2 gives: 
$$\begin{cases} I_1 = I_2 + i_1 + i_2 \\ I_2 + i_2 = i_3 \end{cases}$$

- Applying Ohm's law to express the currents in term of node voltages:

$$i_1 = \frac{V_1 - V_0}{R_1} = G_1 V_1 \quad i_2 = \frac{V_1 - V_2}{R_2} = G_2 (V_1 - V_2) \quad i_3 = \frac{V_2 - V_0}{R_3} = G_3 V_2$$
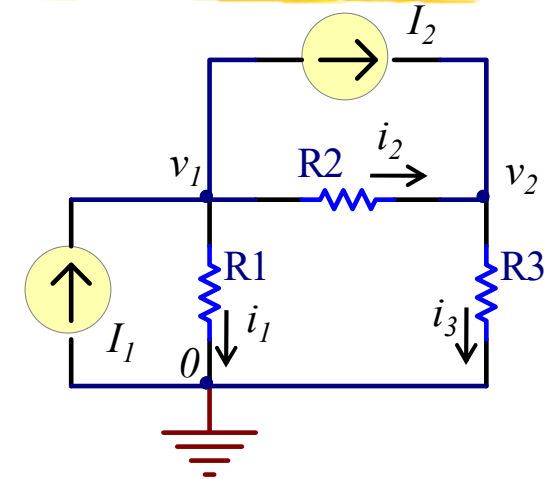
$$\rightarrow \begin{cases} I_1 = I_2 + G_1 V_1 + G_2 (V_1 - V_2) \\ I_2 + G_2 (V_1 - V_2) = G_3 V_2 \end{cases} \rightarrow \begin{cases} (G_1 + G_2) V_1 - G_2 V_2 = I_1 - I_2 \\ -G_2 V_1 + (G_2 + G_3) V_2 = I_2 \end{cases}$$



## II.1. Nodal analysis without voltage sources


Ex 1: Find the currents in this circuit.

$$\rightarrow \begin{cases} (G_1 + G_2)v_1 - G_2v_2 = I_1 - I_2 \\ -G_2v_1 + (G_2 + G_3)v_2 = I_2 \end{cases} \Leftrightarrow \begin{bmatrix} G_1 + G_2 & -G_2 \\ -G_2 & G_2 + G_3 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} I_1 - I_2 \\ I_2 \end{bmatrix}$$

➤ We can obtain the node voltages  $v_1$ ,  $v_2$  using any standard method (*substitution method, elimination method, Cramer's rule, matrix inversion*) with software such as **Matlab**, Mathcad, Maple, Quattro Pro.

➤ After obtaining the node voltages, we can calculate the currents in circuit.

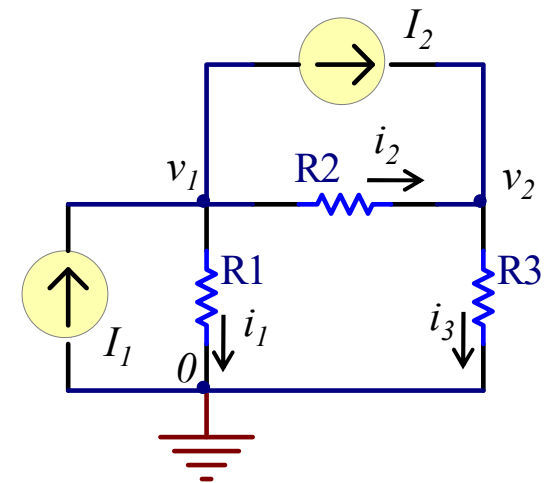
$$i_1 = \frac{V_1}{R_1} \quad i_2 = \frac{V_1 - V_2}{R_2} \quad i_3 = \frac{V_2}{R_3}$$


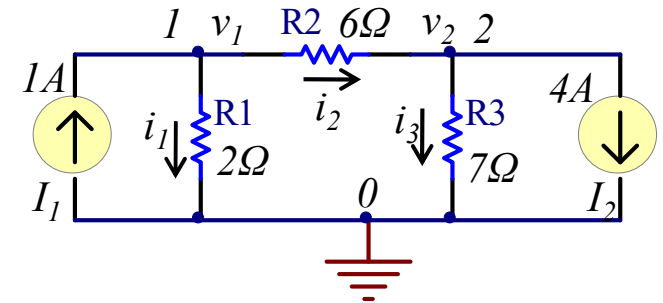
## II.1. Nodal analysis without voltage sources

Ex 2: Find the currents in this circuit.

- Choose node 0 ~ reference node, node 1 ~  $v_1$ , node 2 ~  $v_2$ .



- Applying KCL to each non-reference node: 
$$\begin{cases} I_1 = i_1 + i_2 \\ i_2 = i_3 + I_2 \end{cases}$$

- Applying Ohm's law:  $i_1 = \frac{V_1}{R_1} = G_1 V_1$  ;  $i_2 = \frac{V_1 - V_2}{R_2} = G_2 (V_1 - V_2)$  ;  $i_3 = \frac{V_2}{R_3} = G_3 V_2$

$$\rightarrow \begin{cases} (G_1 + G_2)V_1 - G_2 V_2 = I_1 \\ -G_2 V_1 + (G_2 + G_3)V_2 = -I_2 \end{cases} \rightarrow \begin{cases} 0,667V_1 - 0,167V_2 = 1 \\ -0,167V_1 + 0,31V_2 = -4 \end{cases} \rightarrow \begin{cases} V_1 = -2V \\ V_2 = -14V \end{cases}$$

- The currents in circuit:  $i_1 = \frac{V_1}{R_1} = -1A$  ;  $i_2 = \frac{V_1 - V_2}{R_2} = 2A$  ;  $i_3 = \frac{V_2}{R_3} = -2A$

## II.1. Nodal analysis without voltage sources


Ex 3: Find the voltages at the three non-reference nodes in the circuit.

- Choose node 0 ~ reference node, node 1 ~  $v_1$ , node 2 ~  $v_2$ , node 3 ~  $v_3$ .

- Applying KCL: 
$$\begin{cases} i_1 + i_4 = I_1 \\ i_1 + 4i_x = i_x \\ i_4 = 4i_x + i_3 \end{cases}$$

- Applying Ohm's law:  $i_1 = G_1(v_1 - v_2)$  ;  $i_x = G_2 v_2$  ;  $i_3 = G_3 v_3$  ;  $i_4 = G_4(v_1 - v_3)$

$$\rightarrow \begin{cases} (G_1 + G_4)v_1 - G_1 v_2 - G_4 v_3 = I_1 \\ -G_1 v_1 + (G_1 - 3G_2)v_2 = 0 \\ -G_4 v_1 + 4G_2 v_2 + (G_3 + G_4)v_3 = 0 \end{cases} \rightarrow \begin{cases} \frac{5}{6}v_1 - \frac{1}{3}v_2 - \frac{1}{2}v_3 = 10 \\ -\frac{1}{3}v_1 - \frac{5}{12}v_2 = 0 \\ -\frac{1}{2}v_1 + v_2 + \frac{2}{3}v_3 = 0 \end{cases} \rightarrow \begin{cases} v_1 = 80V \\ v_2 = -64V \\ v_3 = 156V \end{cases}$$

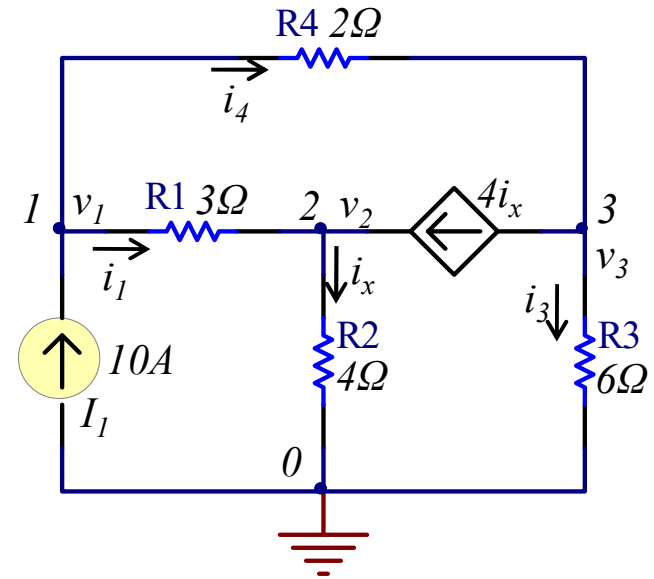


## II.2. Nodal analysis with voltage sources

- We consider the following two possibilities:
  - ❖ Voltage source connects between reference node and non-reference node

Voltage of non-reference node = voltage source

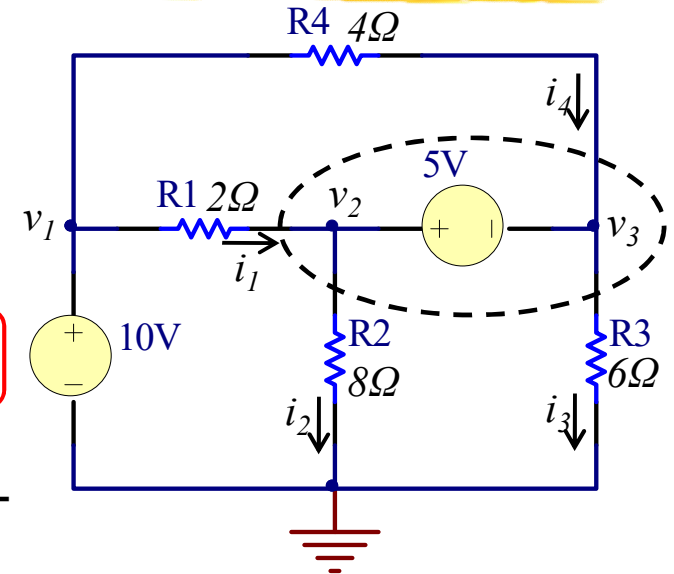- ❖ Voltage source connects between 2 non-reference nodes → form a *super-node*.



**Super-node** is formed by enclosing a (dependent or independent) voltage source connected between two non-reference nodes and any elements connected in parallel with it.

→ Using the same three steps, except the super-node:

$$i_1 + i_4 = i_2 + i_3 \rightarrow \frac{V_1 - V_2}{R_1} + \frac{V_1 - V_3}{R_4} = \frac{V_2}{R_2} + \frac{V_3}{R_3} \quad V_2 - V_3 = 5V$$




## II.2. Nodal analysis with voltage sources

➤ We have a set of equations:

$$\begin{cases} v_1 = 10V \\ v_2 - v_3 = 5V \\ \frac{5}{8}v_2 + \frac{5}{12}v_3 = 7,5 \end{cases} \rightarrow \begin{cases} v_1 = 10V \\ v_2 = 9,2V \\ v_3 = 4,2V \end{cases}$$

➤ **Note that:**

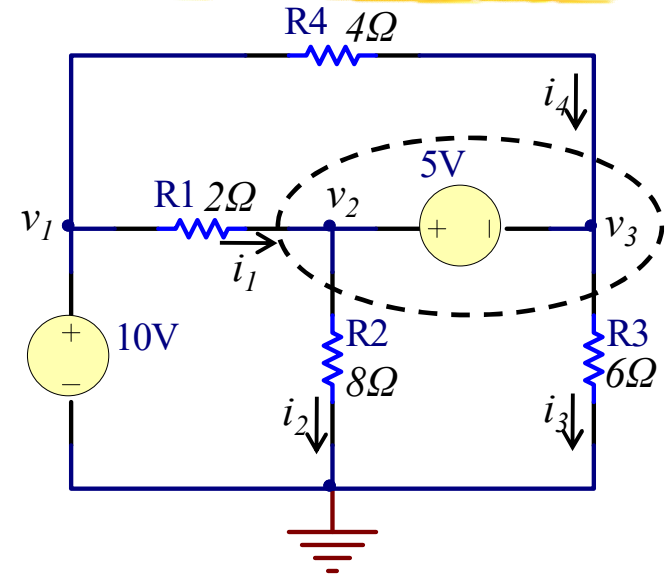- ❖ The voltage source inside the super-node provides a constraint equation needed to solve for the node voltages.
- ❖ A super-node has no voltage of its own.
- ❖ A super-node requires the application of both KCL and KVL.




## II.2. Nodal analysis with voltage sources

Ex 1: Find the voltage node in this circuit using nodal analysis.

- Super-node includes the 2-V source, node 1, node 2 and  $R_3$
- Applying KCL to the super-node gives:

$$2 = i_1 + i_2 + 7 \rightarrow 2 = \frac{V_1}{R_1} + \frac{V_2}{R_2} + 7 \leftrightarrow 2V_1 + V_2 = -20$$

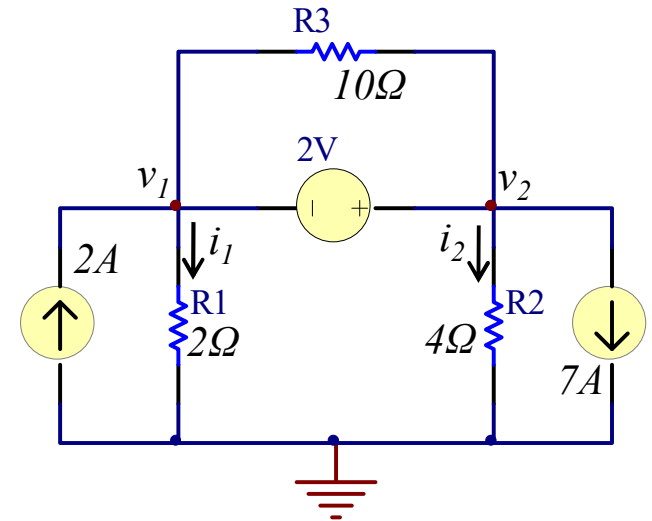
- Applying KVL to the super-node gives:  $V_2 = V_1 + 2$
- Solving the set of equations gives: 
$$\begin{cases} V_1 = -7.33V \\ V_2 = -5.33V \end{cases}$$


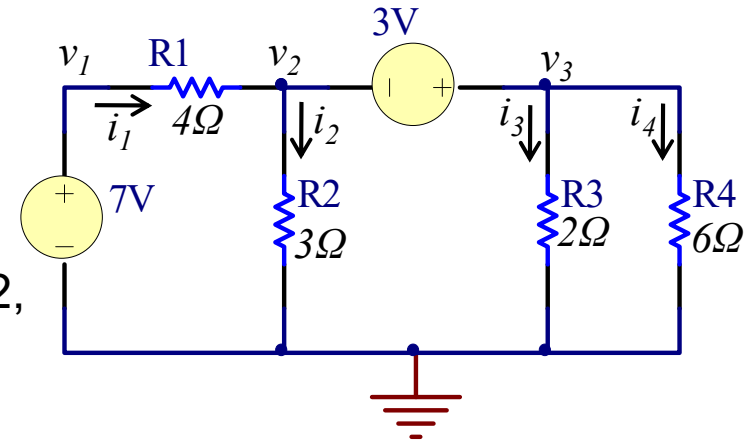
## II.2. Nodal analysis with voltage sources

Ex 2: Find the voltage nodes and the currents in this circuit using nodal analysis.

- Super-node includes the 3-V source, node 2, node 3.



- Applying the KVL and KCL to the super-node gives a set of equations:

$$\left\{ \begin{array}{l} \frac{V_1 - V_2}{R_1} = \frac{V_2}{R_2} + \frac{V_3}{R_3} + \frac{V_3}{R_4} \\ V_1 = 7V \\ V_3 = V_2 + 3 \end{array} \right. \rightarrow \left\{ \begin{array}{l} \frac{7}{12} V_2 + \frac{2}{3} V_3 = \frac{7}{4} \\ V_1 = 7V \\ V_3 = V_2 + 3 \end{array} \right. \rightarrow \left\{ \begin{array}{l} V_1 = 7V \\ V_2 = -0,2V \\ V_3 = 2,8V \end{array} \right.$$

- Applying Ohm's law gives the currents:

$$i_1 = \frac{V_1 - V_2}{R_1} = 1,8A \quad i_3 = \frac{V_3}{R_3} = 1,4A$$

$$i_2 = \frac{V_2}{R_2} = -0,067A \quad i_4 = \frac{V_3}{R_4} = 0,467A$$

## II.2. Nodal analysis with voltage sources

Ex 3: Find the voltage nodes in this circuit using nodal analysis.

- 1<sup>st</sup> super-node: Node 1 + node 2

$$i_1 + i_5 = i_2 + 10$$


$$\frac{V_1}{2} + \frac{V_1 - V_4}{3} = \frac{V_3 - V_2}{6} + 10$$

$$5V_1 + V_2 - V_3 - 2V_4 = 60$$

$$V_1 = 20 + V_2$$

- 2<sup>nd</sup> super-node: Node 3 + node 4:  $i_5 = i_2 + i_3 + i_4 \rightarrow \frac{V_1 - V_4}{3} = \frac{V_3 - V_2}{6} + \frac{V_3}{4} + V_4$
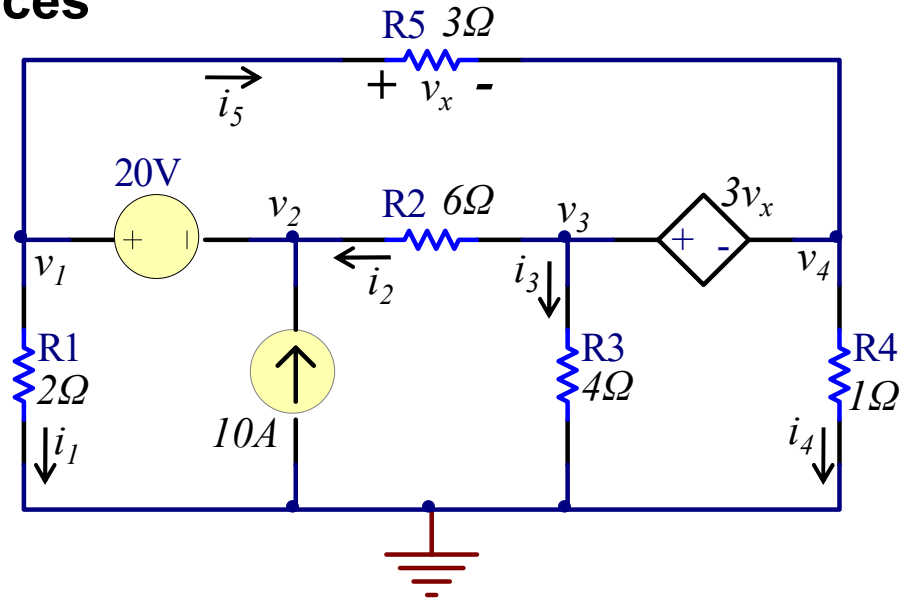
$$4V_1 + 2V_2 - 5V_3 - 16V_4 = 0 \quad V_3 = 3V_x + V_4 = 3(V_1 - V_4) + V_4 \rightarrow 3V_1 - V_3 - 2V_4 = 0$$



## II.2. Nodal analysis with voltage sources

Ex 3: Find the voltage nodes in this circuit using nodal analysis.

➤ We have a set of equations:

$$\begin{cases} 3v_1 - v_3 - 2v_4 = 0 \\ 6v_1 - v_3 - 2v_4 = 80 \\ 6v_1 - 5v_3 - 16v_4 = 40 \end{cases}$$


➤ Using Cramer's rule:

$$\Delta = \begin{vmatrix} 3 & -1 & -2 \\ 6 & -1 & -2 \\ 6 & -5 & -16 \end{vmatrix} = -18$$

$$\Delta_1 = \begin{vmatrix} 0 & -1 & -2 \\ 80 & -1 & -2 \\ 40 & -5 & -16 \end{vmatrix} = -480$$

$$\Delta_3 = \begin{vmatrix} 3 & 0 & -2 \\ 6 & 80 & -2 \\ 6 & 40 & -16 \end{vmatrix} = -3120$$
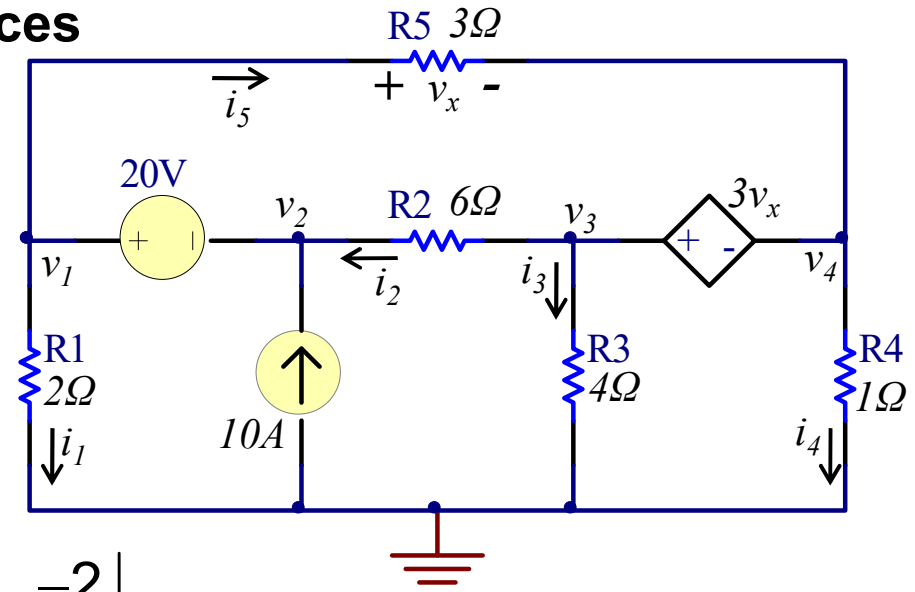
$$\Delta_4 = \begin{vmatrix} 3 & -1 & 0 \\ 6 & -1 & 80 \\ 6 & -5 & 40 \end{vmatrix} = 840$$



➤ The voltages gives:

$$v_1 = \frac{\Delta_1}{\Delta} = 26,67V$$

$$v_3 = \frac{\Delta_3}{\Delta} = 173.33V$$

$$v_4 = \frac{\Delta_4}{\Delta} = -46,67V$$

$$v_2 = v_1 - 20 = 6,67V_{13}$$

## II.2. Nodal analysis with voltage sources

Ex 4: Find the voltage nodes and the current branches in this circuit using nodal analysis.


- 1<sup>st</sup> super-node contains: 10-V source,  $5i_1$  dependent source, and  $R_4$

$$i_1 + i_2 + i_3 = 0 \rightarrow \frac{V_1}{2} + \frac{V_2}{4} + \frac{V_3}{3} = 0$$

$$V_1 - V_2 = 10$$

$$V_3 = 5i_1 + V_2 \rightarrow 5V_1 + 2V_2 - 2V_3 = 0$$

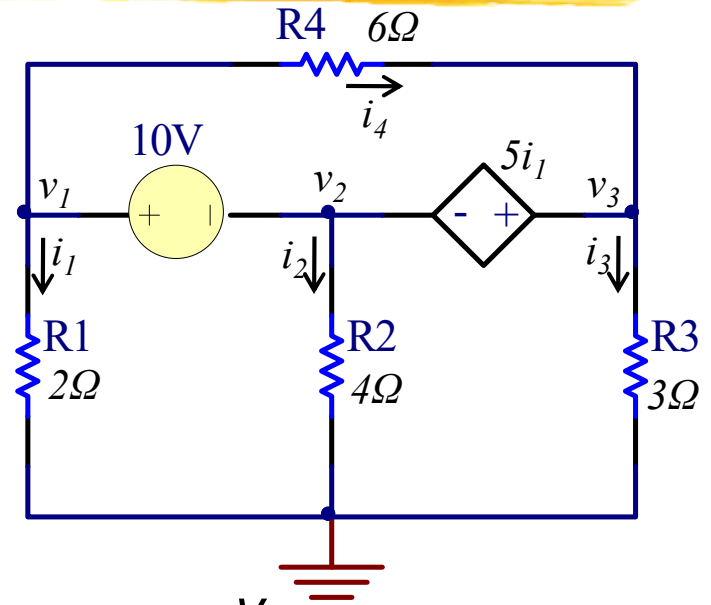- Solving the set of equations gives:
 
$$\begin{cases} V_1 = 3,043V \\ V_2 = -6,956V \\ V_3 = 0,652V \end{cases}$$



$$i_1 = \frac{V_1}{R_1} = 1,522A$$

$$i_2 = \frac{V_2}{R_2} = -1,739A$$

$$i_3 = \frac{V_3}{R_3} = 0,217A$$

$$i_4 = \frac{V_1 - V_3}{R_4} = 0,399A$$



## Chapter 3: Methods of analysis



### II.3. Nodal analysis by inspection

- In general, if a circuit (with only *independent current sources*) has  $N$  non-reference nodes, the node-voltage equations can be written in terms of the conductances as:

$$\text{where:} \quad \begin{bmatrix} G_{11} & G_{12} & \cdots & G_{1N} \\ G_{21} & G_{22} & \cdots & G_{2N} \\ \vdots & \vdots & \vdots & \vdots \\ G_{N1} & G_{N2} & \cdots & G_{NN} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ \vdots \\ v_N \end{bmatrix} = \begin{bmatrix} i_1 \\ i_2 \\ \vdots \\ i_N \end{bmatrix} \quad \Leftrightarrow \quad \mathbf{Gv} = \mathbf{i}$$


- ❖  $G_{kk}$ : Sum of the conductances connected to node  $k$ .
- ❖  $G_{kj} = G_{jk}$ : Negative of the sum of the conductances directly connecting nodes  $k$  and  $j$ ,  $k \neq j$ .
- ❖  $v_k$ : Unknown voltage at node  $k$ .
- ❖  $i_k$ : Sum of all independent current sources directly connected to node  $k$ , with currents entering the node treated as positive.

## II.3. Nodal analysis by inspection

Ex 5: Write the node voltage matrix equations for this circuit.

➤ There are 4 non-reference nodes
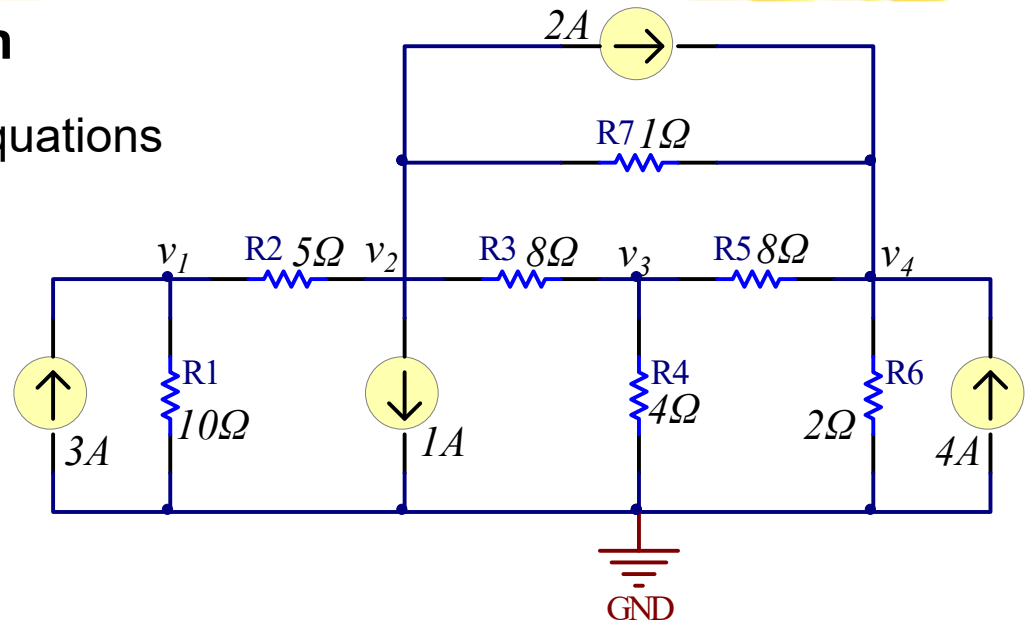
$$\begin{bmatrix} G_{11} & G_{12} & G_{13} & G_{14} \\ G_{21} & G_{22} & G_{23} & G_{24} \\ G_{31} & G_{32} & G_{33} & G_{34} \\ G_{41} & G_{42} & G_{43} & G_{44} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix} = \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix}$$



$$G_{11} = \frac{1}{R_1} + \frac{1}{R_2} = 0,3S$$

$$G_{22} = \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_7} = 1,325S$$

$$G_{33} = \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} = 0,5S$$


$$G_{44} = \frac{1}{R_5} + \frac{1}{R_6} + \frac{1}{R_7} = 1,625S$$



## II.3. Nodal analysis by inspection

Ex 5: Write the node voltage matrix equations for this circuit.

➤ There are 4 non-reference nodes

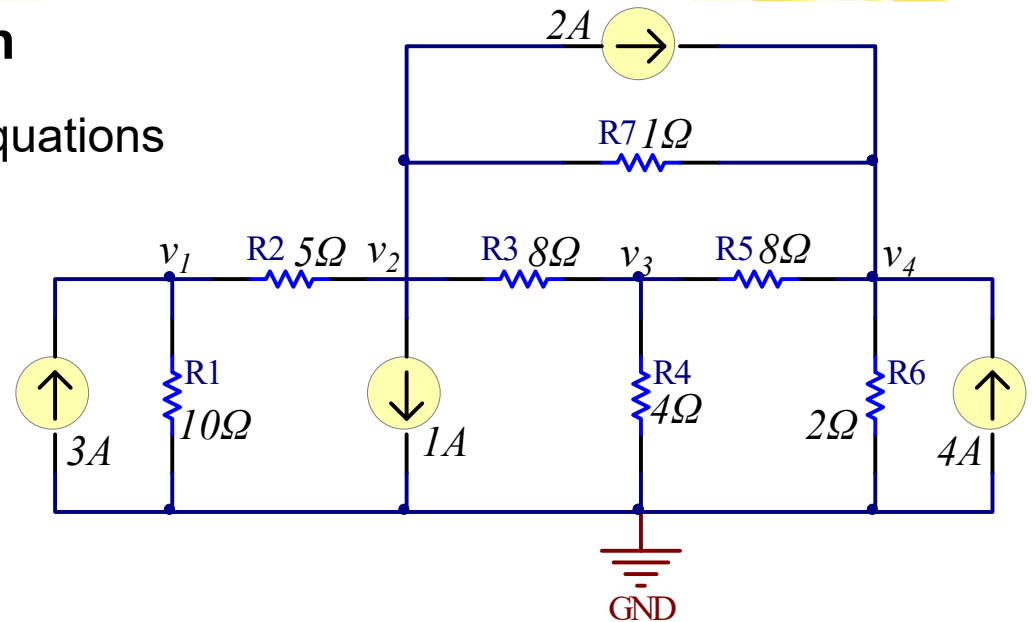

$$\begin{bmatrix} G_{11} & G_{12} & G_{13} & G_{14} \\ G_{21} & G_{22} & G_{23} & G_{24} \\ G_{31} & G_{32} & G_{33} & G_{34} \\ G_{41} & G_{42} & G_{43} & G_{44} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix} = \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix}$$

$$G_{12} = G_{21} = -\frac{1}{R_2} = -0,2S$$

$$G_{13} = G_{31} = 0$$

$$G_{14} = G_{41} = 0$$

$$G_{23} = G_{32} = -\frac{1}{R_3} = -0,125S$$

$$G_{24} = G_{42} = -\frac{1}{R_7} = -1S$$


$$G_{34} = G_{43} = -\frac{1}{R_5} = -0,125S$$

## II.3. Nodal analysis by inspection

Ex 3.5: Write the node voltage matrix equations for this circuit.

➤ There are 4 non-reference nodes
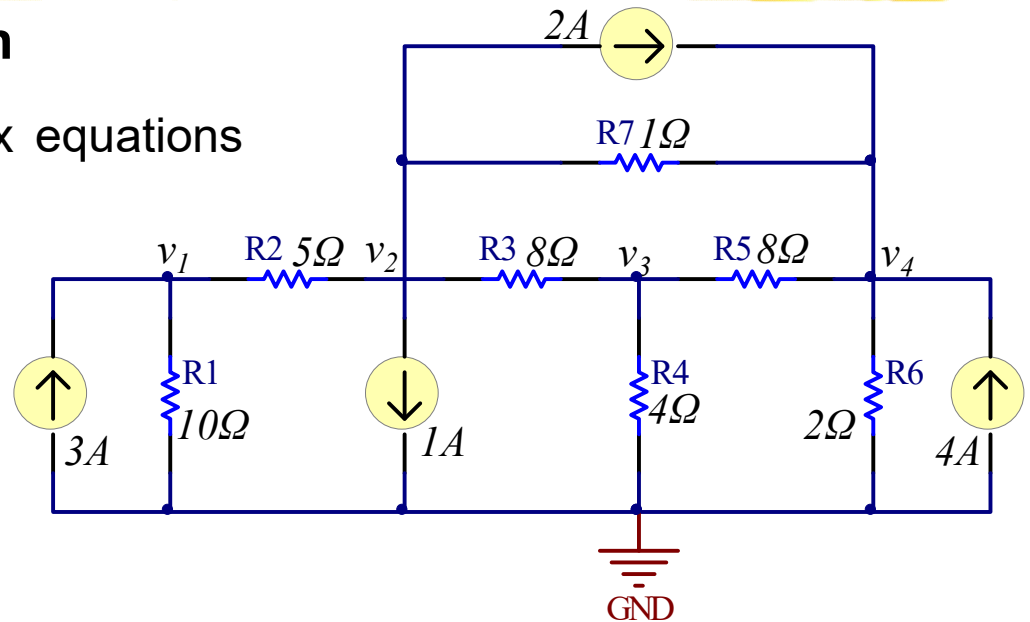
$$\begin{bmatrix} G_{11} & G_{12} & G_{13} & G_{14} \\ G_{21} & G_{22} & G_{23} & G_{24} \\ G_{31} & G_{32} & G_{33} & G_{34} \\ G_{41} & G_{42} & G_{43} & G_{44} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix} = \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix}$$



$$\begin{aligned} i_1 &= 3A \\ i_2 &= -1 - 2 = -3A \\ i_3 &= 0A \\ i_4 &= 2 + 4 = 6A \end{aligned} \rightarrow \begin{bmatrix} 0,3 & -0,2 & 0 & 0 \\ -0,2 & 1,325 & -0,125 & -1 \\ 0 & -0,125 & 0,5 & -0,125 \\ 0 & -1 & -0,125 & 1,625 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix} = \begin{bmatrix} 3 \\ -3 \\ 0 \\ 6 \end{bmatrix}$$

## II.3. Nodal analysis by inspection

Ex 3.6: Write the node voltage matrix equations for this circuit.

➤ There are 4 non-reference nodes


$$\begin{bmatrix} G_{11} & G_{12} & G_{13} & G_{14} \\ G_{21} & G_{22} & G_{23} & G_{24} \\ G_{31} & G_{32} & G_{33} & G_{34} \\ G_{41} & G_{42} & G_{43} & G_{44} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix} = \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix}$$

$$G_{11} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = 1,3S$$

$$G_{33} = \frac{1}{R_3} + \frac{1}{R_4} = 1,25S$$

$$G_{22} = \frac{1}{R_2} = 0,2S$$
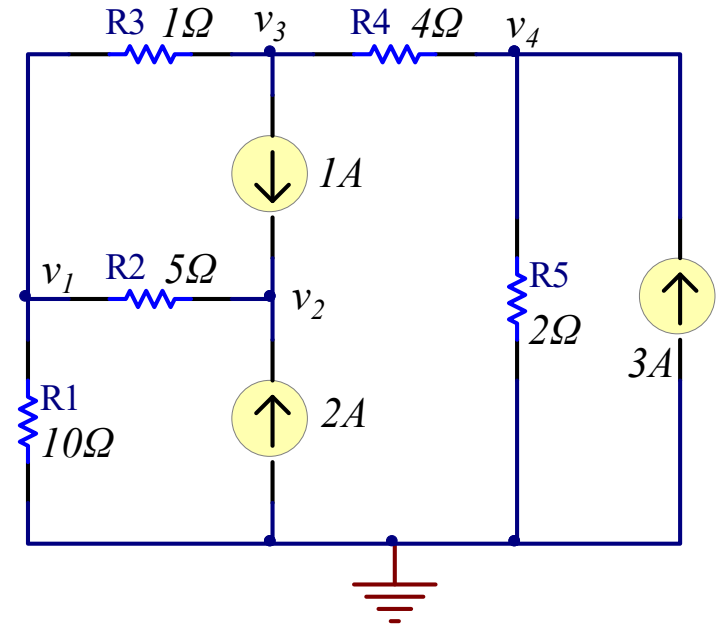
$$G_{44} = \frac{1}{R_4} + \frac{1}{R_5} = 0,75S$$





## Chapter 3: Methods of analysis



### II.3. Nodal analysis by inspection

Ex 3.6: Write the node voltage matrix equations for this circuit.


➤ There are 4 non-reference nodes

$$\begin{bmatrix} G_{11} & G_{12} & G_{13} & G_{14} \\ G_{21} & G_{22} & G_{23} & G_{24} \\ G_{31} & G_{32} & G_{33} & G_{34} \\ G_{41} & G_{42} & G_{43} & G_{44} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix} = \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix}$$

$$G_{12} = G_{21} = -\frac{1}{R_2} = -0,2S \quad G_{23} = G_{32} = 0$$

$$G_{13} = G_{31} = -\frac{1}{R_3} = -1S \quad G_{24} = G_{42} = 0$$

$$G_{14} = G_{41} = 0$$

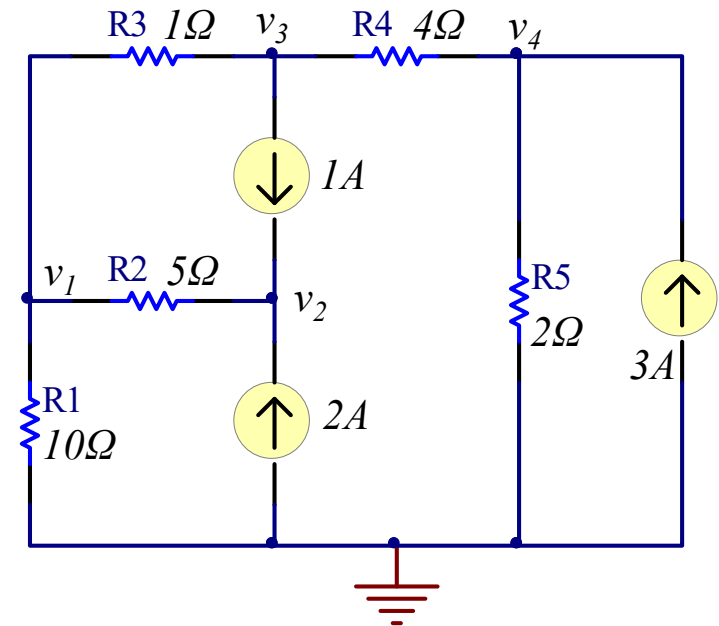


$$G_{34} = G_{43} = -\frac{1}{R_4} = -0,25S$$

## II.3. Nodal analysis by inspection

Ex 3.6: Write the node voltage matrix equations for this circuit.

➤ There are 4 non-reference nodes

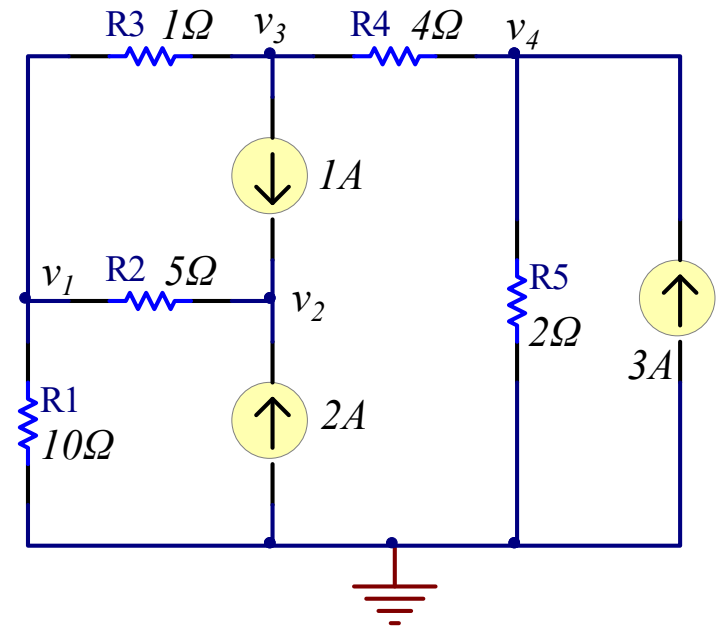

$$\begin{bmatrix} G_{11} & G_{12} & G_{13} & G_{14} \\ G_{21} & G_{22} & G_{23} & G_{24} \\ G_{31} & G_{32} & G_{33} & G_{34} \\ G_{41} & G_{42} & G_{43} & G_{44} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix} = \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix}$$

$$i_1 = 0$$

$$i_2 = 1 + 2 = 3A$$

$$i_3 = -1A$$

$$i_4 = 3A$$

$$\rightarrow \begin{bmatrix} 1,3 & -0,2 & -1 & 0 \\ -0,2 & 0,2 & 0 & 0 \\ -1 & 0 & 1,25 & -0,25 \\ 0 & 0 & -0,25 & 0,75 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix} = \begin{bmatrix} 0 \\ 3 \\ -1 \\ 3 \end{bmatrix}$$



## Chapter 3: Methods of analysis




### III. Mesh analysis

- Mesh analysis provides another general procedure for analyzing circuits, using *mesh current as the circuit variables* (known as loop analysis or the mesh current method).
- Using mesh current as the circuit variables is convenient and *reduces the number of equations*.
- A *mesh* is a loop that does not contain any other loop within it.
- Mesh analysis applies KVL to find unknown currents, and it is only applicable to a planar circuit.
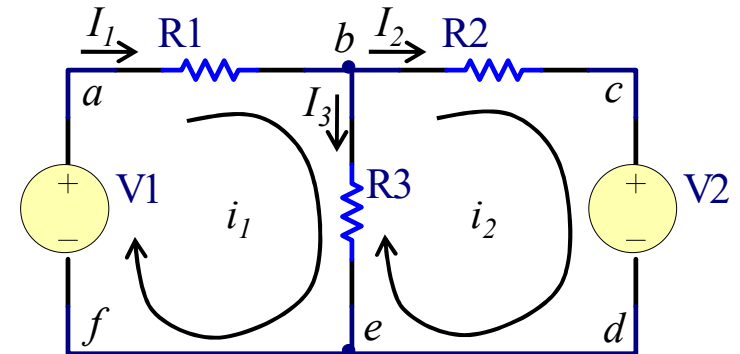
## III.1. Mesh analysis without current sources


- In this circuit, there are two meshes: *abefa*, and *bcdeb* (*abcdefa* is not a mesh)
- The current through a mesh is known as **mesh current**.



- **Steps to determine mesh currents:**
  - ❖ Assign mesh current  $i_1, i_2, \dots, i_n$  to the  $n$  meshes.
  - ❖ Apply KVL to each of the  $n$  meshes. Use Ohm's law to express the voltages in terms of the mesh currents.
  - ❖ Solve the resulting  $n$  equations to get the mesh currents.
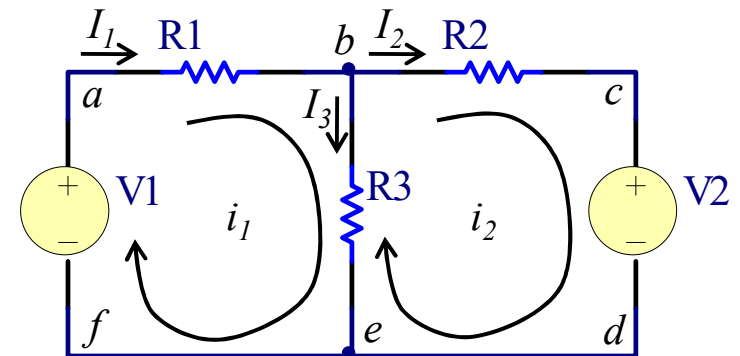
## III.1. Mesh analysis without current sources

- A mesh current may be assigned to each mesh (clockwise or counterclockwise)
- Applying KVL to mesh I, II gives:



$$\begin{aligned} \text{❖ Mesh I: } (R_1 + R_3)i_1 - R_3i_2 &= V_1 \\ \text{❖ Mesh II: } -R_3i_1 + (R_2 + R_3)i_2 &= -V_2 \end{aligned} \rightarrow \begin{bmatrix} R_1 + R_3 & -R_3 \\ -R_3 & R_2 + R_3 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ -V_2 \end{bmatrix}$$

- After solving, we calculate the current elements:  $I_1 = i_1$  ;  $I_2 = i_2$  ;  $I_3 = i_1 - i_2$

### ➤ Notes:

- ❖ A circuit:  $n$  nodes,  $b$  branches, and  $l$  independent loops (mesh)

$$l = b - n + 1$$

- ❖ The branch currents are different from the mesh currents unless the mesh is isolated.



## III.1. Mesh analysis without current sources

Ex 1: Find the branch current  $I_1$ ,  $I_2$ ,  $I_3$  using mesh analysis in this circuit.

➤ Applying KVL gives:


❖ Mesh I:  $-15 + 5i_1 + 10(i_1 - i_2) + 10 = 0$

❖ Mesh II:  $6i_2 + 4i_2 + 10(i_2 - i_1) - 10 = 0$

$$\rightarrow \begin{cases} 3i_1 - 2i_2 = 1 \\ i_1 - 2i_2 = -1 \end{cases} \rightarrow \begin{cases} i_1 = 1A \\ i_2 = 1A \end{cases}$$

➤ The current elements are:
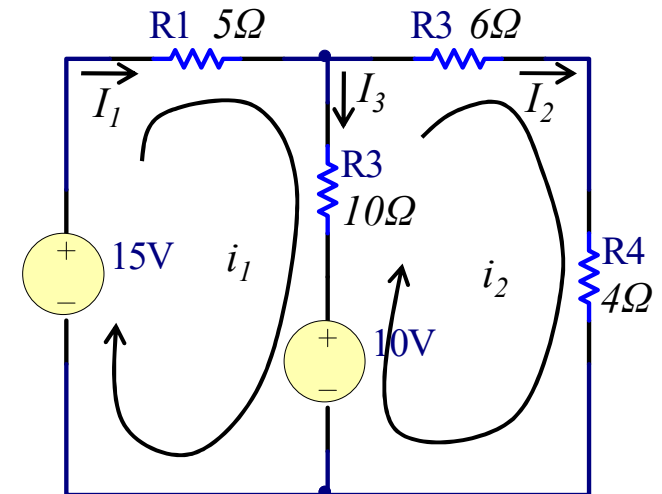
$$I_1 = i_1 = 1A \quad ; \quad I_2 = i_2 = 1A \quad ; \quad I_3 = i_1 - i_2 = 0$$



## III.1. Mesh analysis without current sources

Ex 2: Find the current  $i_0$  in this circuit using mesh analysis.

➤ Applying KVL gives:

❖ Mesh I:  $-24 + 10(i_1 - i_2) + 12(i_1 - i_3) = 0$

$$11i_1 - 5i_2 - 6i_3 = 12$$


❖ Mesh II:  $24i_2 + 4(i_2 - i_3) + 10(i_2 - i_1) = 0$

$$-5i_1 + 19i_2 - 2i_3 = 0$$

❖ Mesh III:  $4i_0 + 12(i_3 - i_1) + 4(i_3 - i_2) = 0$

$$i_0 = i_1 - i_2 \quad \left. \vphantom{i_0 = i_1 - i_2} \right\} \rightarrow -i_1 - i_2 + 2i_3 = 0$$

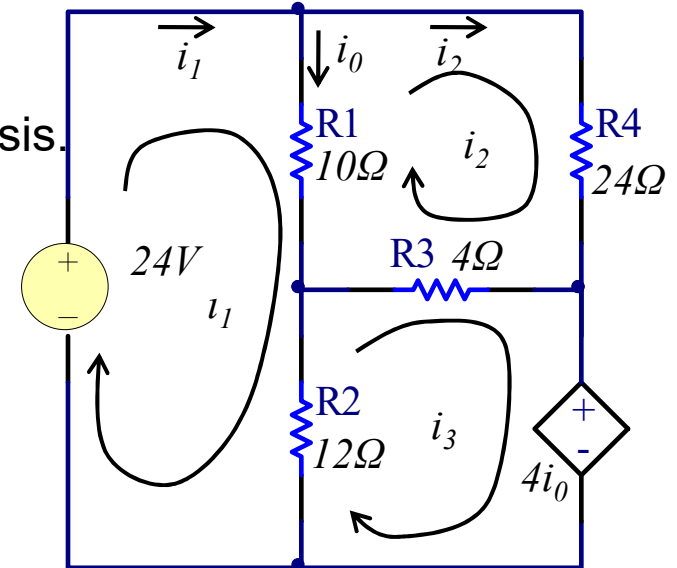➤ Then: 
$$\begin{cases} 11i_1 - 5i_2 - 6i_3 = 12 \\ -5i_1 + 19i_2 - 2i_3 = 0 \\ -i_1 - i_2 + 2i_3 = 0 \end{cases} \rightarrow \begin{cases} i_1 = 2,25A \\ i_2 = 0,75A \\ i_3 = 1,5A \end{cases} \rightarrow i_0 = i_1 - i_2 = 1,5A$$



## III.1. Mesh analysis without current sources

Ex 3: Find the current  $i_0$  in this circuit using mesh analysis.

➤ Applying KVL gives:


❖ Mesh I:  $-20 + 4(i_1 - i_3) + 2(i_1 - i_2) = 0$

$$6i_1 - 2i_2 - 4i_3 = 20$$

❖ Mesh II:  $2(i_2 - i_1) + 8(i_2 - i_3) - 10i_0 = 0$   
 $i_0 = i_3$  }  $\rightarrow -2i_1 + 10i_2 - 18i_3 = 0$


❖ Mesh III:  $4(i_3 - i_1) + 8(i_3 - i_2) + 6i_3 = 0 \rightarrow -4i_1 - 8i_2 + 18i_3 = 0$

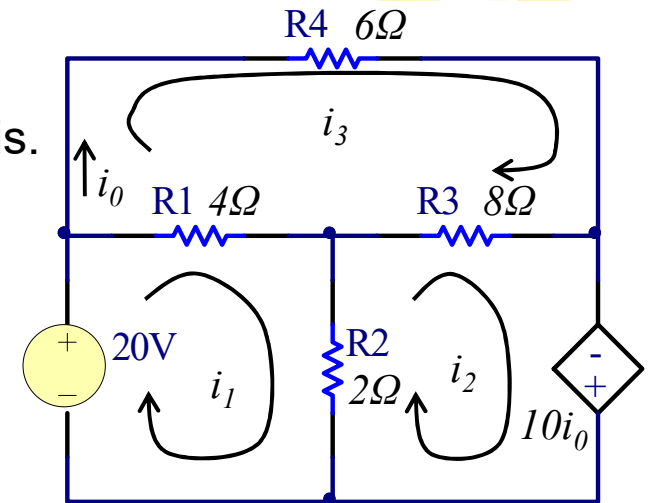➤ Set of equations: 
$$\begin{cases} 6i_1 - 2i_2 - 4i_3 = 20 \\ -2i_1 + 10i_2 - 18i_3 = 0 \\ -4i_1 - 8i_2 + 18i_3 = 0 \end{cases} \rightarrow \begin{cases} i_1 = -3,21A \\ i_2 = -9,64A \\ i_3 = -5A \end{cases} \rightarrow i_0 = -5A$$


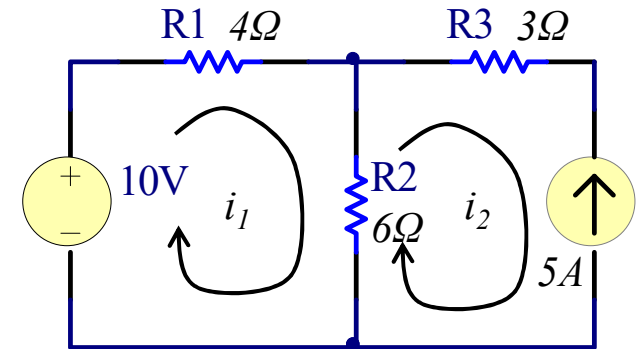
## III.2. Mesh analysis with current sources

- In general, the presence of the current sources reduces the number of equations in the mesh analysis.



- Consider two cases:

- ❖ A current source exists only in one mesh → mesh current = current source

$$\begin{cases} 4i_1 + 6(i_1 - i_2) = 10 \\ i_2 = -5A \end{cases} \rightarrow \begin{cases} i_1 = -2A \\ i_2 = -5A \end{cases}$$

- ❖ A current source exists between two meshes → create a **super-mesh** by excluding the current source and any elements connected in series with it

A **super-mesh** results when two meshes have a (dependent or independent) current source in common.

## III.2. Mesh analysis with current sources

Ex 1: Find the branch currents using mesh analysis.

- There is a current source 6-A between two mesh.
- Create a super-mesh.

- Applying KVL to the super-mesh gives:



$$-20 + 6i_1 + 10i_2 + 4i_2 = 0 \rightarrow 6i_1 + 14i_2 = 20$$

- Applying KCL to the node in the current source branch :

$$i_2 = i_1 + 6$$

- **Note that:**

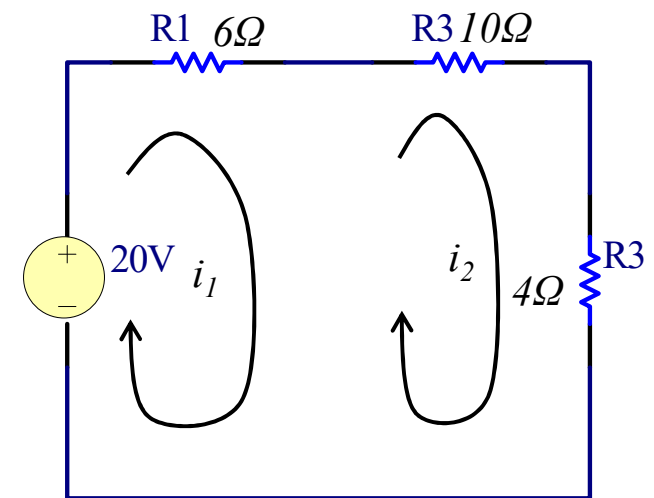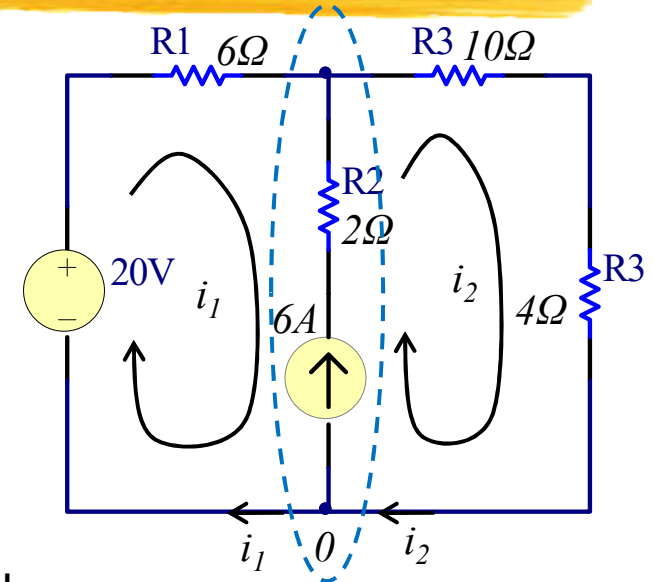- The current source in the super-mesh provides the constraint equation to solve for the mesh currents
- A super-mesh has no current of its own
- A super-mesh requires the using of both KVL and KCL



## III.2. Mesh analysis with current sources

Ex 2: Find  $i_1$ ,  $i_4$  using mesh analysis.

- There are two super-meshes
- Two super-meshes intersect  $\rightarrow$  form a larger super-mesh
- Applying KVL to the larger super-mesh:


$$2i_1 + 4i_3 + 8(i_3 - i_4) + 6i_2 = 0$$

$$\rightarrow i_1 + 3i_2 + 6i_3 - 4i_4 = 0$$

- Applying KCL to the node  $P$ :  $i_2 = i_1 + 5$

- Applying KCL to the node  $Q$ :  $i_2 = i_3 + 3i_0 \xrightarrow{i_0 = -i_4} i_2 = i_3 - 3i_4$

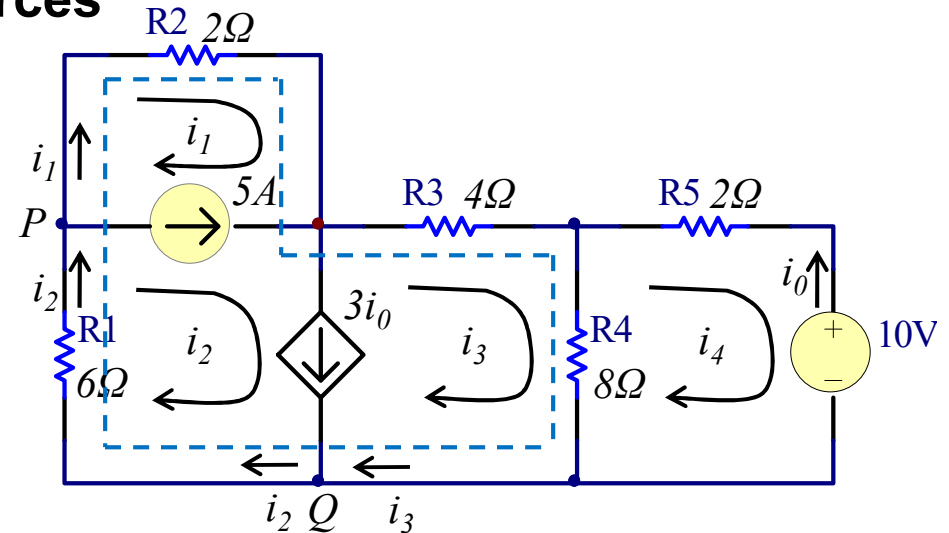- Applying KVL in mesh 4:  $2i_4 + 8(i_4 - i_3) + 10 = 0 \rightarrow 5i_4 - 4i_3 = -5$



- These equations give:

$$i_1 = -7.5A \quad i_2 = -2.5A$$

$$i_3 = 3.93A \quad i_4 = 2.14A$$

## III.2. Mesh analysis with current sources

Ex 3.3: Find  $i_1$ ,  $i_2$ ,  $i_3$  using mesh analysis.

- Applying KVL to super-mesh:

$$-6 + 2(i_1 - i_3) + 4(i_2 - i_3) + 8i_2 = 0$$


$$\rightarrow \boxed{2i_1 + 12i_2 - 6i_3 = 6}$$

- Applying KCL to node A gives:  $\boxed{i_1 - i_2 = 3}$

- Applying KCL to the mesh III:

$$2(i_3 - i_1) + 4(i_3 - i_2) + 2i_3 = 0 \rightarrow \boxed{-2i_1 - 4i_2 + 8i_3 = 0}$$

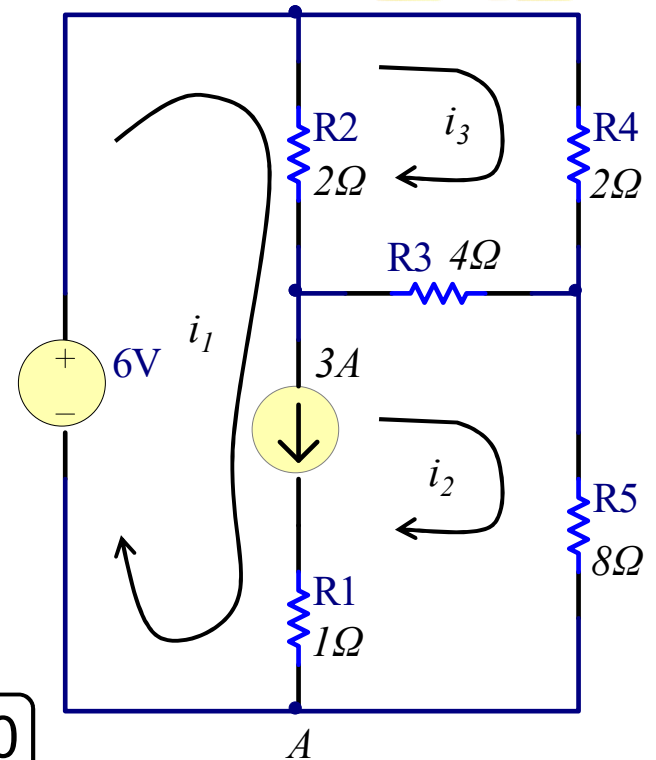- We have a set of equations: 
$$\begin{cases} 2i_1 + 12i_2 - 6i_3 = 6 \\ i_1 - i_2 = 3 \\ -2i_1 - 4i_2 + 8i_3 = 0 \end{cases} \rightarrow \begin{cases} i_1 = 3,47A \\ i_2 = 0,47A \\ i_3 = 1,11A \end{cases}$$



## III.3. Mesh analysis by inspection

- In general, if a circuit (with only *independent voltage sources*) has  $N$  meshes, the mesh current equations can be expressed in terms of the resistances as:

$$\begin{bmatrix} R_{11} & R_{12} & \dots & R_{1N} \\ R_{21} & R_{22} & \dots & R_{2N} \\ \vdots & \vdots & \vdots & \vdots \\ R_{N1} & R_{N2} & \dots & R_{NN} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ \vdots \\ i_N \end{bmatrix} = \begin{bmatrix} v_1 \\ v_2 \\ \vdots \\ v_N \end{bmatrix} \quad \Leftrightarrow \quad \mathbf{R} = \mathbf{v}$$

where:

- ❖  $R_{kk}$ : Sum of the resistances in mesh  $k$ .
- ❖  $R_{kj} = R_{jk}$ : Negative of the sum of the resistances in common with meshes  $k$  and  $j$ ,  $k \neq j$ .
- ❖  $i_k$ : Unknown mesh current for mesh  $k$  in the clockwise direction.
- ❖  $v_k$ : Sum taken clockwise of all independent voltage sources in mesh  $k$ , with voltage rise treated as positive.



## III.3. Mesh analysis by inspection

Ex 3.4: Write the mesh current equations.


➤ There are 5 meshes

$$\begin{bmatrix} R_{11} & R_{12} & R_{13} & R_{14} & R_{15} \\ R_{21} & R_{22} & R_{23} & R_{24} & R_{25} \\ R_{31} & R_{32} & R_{33} & R_{34} & R_{35} \\ R_{41} & R_{42} & R_{43} & R_{44} & R_{45} \\ R_{51} & R_{52} & R_{53} & R_{54} & R_{55} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \end{bmatrix}$$

$$R_{11} = R_6 + R_8 + R_{10} = 9\Omega$$

$$R_{22} = R_2 + R_4 + R_5 + R_6 + R_7 = 10\Omega$$
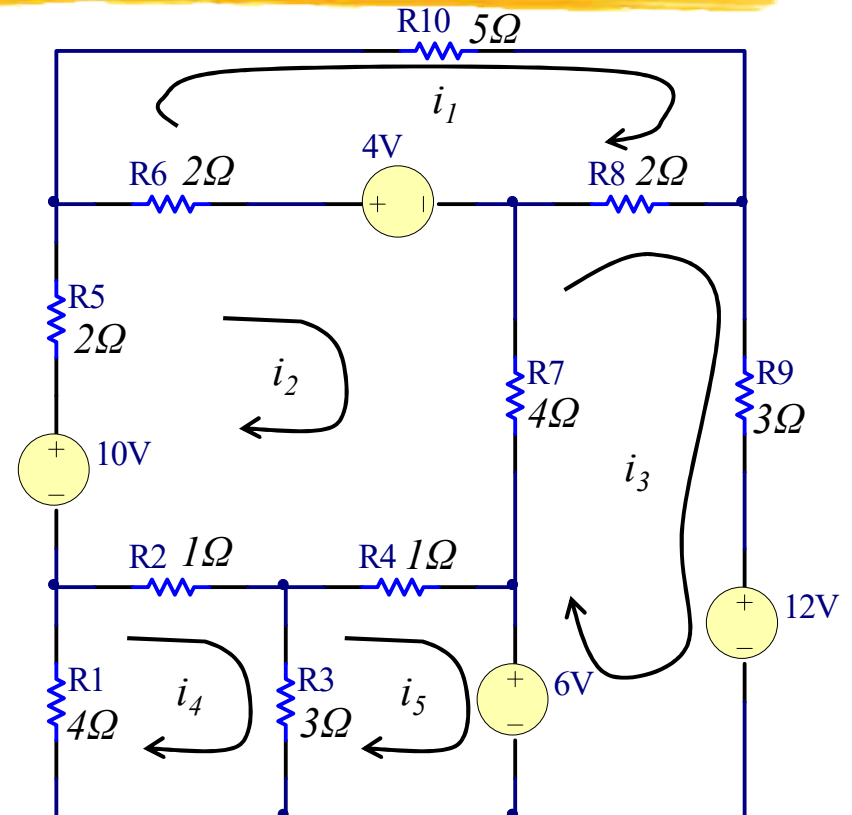
$$R_{33} = R_7 + R_8 + R_9 = 9\Omega \quad R_{44} = R_1 + R_2 + R_3 = 8\Omega \quad R_{55} = R_3 + R_4 = 4\Omega$$




## III.3. Mesh analysis by inspection

Ex 3.4: Write the mesh current equations.

➤ There are 5 meshes
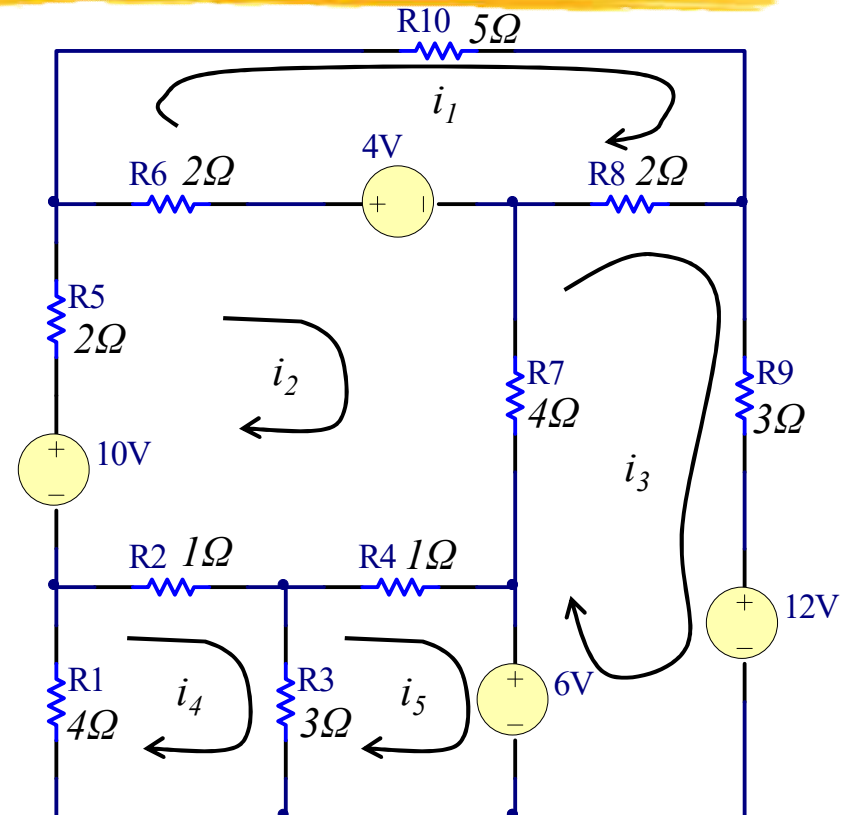
$$\begin{bmatrix} R_{11} & R_{12} & R_{13} & R_{14} & R_{15} \\ R_{21} & R_{22} & R_{23} & R_{24} & R_{25} \\ R_{31} & R_{32} & R_{33} & R_{34} & R_{35} \\ R_{41} & R_{42} & R_{43} & R_{44} & R_{45} \\ R_{51} & R_{52} & R_{53} & R_{54} & R_{55} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \end{bmatrix}$$



$$R_{12} = R_{21} = -R_6 = -2\Omega$$

$$R_{13} = R_{31} = -R_8 = -2\Omega \quad R_{23} = R_{32} = -R_7 = -4\Omega \quad R_{34} = R_{43} = 0$$

$$R_{14} = R_{41} = 0 \quad R_{24} = R_{42} = -R_2 = -1\Omega \quad R_{35} = R_{53} = 0$$

$$R_{15} = R_{51} = 0 \quad R_{25} = R_{52} = -R_4 = -1\Omega \quad R_{45} = R_{54} = -R_3 = -3\Omega$$


## III.3. Mesh analysis by inspection

Ex 3.4: Write the mesh current equations.

➤ There are 5 meshes

$$\begin{bmatrix} R_{11} & R_{12} & R_{13} & R_{14} & R_{15} \\ R_{21} & R_{22} & R_{23} & R_{24} & R_{25} \\ R_{31} & R_{32} & R_{33} & R_{34} & R_{35} \\ R_{41} & R_{42} & R_{43} & R_{44} & R_{45} \\ R_{51} & R_{52} & R_{53} & R_{54} & R_{55} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \end{bmatrix}$$
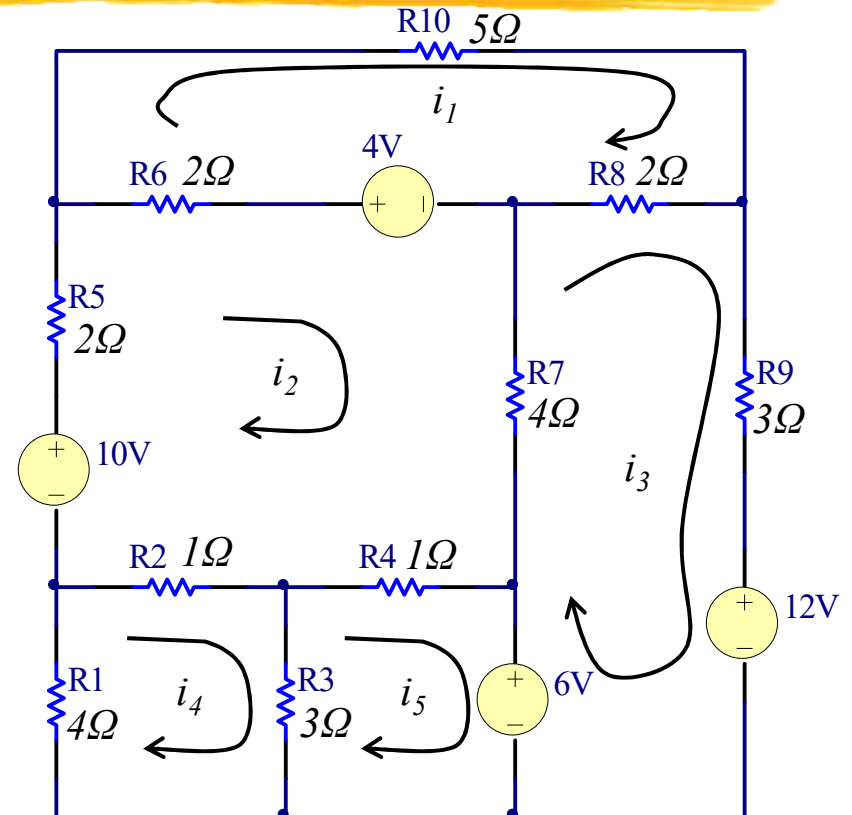
$$\rightarrow \begin{bmatrix} 9 & -2 & -2 & 0 & 0 \\ -2 & 10 & -4 & -1 & -1 \\ -2 & -4 & 9 & 0 & 0 \\ 0 & -1 & 0 & 8 & -3 \\ 0 & -1 & 0 & -3 & 4 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix} = \begin{bmatrix} 4 \\ 6 \\ -6 \\ 0 \\ -6 \end{bmatrix}$$



$$V_1 = 4V$$

$$V_4 = 0$$

$$V_2 = 10 - 4 = 6V$$

$$V_5 = -6V$$


$$V_3 = 6 - 12 = -6V$$

## III.3. Mesh analysis by inspection

Ex 3.5: Write the mesh current equations.

➤ There are 5 meshes
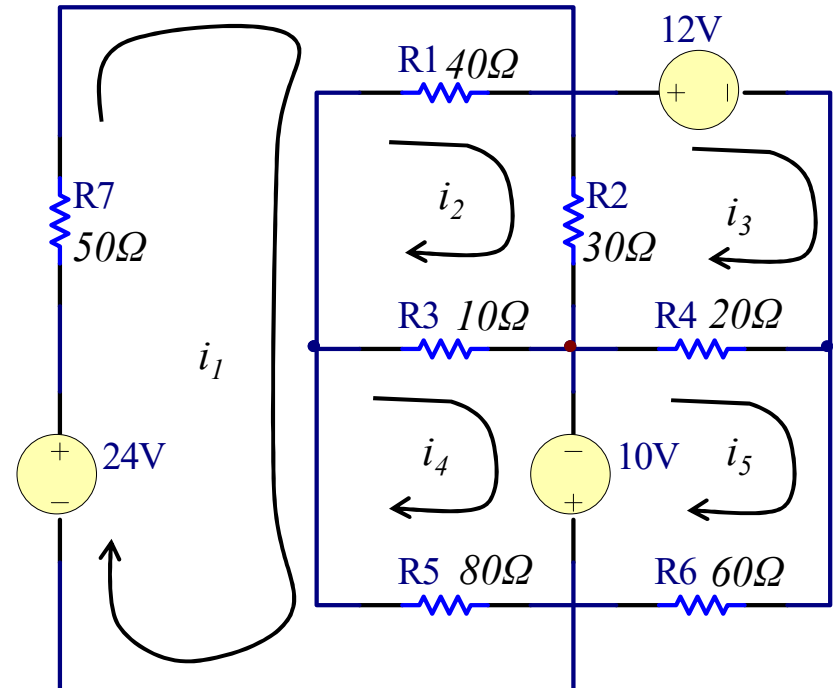
$$\begin{bmatrix} R_{11} & R_{12} & R_{13} & R_{14} & R_{15} \\ R_{21} & R_{22} & R_{23} & R_{24} & R_{25} \\ R_{31} & R_{32} & R_{33} & R_{34} & R_{35} \\ R_{41} & R_{42} & R_{43} & R_{44} & R_{45} \\ R_{51} & R_{52} & R_{53} & R_{54} & R_{55} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \end{bmatrix}$$



$$R_{11} = R_1 + R_5 + R_7 = 170\Omega$$

$$R_{22} = R_1 + R_2 + R_3 = 80\Omega$$

$$R_{33} = R_2 + R_4 = 50\Omega$$

$$R_{44} = R_3 + R_5 = 90\Omega$$


$$R_{55} = R_4 + R_6 = 80\Omega$$

## III.3. Mesh analysis by inspection

Ex 3.5: Write the mesh current equations.

➤ There are 5 meshes
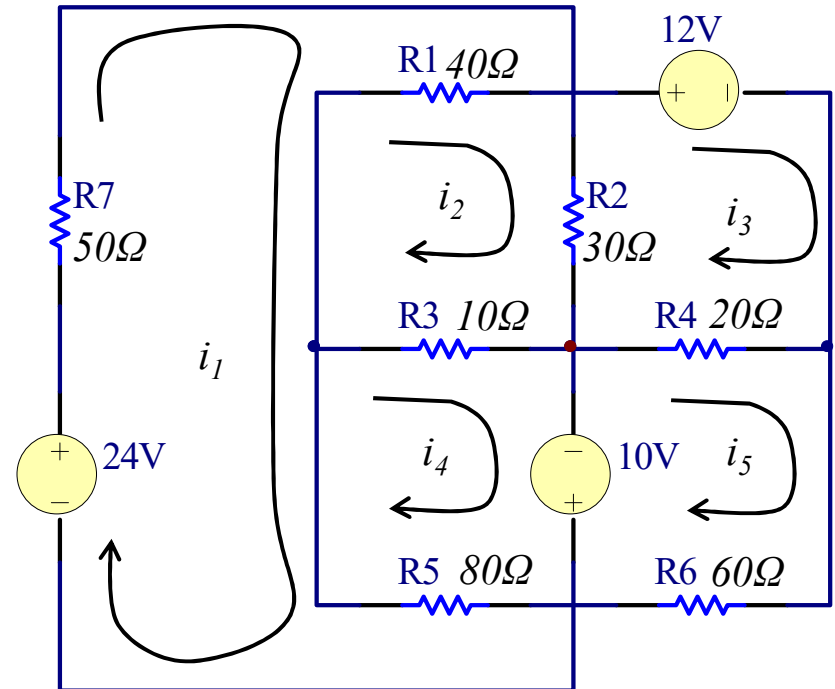
$$\begin{bmatrix} R_{11} & R_{12} & R_{13} & R_{14} & R_{15} \\ R_{21} & R_{22} & R_{23} & R_{24} & R_{25} \\ R_{31} & R_{32} & R_{33} & R_{34} & R_{35} \\ R_{41} & R_{42} & R_{43} & R_{44} & R_{45} \\ R_{51} & R_{52} & R_{53} & R_{54} & R_{55} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \end{bmatrix}$$



$$R_{12} = R_{21} = -R_1 = -40\Omega$$

$$R_{13} = R_{31} = 0$$

$$R_{23} = R_{32} = -R_2 = -30\Omega$$

$$R_{34} = R_{43} = 0$$

$$R_{14} = R_{41} = -R_5 = -80\Omega$$

$$R_{24} = R_{42} = -R_3 = -10\Omega$$

$$R_{35} = R_{53} = -R_4 = -20\Omega$$

$$R_{15} = R_{51} = 0$$

$$R_{25} = R_{52} = 0$$


$$R_{45} = R_{54} = 0$$

## III.3. Mesh analysis by inspection

Ex 3.5: Write the mesh current equations.

➤ There are 5 meshes
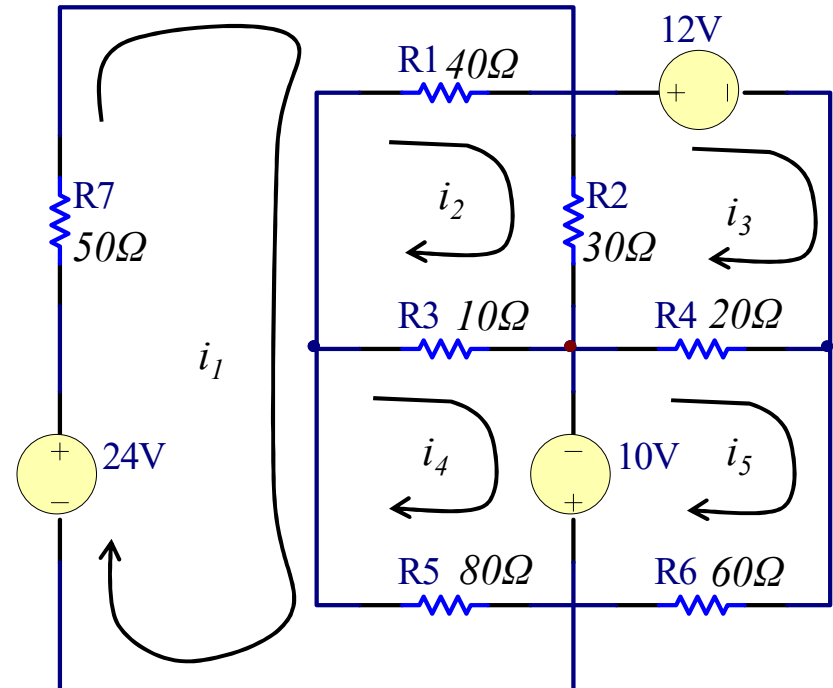
$$\begin{bmatrix} R_{11} & R_{12} & R_{13} & R_{14} & R_{15} \\ R_{21} & R_{22} & R_{23} & R_{24} & R_{25} \\ R_{31} & R_{32} & R_{33} & R_{34} & R_{35} \\ R_{41} & R_{42} & R_{43} & R_{44} & R_{45} \\ R_{51} & R_{52} & R_{53} & R_{54} & R_{55} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \end{bmatrix}$$



$$\rightarrow \begin{bmatrix} 170 & -40 & 0 & -80 & 0 \\ -40 & 80 & -30 & -10 & 0 \\ 0 & -30 & 50 & 0 & -20 \\ -80 & -10 & 0 & 90 & 0 \\ 0 & 0 & -20 & 0 & 80 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix} = \begin{bmatrix} 24 \\ 0 \\ -12 \\ 10 \\ -10 \end{bmatrix}$$

$$V_1 = 24V$$

$$V_4 = 10V$$

$$V_2 = 0$$

$$V_5 = -10V$$

$$V_3 = -12V$$



## Chapter 3: Methods of analysis



### IV. Nodal versus Mesh analysis

- Nodal and mesh analyses provide a systematic way of analyzing a complex network.
- **Question: Given a network, which method is better or more efficient ?**
  - ❖ Select method that results in the *smaller number of equations*
    - ❑ **Mesh analysis** → many series-connected elements, voltage sources, or super-meshes; **nodal analysis** → parallel-connected elements, current sources, or super-nodes.
    - ❑ Circuits have  $n < l \rightarrow$  nodal analysis; but  $l < n \rightarrow$  mesh analysis.
  - ❖ *Information required:*
    - ❑ Node voltages are required → nodal analysis.
    - ❑ Branch or mesh currents are required → mesh analysis.
  - ❖ *Particular problems:* Analyzing transistor , op amp circuits, or non-planar circuit.