



FUNDAMENTALS OF ELECTRIC CIRCUITS

Part 1: DC CIRCUITS



Chapter 6: Capacitors and Inductors

I. Introduction.

II. Capacitors.

III. Series and parallel capacitors.

VI. Inductors.

V. Series and parallel inductors.

VI. Applications.



Chapter 6: Capacitors and Inductors



I. Introduction

- So far we have limited our study to *resistive circuits*. In this chapter, we shall introduce two new and important passive linear circuit elements:
 - ❖ The capacitor
 - ❖ The inductors
- Capacitors and inductors *do not dissipate but store energy* which can be retrieved at a later time → be called *storage elements*.
- With the introduction of capacitors and inductors, we will be able to analyze more important and practical circuits (applying the circuit analysis techniques)
- Applications: Capacitors can be combined with op amps to form *integrators, differentiators, and analog computers*.


II. Capacitors

- A capacitor is a passive element designed to store energy in its electric field.
- A **capacitor** consists of two conducting plates separated by an insulators (or dielectric) (*air, ceramic, paper, mica*).


- When a voltage v is connected:
 - ❖ Positive charge q on one plate
 - ❖ Negative charge $-q$ on the other

$$q = Cv$$

$$1F = \frac{1C}{1V}$$

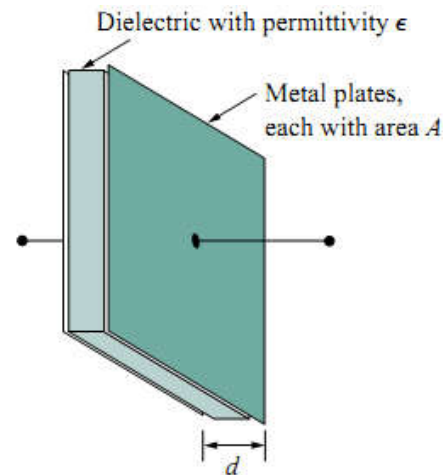

A typical capacitor

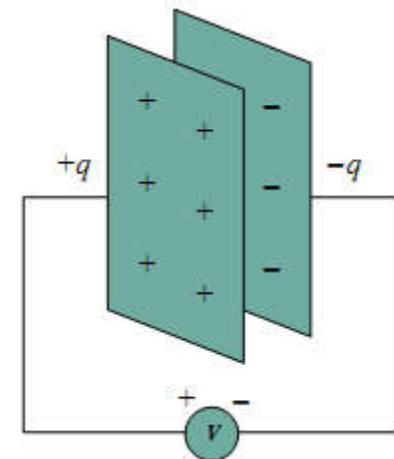

A capacitor with applied voltage v

- **Capacitance** is the ratio of the charge on one plate of a capacitor to the voltage difference between the two plates, measured in farads (**F**)

II. Capacitors

- Capacitance C depend on its physical dimension (not q and v)


$$C = \frac{\epsilon A}{d}$$

Apply only for parallel plate capacitors

A : surface area of each plate


d : distance between the plates

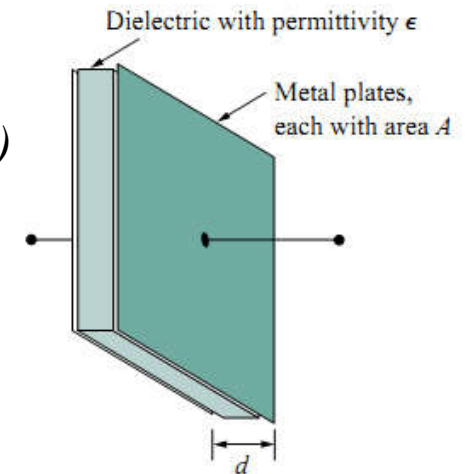ϵ : the permittivity of the dielectric material between the plates




A typical capacitor

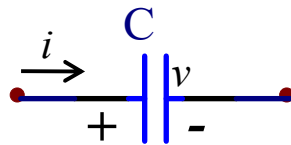
- Typically, capacitors have values in the pF to μF



Fix, un-polarized capacitor

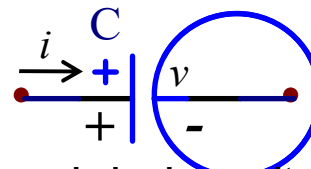

Fix, polarized capacitor

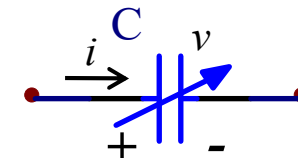

Variable capacitor



Ceramic capacitor



Electrolytic capacitor



Trimmer capacitor



Chapter 6: Capacitors and Inductors




II. Capacitors

- Capacitors are used to block dc, pass ac, shift phase, store energy, start motors and suppress noise.

$$i = \frac{dq}{dt} = \frac{\partial q}{\partial u} \cdot \frac{dv}{dt} = C \frac{dv}{dt}$$
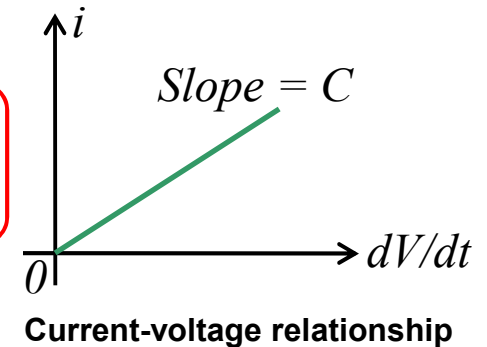
$$v = \frac{1}{C} \int_{-\infty}^t i dt = \frac{1}{C} \int_{t_0}^t i dt + v(t_0)$$



- Classification:

- ❖ *Linear capacitor* ← We focus only the linear capacitor
- ❖ *Nonlinear capacitor* (a few)

- Instantaneous power: $p = vi = Cv \frac{dv}{dt}$

- Energy: $w = \int_{-\infty}^t p \cdot dt = C \int_{-\infty}^t v \frac{dv}{dt} dt = \frac{1}{2} Cv^2 \Big|_{t=-\infty}^t \rightarrow w = \frac{1}{2} Cv^2 = \frac{q^2}{2C}$




Chapter 6: Capacitors and Inductors



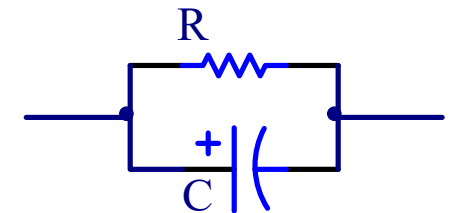II. Capacitors

➤ Properties of a capacitor:

- ❖ A capacitor is an *open circuit to DC*.
- ❖ The voltage on a capacitor *cannot change abruptly*: A discontinuous change in voltage requires an infinite current.
- ❖ The ideal capacitor does *not dissipate energy*: It takes power from the circuit when storing energy in its field and returns previously stored energy when delivering power to the circuit.
- ❖ A *non-ideal capacitor* has a parallel-model leakage resistance ($\sim 100\text{M}\Omega$ the leakage resistance may be neglected for most practical application).




Circuit model of a non-ideal capacitor

II. Capacitors

Ex 6.1: Determine the current through a $200\mu\text{F}$ capacitor whose voltage is


➤ The voltage can be described mathematically as:
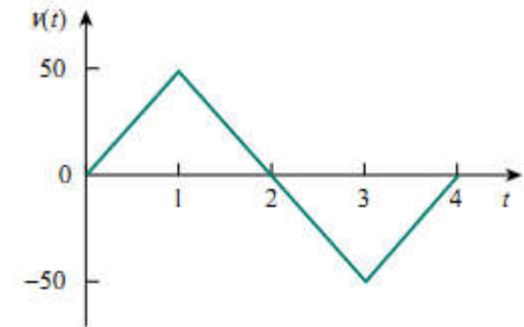
$$v(t) = \begin{cases} 50t \text{ V} & 0 < t < 1 \\ 100 - 50t \text{ V} & 1 < t < 3 \\ -200 + 50t \text{ V} & 3 < t < 4 \\ 0 \text{ V} & \text{otherwise} \end{cases}$$



➤ Applying $i = C dv/dt$ gives
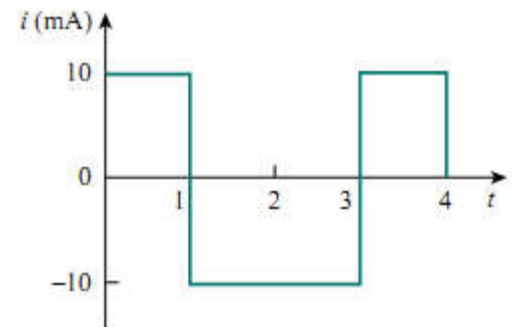
$$i(t) = 200 \cdot 10^{-6} \cdot \begin{cases} 50 \text{ V} & 0 < t < 1 \\ -50 \text{ V} & 1 < t < 3 \\ 50 \text{ V} & 3 < t < 4 \\ 0 \text{ V} & \text{otherwise} \end{cases} = \begin{cases} 10 \text{ mA} & 0 < t < 1 \\ -10 \text{ mA} & 1 < t < 3 \\ 10 \text{ mA} & 3 < t < 4 \\ 0 \text{ mA} & \text{otherwise} \end{cases}$$



II. Capacitors

Ex 6.2: Obtain the energy stored in each capacitor under DC condition

- Under DC conditions, each capacitor is an open circuit
- Applying the current division gives


$$i = \frac{R_1}{R_1 + R_2 + R_4} 6mA = 2mA$$

- The voltages across C_1 and C_2 are

$$v_1 = R_2 \cdot i = 2000 \cdot 2 \cdot 10^{-3} = 4V \quad v_2 = R_4 \cdot i = 4000 \cdot 2 \cdot 10^{-3} = 8V$$

- The energies stored in C_1 , C_2
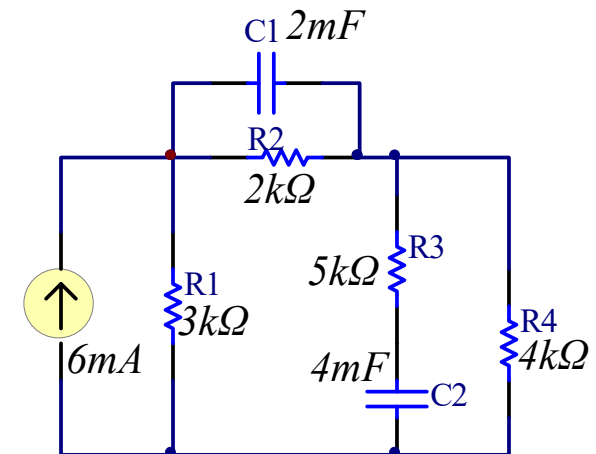
$$w_1 = \frac{1}{2} C_1 v_1^2 = 16mJ \quad ; \quad w_2 = \frac{1}{2} C_2 v_2^2 = 128mJ$$



III. Series and parallel capacitors



- In order to obtain the equivalent capacitor C_{eq} of N capacitors in parallel, we apply KCL

$$i = i_1 + i_2 + i_3 + \dots + i_N$$

$$\rightarrow i = C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt} + C_3 \frac{dv}{dt} + \dots + C_N \frac{dv}{dt}$$

$$\rightarrow i = \left(\sum_{k=1}^N C_k \right) \frac{dv}{dt} = C_{eq} \frac{dv}{dt}$$
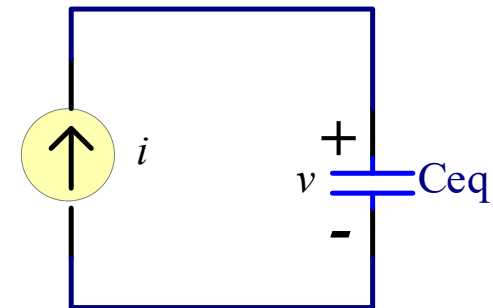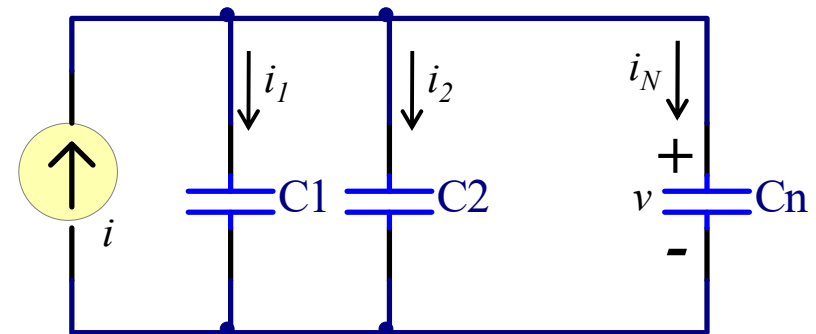
$$C_{eq} = C_1 + C_2 + C_3 + \dots + C_N$$



- The **equivalent capacitance** of N parallel-connected capacitors is the sum of the individual capacitances

III. Series and parallel capacitors

- Applying KVL to the loop:

$$V = V_1 + V_2 + V_3 + \dots + V_N$$



$$\text{But } v_k = \frac{1}{C_k} \int_{t_0}^t i dt + v_k(t_0)$$

$$\rightarrow v = \frac{1}{C_1} \int_{t_0}^t i dt + v_1(t_0) + \frac{1}{C_2} \int_{t_0}^t i dt + v_2(t_0) + \dots + \frac{1}{C_N} \int_{t_0}^t i dt + v_N(t_0)$$

$$\rightarrow v = \left(\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N} \right) \int_{t_0}^t i dt + v_1(t_0) + v_2(t_0) + \dots + v_N(t_0) = \frac{1}{C_{eq}} \int_{t_0}^t i dt + v(t_0)$$

- The **equivalent capacitance** of series-connected capacitors is the reciprocal of the sum of the reciprocals of the individual capacitances.
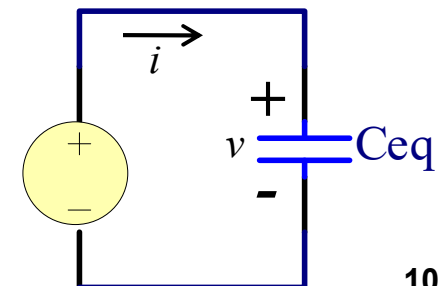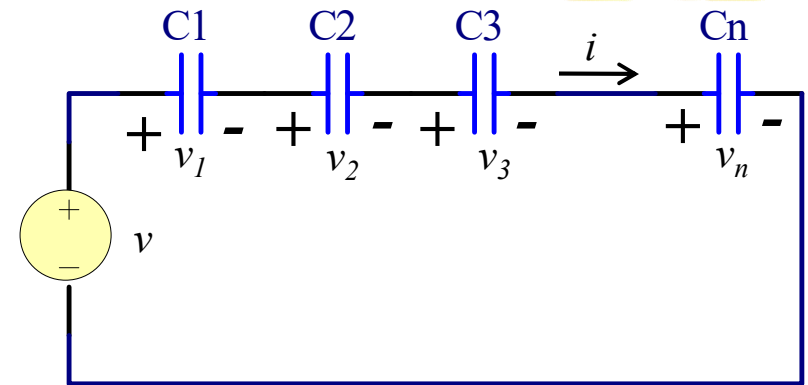
$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N}$$



III. Series and parallel capacitors

Ex 6.3: Find the voltage across each capacitor.

- C_3 and C_4 can be combined to get:

$$C_{34} = 40 + 20 = 60mF$$

- This capacitor is in series with C_1 and C_2


$$C_{eq} = \frac{1}{\frac{1}{C_{34}} + \frac{1}{C_1} + \frac{1}{C_2}} = 10mF$$

- The total charge: $q = C_{eq} v = 10 \cdot 10^{-3} \cdot 30 = 0,3C$ (charge on the C_1 and C_2)

$$\rightarrow v_1 = \frac{q}{C_1} = \frac{0,3}{20 \cdot 10^{-3}} = 15V ; \quad v_2 = \frac{q}{C_2} = \frac{0,3}{30 \cdot 10^{-3}} = 10V \rightarrow v_3 = 30 - v_1 - v_2 = 5V$$

- Another solution: $C_3 // C_4 \rightarrow C_{34} = 20 + 40 = 60mF$

$$\rightarrow C_{34} \text{ is in series with } C_1 \text{ and } C_2 \rightarrow v_3 = \frac{q}{C_{34}} = \frac{0,3}{60 \cdot 10^{-3}} = 5V$$

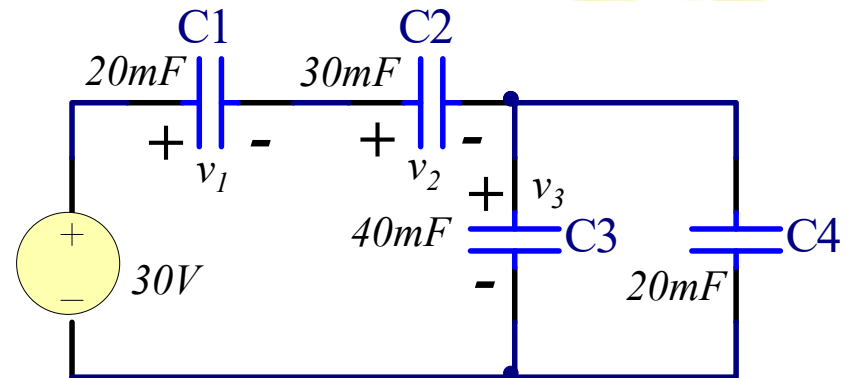




Chapter 6: Capacitors and Inductors



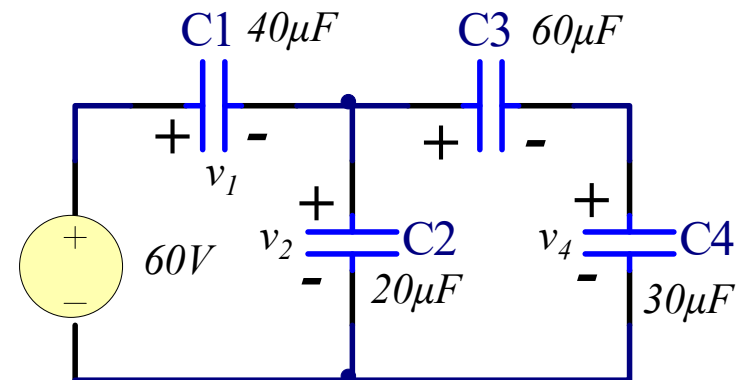
III. Series and parallel capacitors

Ex 6.4: Find the voltage across each capacitor.



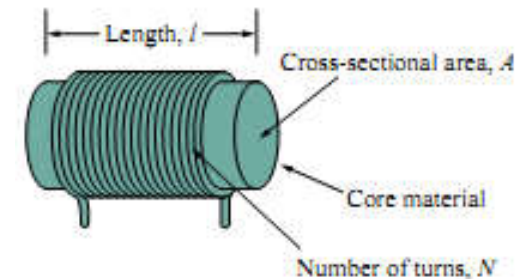
IV. Inductors

- *An inductor* is a passive element designed to store energy in its magnetic field.
- An inductor consists of a coil of conducting wire.
- If current is allowed to pass through an inductor, the voltage across the inductor is directly proportional to the time rate of change of the current.




Typical form of an inductor
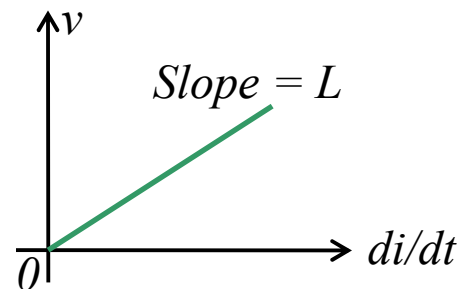
$$v = L \frac{di}{dt} ; i = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0)$$



Voltage-current relationship

L: inductance of the inductor [H]

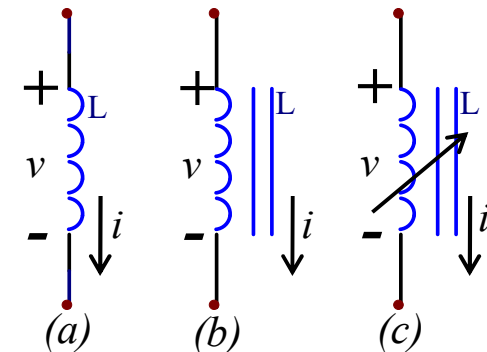

Circuit symbols for inductors: (a) air-core, (b) iron-core, (c) variable iron-core

IV. Inductors

➤ **Inductance** is the property whereby an inductor exhibits opposition to the change of current flowing through it, measured in [H]. It depends on:

- ❖ Physical dimension
- ❖ Construction

$$L = \frac{N^2 \mu A}{l}$$

N: number of turns

l: length of coil

A: cross-sectional area

μ : permeability of the core

➤ Inductor classification:

- ❖ Fixed - variable
- ❖ Linear - in-linear
- ❖ Core: iron, steel, plastic, air, ...



Toroidal inductor



Solenoidal
wound inductor



Inductor

IV. Inductors


➤ Power: $p = v \cdot i = \left(L \frac{di}{dt} \right) i$

➤ Energy:


$$w = \int_{-\infty}^t p dt = \int_{-\infty}^t \left(L \frac{di}{dt} \right) i dt = L \int_{-\infty}^t i di \rightarrow w = \frac{1}{2} Li^2$$

➤ Note that:

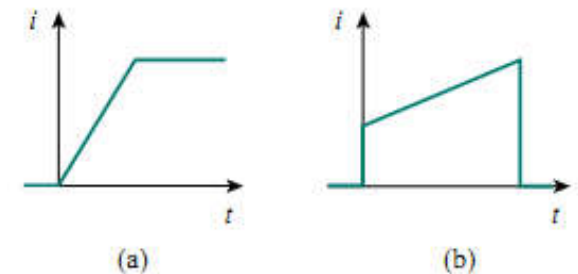- ❖ An inductor acts like a *short circuit to DC*
- ❖ The current *cannot change instantaneously*.
- ❖ The ideal inductor does *not dissipate energy*.
- ❖ *Non-ideal inductor* has a significant resistive component:
 - ❖ winding resistance (very small)
 - ❖ Winding capacitance (very small, except at high frequencies)



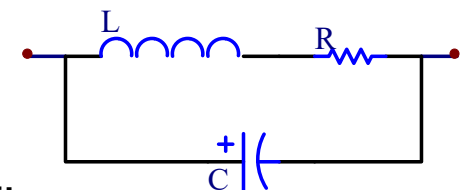Current through an inductor: (a) allowed, (b) not allowable, an abrupt change is not possible.



Circuit model for a practical inductor



Chapter 6: Capacitors and Inductors



IV. Inductors

Ex 6.5: Find the current through a 5H inductor and the energy stored within $0 < t < 5s$, if the its voltage is:

$$v(t) = \begin{cases} 30t^2, & t > 0 \\ 0, & t < 0 \end{cases}$$

➤ The current through the inductor:

$$i = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0) = \frac{1}{5} \int_0^t 30t^2 dt + 0 = 2t^3 (A)$$

➤ The power: $p = v.i = 60t^5$

➤ The energy: $w = \int p dt = \int_0^5 60t^5 dt = 60 \frac{t^6}{6} \Big|_0^5 = 156,25 kJ$

➤ The energy could be calculated by applying the equation:

$$w = \frac{1}{2} \cdot 5 \cdot (2 \cdot 5^3)^2 = 156,25 kJ$$



Chapter 6: Capacitors and Inductors



IV. Inductors

Ex 6.6: Find i , v_C , i_L , energy stored in the capacitor and inductor under DC condition.

➤ Under DC condition, replacing:


❖ capacitor \rightarrow open circuit

❖ Inductor \rightarrow short circuit

$$\rightarrow i = i_L = \frac{12V}{R_1 + R_3} = 2A \rightarrow v_C = R_3 \cdot i = 5 \cdot 2 = 10V$$

➤ The energy in the capacitor: $w_C = \frac{1}{2} C v_C^2 = \frac{1}{2} \cdot 1 \cdot 10^2 = 50J$

➤ The energy in the inductor: $w_L = \frac{1}{2} \cdot L \cdot i_L^2 = \frac{1}{2} \cdot 2 \cdot 2^2 = 4J$

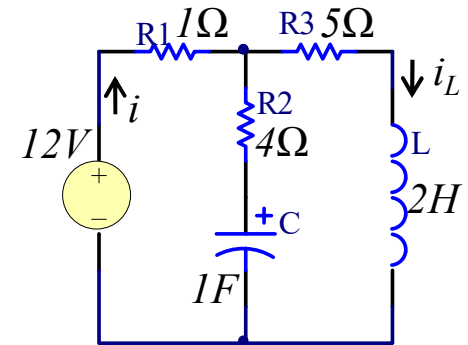



Chapter 6: Capacitors and Inductors



V. Series and parallel inductors

- Consider a series connection of N inductors



- ❖ Applying KVL to the loop:

$$V = V_1 + V_2 + V_3 + \dots + V_N$$

$$\rightarrow v = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + \dots + L_N \frac{di}{dt} = \left(\sum_{k=1}^N L_k \right) \frac{di}{dt} = L_{eq} \frac{di}{dt}$$

$$L_{eq} = L_1 + L_2 + L_3 + \dots + L_N$$

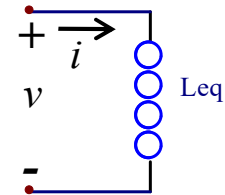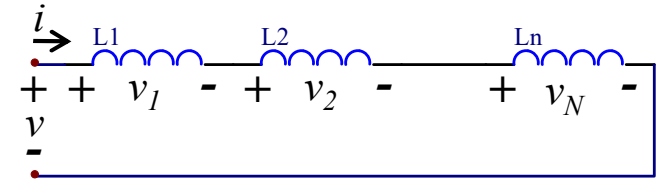- The equivalent inductance of series-connected inductors is the sum of the individual inductances.



V. Series and parallel inductors

➤ Consider a parallel connection of N inductors


❖ Applying KCL:

$$i = i_1 + i_2 + i_3 + \dots + i_N$$

$$\rightarrow i = \frac{1}{L_1} \int_{t_0}^t v dt + i_1(t_0) + \frac{1}{L_2} \int_{t_0}^t v dt + i_2(t_0) + \dots + \frac{1}{L_N} \int_{t_0}^t v dt + i_N(t_0)$$

$$\rightarrow i = \left(\sum_{k=1}^N \frac{1}{L_k} \right) \int_{t_0}^t v dt + \sum_{k=1}^N i_k(t_0) = \frac{1}{L_{eq}} \int_{t_0}^t v dt + i(t_0)$$
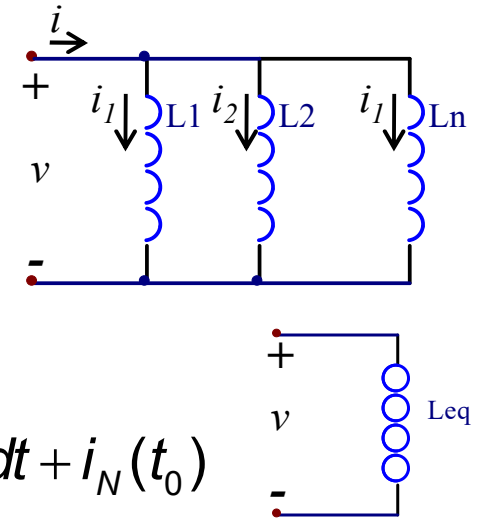
$$L_{eq} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N}}$$



➤ The equivalent inductance of parallel inductors is reciprocal of the sum of the reciprocals of the individual inductances.



Chapter 6: Capacitors and Inductors



V. Series and parallel inductors

Ex 6.7: Find $i_2(0)$, $v(t)$, $v_1(t)$, $v_2(t)$, $i_2(t)$, $i_n(t)$ if $i_1(t) = 4.(2 - e^{-10t})$ mA and $i_n(0) = -1$ mA.

➤ From $i_1(t) = 4.(2 - e^{-10t})$ mA $\rightarrow i_1(0) = 4.(2 - 1) = 4$ mA

$$i_1 = i_2 + i_n \rightarrow i_2(0) = i_1(0) - i_n(0) = 4 - (-1) = 5 \text{ mA}$$


➤ The equivalent inductance is

$$L_{eq} = (L_2 // L_N) + L_1 = 2 + \frac{4.12}{4 + 12} = 5 \text{ H}$$

➤ Thus: $v(t) = L_{eq} \frac{di_1}{dt} = 5.(-4).(-10)e^{-10t} = 200e^{-10t}$ mV

$$v_1(t) = 4 \frac{di_1}{dt} = 4.(-4).(-10)e^{-10t} = 80e^{-10t} \text{ mV}$$

➤ Thus: $v(t) = v_1 + v_2 \rightarrow v_2(t) = v(t) - v_1(t) = 120e^{-10t}$ mV

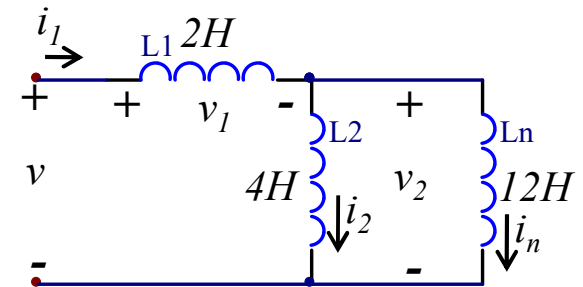



Chapter 6: Capacitors and Inductors



V. Series and parallel inductors

Ex 6.7: Find $i_2(0)$, $v(t)$, $v_1(t)$, $v_2(t)$, $i_2(t)$, $i_n(t)$ if $i_1(t) = 4 \cdot (2 - e^{-10t})$ mA and $i_n(0) = -1$ mA.


➤ Current i_1

$$i_2(t) = \frac{1}{4} \int_0^t v_2 dt + i_2(0) = \frac{120}{4} \int_0^t e^{-10t} dt + 5 = 8 - 3e^{-10t} \text{ (mA)}$$

➤ Current i_n

$$i_n(t) = \frac{1}{12} \int_0^t v_2 dt + i_n(0) = \frac{120}{12} \int_0^t e^{-10t} dt - 1 = -e^{-10t} \text{ (mA)}$$

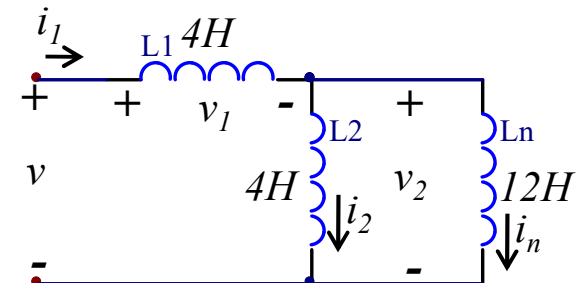
➤ For validation: $i_1(t) = i_2(t) + i_n(t)$





V. Series and parallel inductors

Ex 6.8: Find $i_2(0)$, $i_2(t)$, $i(t)$, $v(t)$, $v_1(t)$, $v_2(t)$ nếu $i_1(t) = 0,6.e^{-2t}$
và $i(0) = 1,4A$

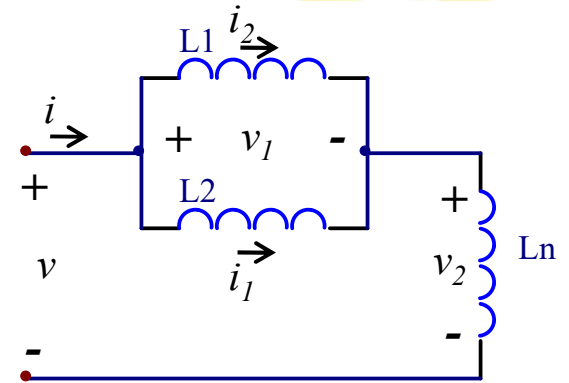



Chapter 6: Capacitors and Inductors




VI. Applications

- Circuit elements (R , C) are available in either discrete form or integrated circuit (IC) form, but inductance are difficult to produce on IC substrates.
- The inductor are used in some applications:
 - ❖ Relays, delays, sensing devices, pick-up head
 - ❖ Telephone circuits, radio, TV receivers
 - ❖ Power supplies, electric motors, microphones, loudspeakers
- Capacitors and inductors possess 03 special properties:
 - ❖ Useful for generating a current or voltage in short period of time (DC circuit).
 - ❖ Useful for suppression and converting pulsating DC voltage into relatively smooth DC voltage (DC circuit).
 - ❖ Useful for frequency discrimination (AC circuit).

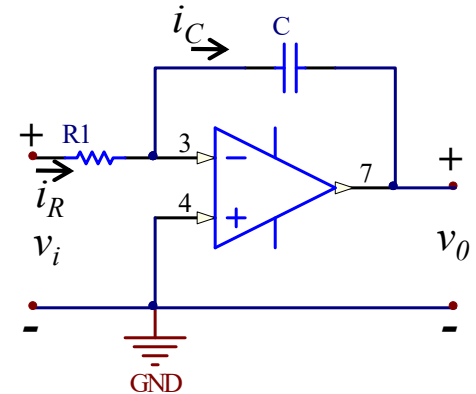VI. Applications

VI.1. Integrator

- An *integrator* is an op amp circuit whose output is proportional to the integral of the input signal.



- At node 3:

$$i_R = i_C \rightarrow \frac{v_i}{R} = i_R = i_C = -C \frac{dv_0}{dt} \rightarrow v_0(t) - v_0(0) = -\frac{1}{RC} \int_0^t v_i(t) dt$$

$$v_0(t) = -\frac{1}{RC} \int_0^t v_i(t) dt$$

- In practice, note that:
 - ❖ The op amp integrator requires a *feedback resistor to reduce DC gain and prevent saturation*.
 - ❖ The op amp operates within the *linear range* so that it does not saturate.

VI. Applications

VI.1. Integrator


Ex 6.9: Find v_o in the op amp circuit if $v_1 = 10.\cos 2t$ (mV) and $v_2 = 0,5t$ (mV) (assume that the voltage across the capacitor is initially zero)

➤ This is a summing integrator

$$v_o = -\frac{1}{R_1 C} \int v_1 dt - \frac{1}{R_2 C} \int v_2 dt$$

$$v_o = -\frac{1}{3 \cdot 10^6 \cdot 2 \cdot 10^{-6}} \int_0^t 10 \cos 2t dt - \frac{1}{100 \cdot 10^3 \cdot 2 \cdot 10^{-6}} \int_0^t 0,5t dt$$
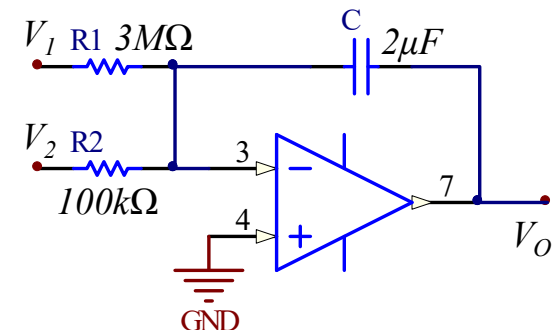
$$v_o = -\frac{1}{6} \frac{10}{2} \sin 2t - \frac{1}{0,2} \frac{0,5t^2}{2} = -0,833 \sin 2t - 1,25t^2 \text{ (mV)}$$



VI. Applications

VI.2. Differentiator

- An **differentiator** is an op amp circuit whose output is proportional to the rate of change of the inputs signal.


- Applying KCL at node a

$$i_R = i_C \leftrightarrow -\frac{V_0}{R} = i_R = i_C = C \frac{dv_i}{dt}$$

$$v_0(t) = -RC \frac{dv_i}{dt}$$

- Note that:

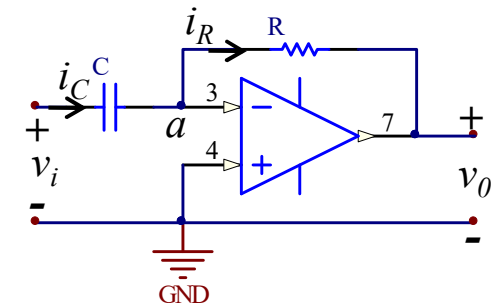- ❖ Differentiator circuits are **electronically unstable** because any electrical noise within the circuit is exaggerated by the differentiator.
- ❖ Differentiator circuit is not as useful and popular as the integrator.



VI. Applications

VI.2. Differentiator

Ex 6.10: Find the output voltage with the given input. Take $v_o = 0$ at $t = 0$.

- This is a differentiator with: $RC = 5 \cdot 10^3 \cdot 0,2 \cdot 10^{-6} = 10^{-3}$
- For $0 < t < 4\text{ms}$ or $4 < t < 8\text{ms}$, the input voltage is:

$$v_i = \begin{cases} 2t & 0 < t < 2\text{ms}, 4 < t < 6\text{ms} \\ 8 - 2t & 2 < t < 4\text{ms}, 6 < t < 8\text{ms} \end{cases}$$

$$\rightarrow v_o = -RC \frac{dv_i}{dt} = \begin{cases} -2\text{mV} & 0 < t < 2\text{ms}, 4 < t < 6\text{ms} \\ 2\text{mV} & 2 < t < 4\text{ms}, 6 < t < 8\text{ms} \end{cases}$$

