



FUNDAMENTALS OF ELECTRIC CIRCUITS

Part 1: DC CIRCUITS



Chapter 1: Basic concepts

I. Introduction.

II. Systems of units.

III. Charge and current.

IV. Voltage.

V. Power and Energy.

VI. Circuit elements.



Chapter 1: Basic concepts




I. Introduction.

- **Electric circuit theory** and **electromagnetic theory** are the two fundamental theories upon which all branches of electrical engineering are built, such as:
 - ❖ Power
 - ❖ Electric machines
 - ❖ Control
 - ❖ Electronics
 - ❖ Communications
 - ❖ Instrumentation
 - ❖ etc.
- The basic electric engineering theory course is:
 - ❖ The most important course for an electrical engineering student.
 - ❖ Excellent starting point for a beginning student in electrical engineering education.
 - ❖ Valuable to students specializing in other branches of the physical sciences.
- An **electric circuit** is an **interconnection** of **electrical elements**.

Ex1: A simple electric circuit consists of 4 basic components:

- ❖ A battery.
- ❖ A contact.
- ❖ A lamp.
- ❖ Connecting wires.

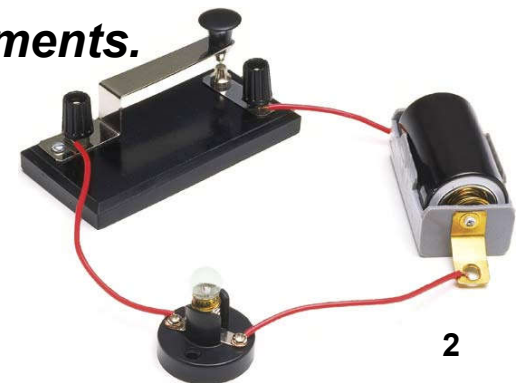



Chapter 1: Basic concepts



I. Introduction.

- **Electric circuit** are used in many electrical systems to accomplish different task.
- Objective in this course:
 - ❖ Not the study of various uses and applications of circuits.
 - ❖ The **analysis of the circuits**:
 - ☐ How does it respond to a give input ?
 - ☐ How do the interconnected elements and devices in the circuit interact?
- Study commence by defining some basic concepts:
 - ❖ Charge
 - ❖ Current
 - ❖ Voltage
 - ❖ Circuit element.
 - ❖ Power
 - ❖ Energy



Chapter 1: Basic concepts



II. Systems of units.

- An international measurement language is the International System of Unit (**SI**), adopt by the General Conference on Weight and Measures in 1960.
- In SI, there are **six principal units**:

- ❖ From which the units of all other physical quantities can be derived.
- ❖ Use prefixes base on the power of 10 to relate larger and smaller unit to the basic unit.

Quantity	Basic unit	Symbol
Length	Meter	m
Mass	Kilogram	Kg
Time	Second	s
Electric current	Ampere	A
Thermodynamic temperature	Kelvin	K
Luminous intensity	Candela	cd



Chapter 1: Basic concepts




III. Charge and current.

- The concept of electric charge is the underlying principle for explaining all electrical phenomena.
- **Charge** is an electrical property of the atomic particles of which matter consists, measured in coulombs (C)
- In atom physic, each atom consists of electrons, protons and neutrons:
 - ❖ Electron charge e : $-1.602 \times 10^{-19} \text{ C}$
 - ❖ Proton charge: $1.602 \times 10^{-19} \text{ C}$
- Notes:
 - ❖ $1\text{C} = 6.24 \times 10^{18}$ electrons $\rightarrow \text{pC}, \text{nC}, \mu\text{C}$
 - ❖ Only charges occuring in nature are integral multiples of the electronic charge $e = -1.602 \times 10^{-19} \text{ C}$.
 - ❖ Law of conservation of charge: Charge can neither be created nor destroyed, only transferred.

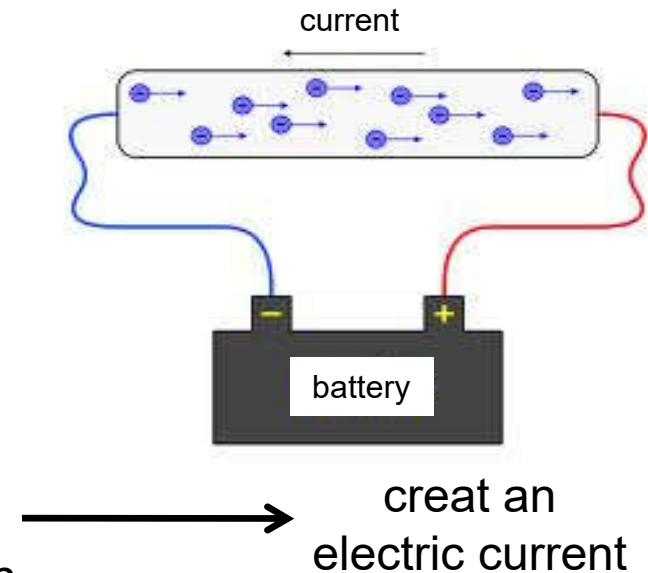III. Charge and current.





- Electric charge is mobile:
 - ❖ Can be transferred from one place to another
 - ❖ Can be converted to another form of energy.
- When a conducting wire is connected to a battery:
 - ❖ Positive charges move in one direction
 - ❖ Negative charges move in the opposite direction
- It is conventional to take the current flow as the movement of positive charge, opposite to the flow of negative charges (the current in metallic conductors is due to negatively charged electrons).
- **Electric current** is the time rate of change of charge, measured in amperes (A)



$$i = \frac{dq}{dt} ; [A] = \frac{[C]}{[s]}$$

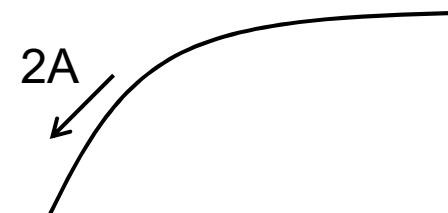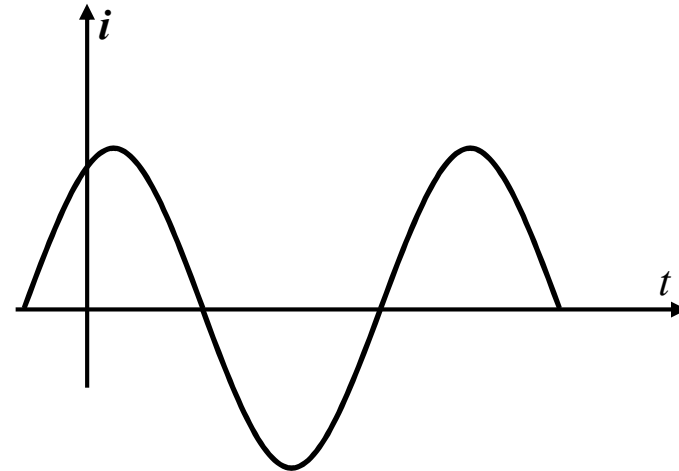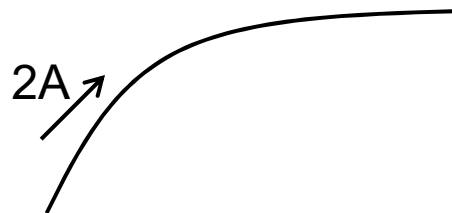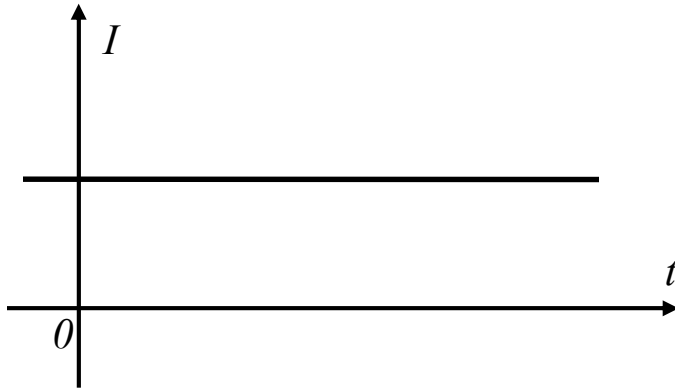III. Charge and current.

- There are two common types of current:
 - ❖ A **direct current** (DC) is a current that remains constant with time (I).
 - ❖ An **alternating current** (AC) is a current that varies sinusoidally with time (i).



a current of 2A may be represented
positively or ***negatively***



Chapter 1: Basic concepts




IV. Voltage.

- In order to move the electron in a conductor in a particular direction requires some work or energy transfer (*external electromotive force, emf*, as known as *voltage* or *potential difference*).
- **Voltage** (or potential difference) is the energy required to move a unit charge through an element, measured in volts (V).

$$v_{ab} = \frac{dw}{dq} \quad ; \quad [V] = \frac{[J]}{[C]} = \frac{[Nm]}{[C]}$$

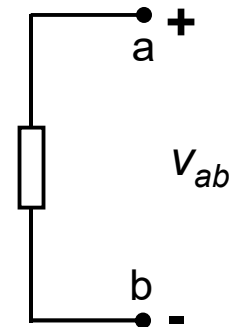- The v_{ab} can be interpreted in two ways:
 - ❖ Point a is at a potential of v_{ab} volts higher than point b .
 - ❖ The potential at point a with respect to point b is v_{ab} .



$$\rightarrow V_{ab} = -V_{ba}$$

- There are two common types of voltage:
 - ❖ DC voltage: produced by a battery, represented by V
 - ❖ AC voltage: produced by an electric generator, represented by V




Chapter 1: Basic concepts

V. Power and energy.


- Although current and voltage are the two basic variables in an electric circuit, they are not sufficient by themselves.
 - In fact:
 - ❖ Need to know how much **power** an electric device can handle ?
 - ❖ The EVN's bills are paid for the electric energy consumed over a certain period of time.
- **power** and **energy** calculations are important in circuit analysis.
- **Power** is the time rate of expending or absorbing energy, measured in watts (W)

$$p = \frac{dw}{dt} = \frac{dw}{dq} \cdot \frac{dq}{dt} = vi$$

p: the instantaneous power

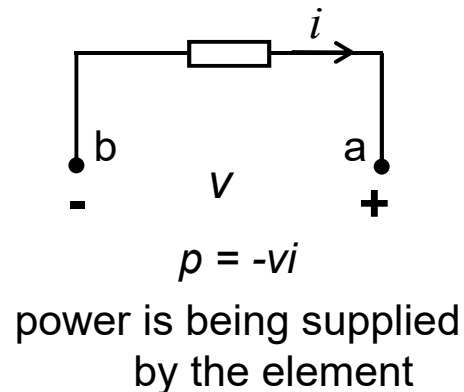

Passive sign convention is satisfied when the current enters through the positive terminal of an element, and $p = vi$. If the current enters through the negative terminal, $p = -vi$

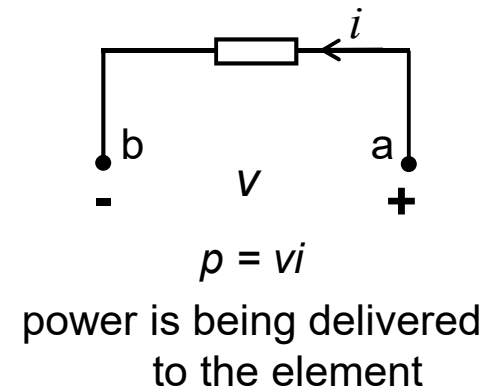



Chapter 1: Basic concepts



V. Power and energy.

- *Law of conservation of energy:*

$$\sum p = 0$$

- *Energy* is the capacity to do work, measured in Joules (J)

$$\omega = \int_{t_0}^t p dt = \int_{t_0}^t v i dt$$

- The electric power utility companies measure energy in Watt-hours (Wh)

$$1 \text{ Wh} = 3,600 \text{ J}$$



Chapter 1: Basic concepts




VI. Circuit elements.


- An element is the basic building block of a circuit.
- An electric circuit is simply an interconnection of the elements.
- Circuit analysis is the process of determining voltages across (or the currents through) the element of the circuit.
- Types of circuit elements:
 - ❖ Passive elements: Not be able to generate energy.
Ex. : Resistors, capacitors, inductors, ...
 - ❖ Active elements: To be able to generate energy.
Ex. : Generators, batteries, operational amplifiers, voltage sources, current sources ...
- Two kinds of sources:
 - ❖ Independent sources.
 - ❖ Dependent sources.

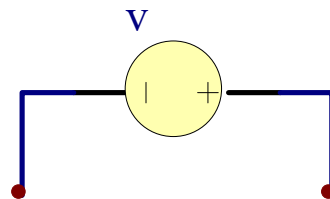VI. Circuit elements.

- An ideal independent source is an active element that provides a specified voltage or current that is completely independent of other circuit variables.
- ❖ An ideal independent voltage source delivers to the circuit whatever current is necessary to maintain its terminal voltage.




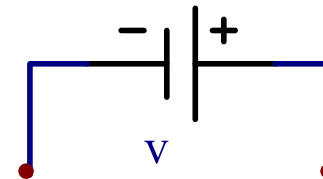DC or time varying independent voltage source



DC independent voltage source

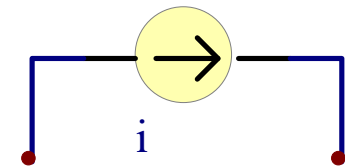- ❖ An ideal independent current source is an active element that provides a specified current completely independent of the voltage across the source (*the arrow indicates the direction of current i*)



Independent current source




Chapter 1: Basic concepts




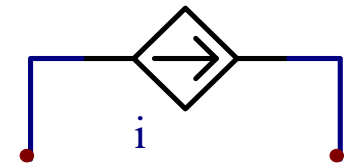VI. Circuit elements.

- An ideal dependent (or controlled) source is an active element in which the source quantity is controlled by another voltage or current.
- There are 4 possible types of dependent sources:
 - ❖ A voltage-controlled voltage source (VCVS)
 - ❖ A current-controlled voltage source (CCVS)
 - ❖ A voltage-controlled current source (VCCS)
 - ❖ A current-controlled current source (CCCS)
- Dependent sources are useful in modeling elements:
 - Transistors.
 - Operational amplifier.
 - Integrated circuits.
 - ...



Dependent current source

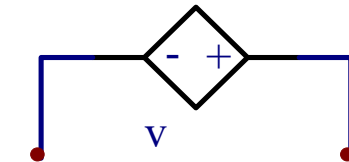

Dependent voltage source