



FUNDAMENTALS OF ELECTRIC CIRCUITS

Part 1: DC CIRCUITS



Chapter 5: Operational amplifiers

I. Introduction.

II. Operational amplifier.

III. Ideal Op Amp.

VI. Inverting – Non-inverting amplifier.

V. Summing amplifier.

VI. Difference amplifier.

VII. Cascaded Op Amp circuits

VIII. Applications



Chapter 5: Operational amplifiers



I. Introduction

- The operational amplifier (*op amp*) is an electronic unit that behaves like a voltage-controlled voltage source.
- An op amp can: sum signals, amplify, integrate, or differentiate a signal.
- Nowadays, op amp are popular in practical circuit designs because they are versatile, inexpensive, easy to use ...
- This chapter presents the ideal op amp first and consider the non-ideal op amp later.
- Using nodal analysis as a tool, we consider ideal op amp circuits such as the inverter, voltage follower, summer and difference amplifier.

II. Operational amplifiers

➤ An **op amp** is an active circuit element designed to perform mathematical operations of addition, subtraction, multiplication, division, differentiation, and integration.




An op amp package


➤ The op amp is an electronic device consisting of a complex arrangement of resistor, transistor, capacitor, and diodes → treat them as a circuit building block, study what takes place at its terminals.

➤ There are several important terminal in an op amp:

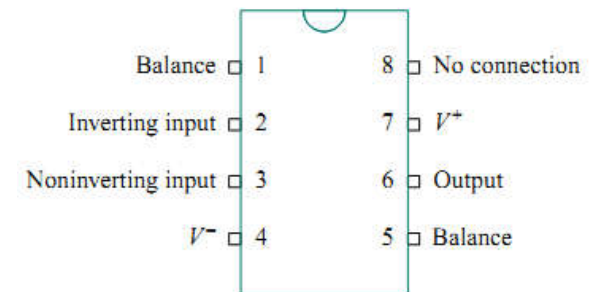- ❖ The inverting input: pin 2 (-)
- ❖ The non-inverting input: pin 3 (+)
- ❖ The output: pin 6
- ❖ The positive power supply V^+ : pin 7
- ❖ The negative power supply V^- : pin 4




Dual in-line package of op amp

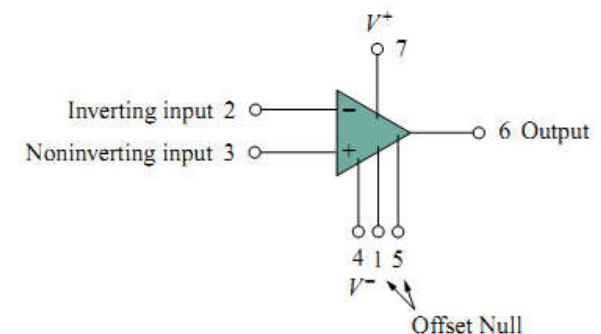

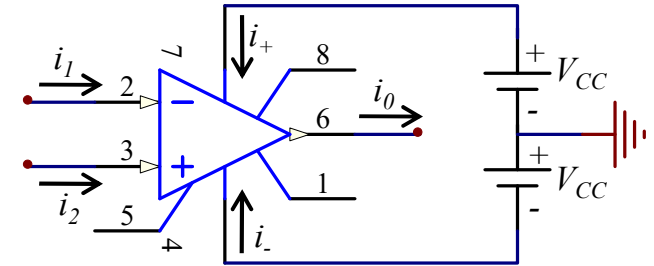II. Operational amplifiers


- An op amp must be powered by a voltage supply which are often ignored in op amp circuit diagram, but the power supply currents must not be overlook.



$$i_0 = i_1 + i_2 + i_+ + i_-$$

- The equivalent circuit model of a non-ideal op amp:

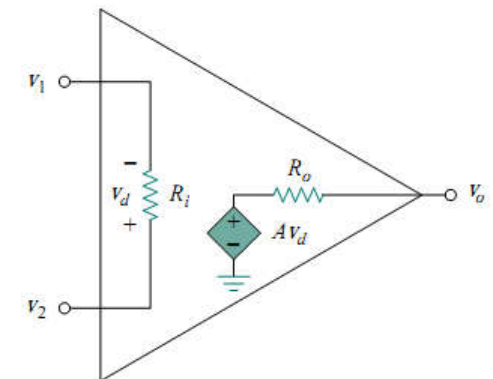- ❖ The output section: Voltage-controlled source $A.v_d$ in series with output resistance R_o .
- ❖ R_i : Thevenin equivalent resistance seen at input terminals
- ❖ R_o : Thevenin equivalent resistance seen at the output



The equivalent circuit of the non-ideal op amp

- ❖ Voltage output: $v_0 = A.v_d = A.(v_2 - v_1)$ A : Open-loop voltage gain (gain of the op amp without any external feedback from output to input).




Chapter 5: Operational amplifiers



II. Operational amplifiers

➤ Table shows typical parameter values of op am:

Parameter	Typical range	Ideal value
Open-loop gain, A	$10^5 - 10^8$	∞
Input resistance, R_i	$10^6 - 10^{13} \Omega$	$\infty \Omega$
Output resistance, R_o	$10 - 100 \Omega$	0Ω
Supply voltage, V_{cc}	$5 - 24 \text{ V}$	

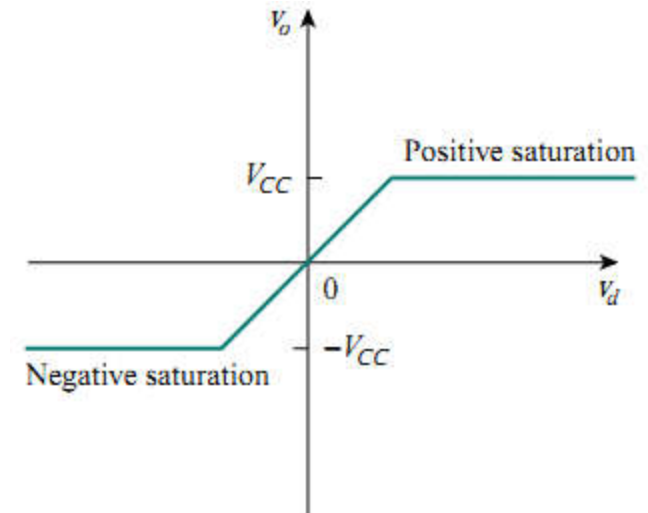

➤ Op amp can operate in three modes, depending on the v_d

- ❖ Positive saturation: $v_o = V_{cc}$
- ❖ **Linear region:** $-V_{cc} \leq v_o = A \cdot v_d \leq V_{cc}$
- ❖ Negative saturation: $v_o = -V_{cc}$

Chapter 5: Operational amplifiers

II. Operational amplifiers

Ex 5.1: Find the closed-loop gain V_0 / V_s . Determine current i when $V_s = 2V$

➤ Using the op amp model, we obtain the equivalent circuit → applying the nodal analysis gives:

❖ At node 1: $\frac{V_s - V_1}{R_1} = \frac{V_1}{R_1} + \frac{V_1 - V_0}{R_2} \rightarrow V_1 = \frac{2V_s + V_0}{3}$

❖ At node 0:



$$\begin{cases} \frac{V_1 - V_0}{R_2} = \frac{V_0 - AV_d}{R_0} \\ V_d = -V_1 \end{cases} \rightarrow \begin{cases} V_1 - V_0 = 400(V_0 + 2.10^6 \cdot V_1) \\ \frac{V_0}{V_s} \approx -1.9999699 \end{cases}$$

❖ When $v_s = 2V$:

$$V_1 = \frac{2V_s + V_0}{3} = 20,067 \mu V$$

$$\rightarrow i = \frac{V_1 - V_0}{R_2} \approx 0,2mA$$

741 parameter	Value
Open-loop gain, A	2.10^5
Input resistance, R_i	$2 \text{ M } \Omega$
Output resistance, R_0	50Ω

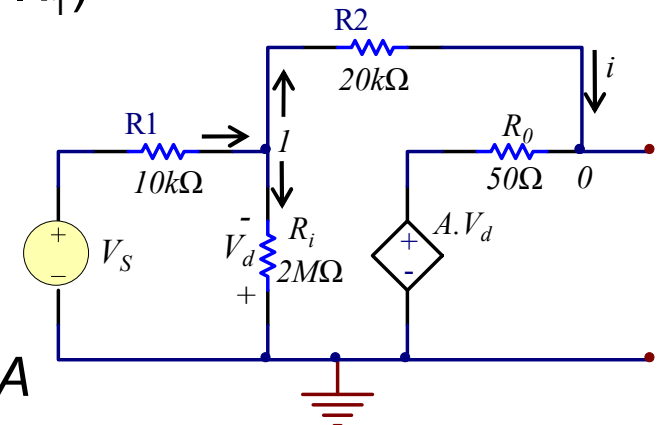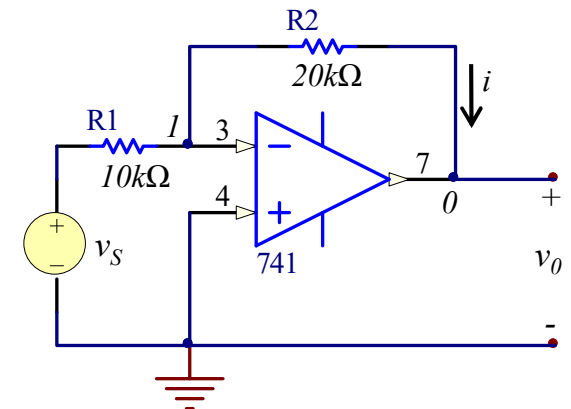



Chapter 5: Operational amplifiers



III. Ideal op amp

➤ An *ideal op amp* is an amplifier with infinite open-loop gain ($A = \infty$), infinite input resistance ($R_i = \infty$), and zero output resistance ($R_o = 0$).


➤ Important characteristics of an ideal op amp:

❖ The currents into both input terminal are zero

$$i_1 = 0 \quad ; \quad i_2 = 0$$

❖ The voltage across the input terminals is small

$$V_d = V_2 - V_1 \simeq 0 \quad ; \quad V_1 = V_2$$

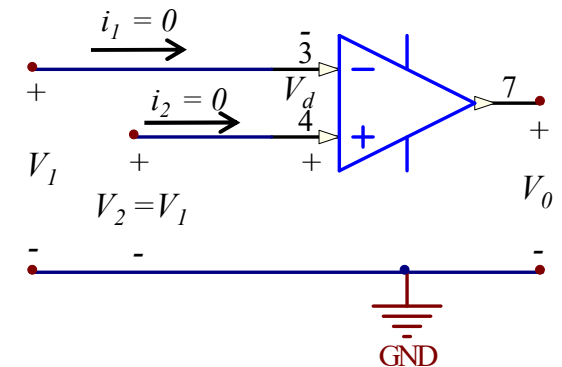



Chapter 5: Operational amplifiers




III. Ideal op amp

Ex 5.2: Considering 741 op amp as an ideal op amp. Calculate the V_0/V_s . Find i_0 when $v_s = 1V$

- As an ideal op amp, we have: $V_2 = V_s$
- Since $i_1 = 0 \rightarrow R_1$ and R_2 are in series
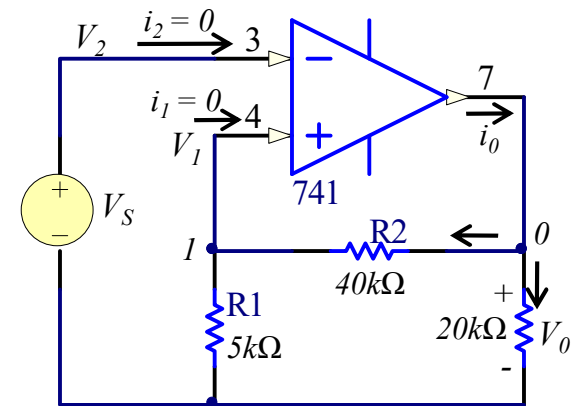
$$V_1 = \frac{V_0}{R_1 + R_2} R_1 = \frac{V_0}{9}$$



- From these equations, we have: $V_s = \frac{V_0}{9} \rightarrow \frac{V_0}{V_s} = 9$
- Applying KCL at node 0 gives: $i_0 = \frac{V_0}{R_1 + R_2} + \frac{V_0}{20 \cdot 10^3} \xrightarrow{V_s=1} \begin{cases} V_0 = 9V \\ i_0 = 0,65mA \end{cases}$

IV. Inverting – Non-inverting amplifier

IV.1. Inverting amplifier

- Applying KCL at node 1:

$$i_1 = i_2 \rightarrow \frac{V_i - V_1}{R_1} = \frac{V_1 - V_0}{R_2} \rightarrow \frac{V_i}{R_1} = -\frac{V_0}{R_2} \rightarrow V_0 = -\frac{R_2}{R_1} V_i$$



- Ideal op amp: $V_1 = V_2 = 0$

- **Notes:**

- ❖ The voltage gain $A_v = -\frac{R_2}{R_1}$ depends only on the external element connected to the op amp.

- ❖ A key feature of the inverting amplifier is that both the input signal and the feedback are applied at the inverting terminal of the op amp.

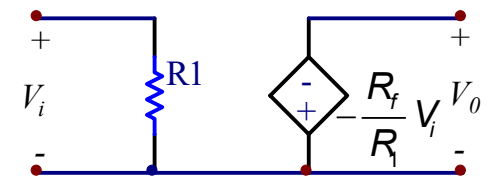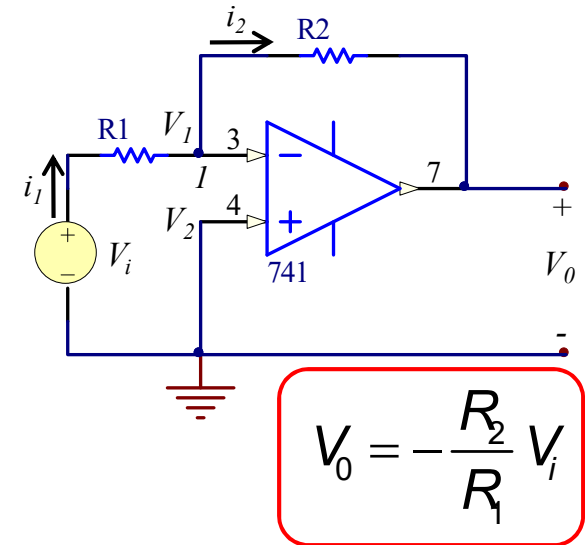- ❖ The inverting amplifier is used in a current to voltage converter.



IV. Inverting – Non-inverting amplifier

IV.1. Inverting amplifier

Ex 5.3: Calculate the output voltage v_o and the current through R_1 and R_2 if $v_i = 0,5V$

- This is an inverting amplifier


$$V_o = -\frac{R_2}{R_1} \cdot V_i = -\frac{25}{10} \cdot 0,5 = -1,25V$$

- Calculating the current through the R_1

$$i_{R1} = \frac{V_i - 0}{R_1} = \frac{0,5}{10 \cdot 10^3} = 50 \mu A$$

- Calculating the current through the R_2

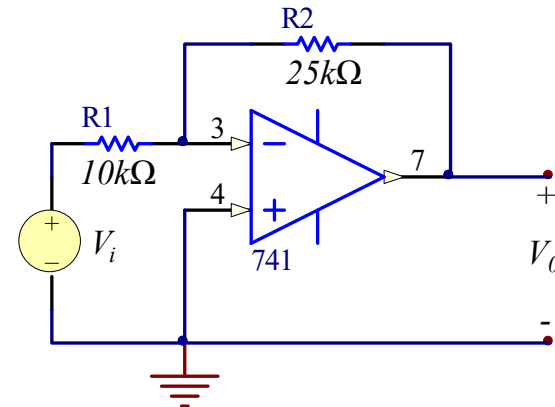
$$i_{R2} = \frac{V_o - 0}{R_2} = \frac{-1,25}{25 \cdot 10^3} = -50 \mu A$$



IV. Inverting – Non-inverting amplifier

IV.1. Inverting amplifier

Ex 5.4: Calculate the output voltage V_o

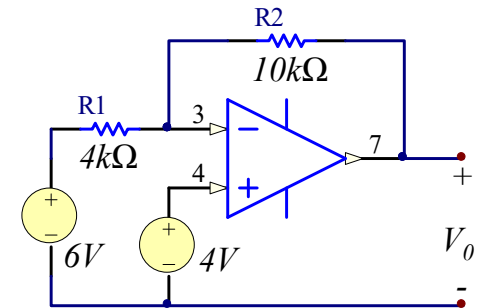

➤ Applying KCL at node 3:

$$\frac{6 - V_3}{R_1} = \frac{V_3 - V_o}{R_2} \rightarrow \frac{6 - V_3}{4} = \frac{V_3 - V_o}{10}$$

➤ Because of an ideal op amp, we have $V_3 = V_4 = 4V$

$$\rightarrow \frac{6 - 4}{4} = \frac{4 - V_o}{10} \rightarrow V_o = -1V$$


IV. Inverting – Non-inverting amplifier

IV.2. Non-inverting amplifier

➤ A *non-inverting amplifier* is an op amp circuit designed to provide a positive voltage gain:

❖ Input voltage V_i is applied directly at the non-inverting input terminal.

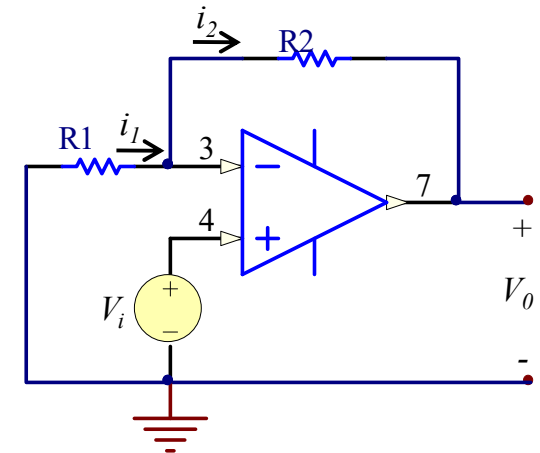❖ R_1 is connected between the ground and the inverting terminal.



$$i_1 = i_2 \rightarrow \frac{0 - V_3}{R_1} = \frac{V_3 - V_0}{R_2} \rightarrow \frac{-V_i}{R_1} = \frac{V_i - V_0}{R_2} \rightarrow V_0 = \left(1 + \frac{R_2}{R_1}\right) V_i$$


$V_3 = V_4 = V_i$

IV. Inverting – Non-inverting amplifier

IV.2. Non-inverting amplifier


➤ Note:

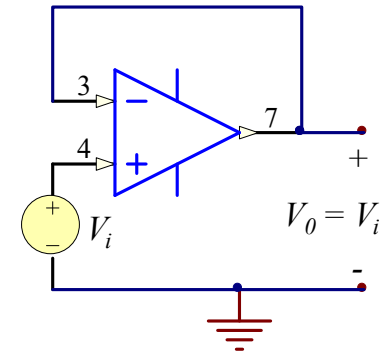- ❖ If $R_2 = 0$ or $R_1 = \infty \rightarrow$ the voltage gain becomes 1
- ❖ In this case, the circuit is call a *voltage follower* (or *unity gain amplifier*)



➤ Characteristic of voltage follower:

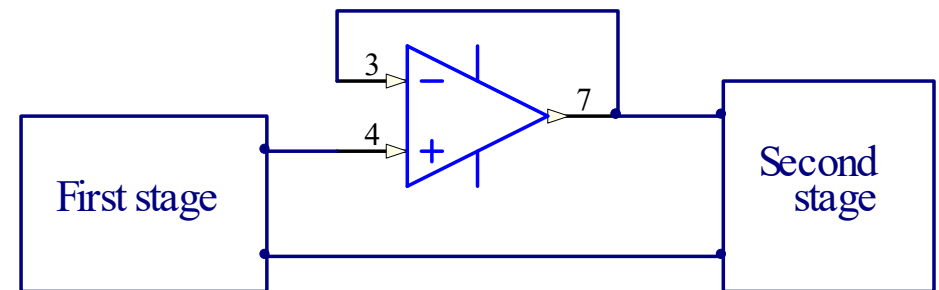- ❖ A very high input impedance
- ❖ Useful as an intermediate - stage (or *buffer*) amplifier to isolate one circuit from another.
- ❖ Minimize interaction between the two stages and eliminate inter-stage loading.



Voltage follower used to isolate two cascaded stages of a circuit

IV. Inverting – Non-inverting amplifier

IV.2. Non-inverting amplifier

Ex 5.5: Calculate the output voltage V_O


- Using superposition lets: $V_O = V_{O1} + V_{O2}$
 - ❖ V_{O1} is due to the 6V voltage source
 - ❖ V_{O2} is due to the 4V voltage source
- Calculate V_{O1} : Set the 4V voltage source to zero, the circuit becomes an inverter.

$$V_{O1} = -\frac{R_2}{R_1} 6 = -\frac{10}{4} 6 = -15V$$

- Calculate V_{O2} : Set the 6V voltage source to zero, the circuit becomes an non-inverter amplifier

$$V_{O2} = \left(1 + \frac{R_2}{R_1}\right) 4 = \left(1 + \frac{10}{4}\right) 4 = 14V$$

$$\rightarrow V_O = V_{O1} + V_{O2} = -1V$$

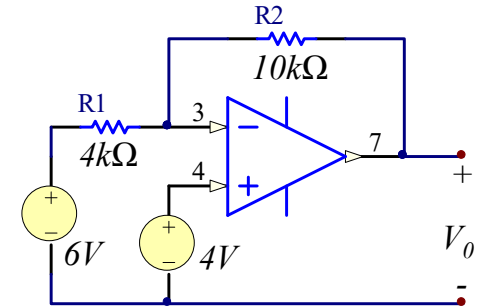




Chapter 5: Operational amplifiers



IV. Inverting – Non-inverting amplifier

IV.2. Non-inverting amplifier

Ex 5.6: Calculate the output voltage V_o

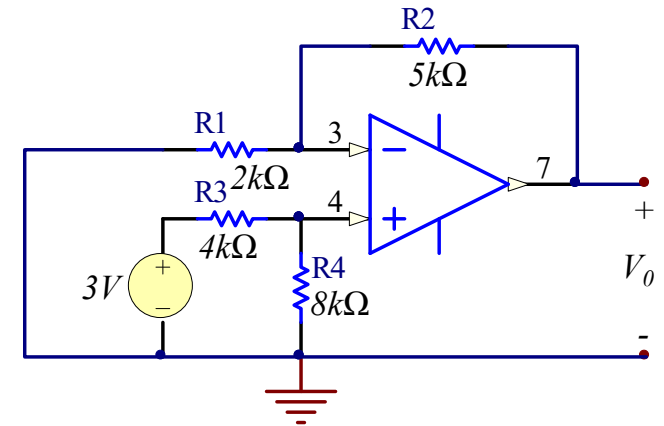

V. Summing amplifier


- A **summing amplifier** is an op amp circuit that combines several inputs and produces an output that is the weighted sum of the inputs.
- The summing amplifier is a variation of the inverting amplifier

- Applying KCL at node a gives:

$$i = i_1 + i_2 + i_3 \rightarrow \frac{V_a - V_O}{R_f} = \frac{V_1 - V_a}{R_1} + \frac{V_2 - V_a}{R_2} + \frac{V_3 - V_a}{R_3}$$

- Note that: $V_a = 0$ (ideal op amp)
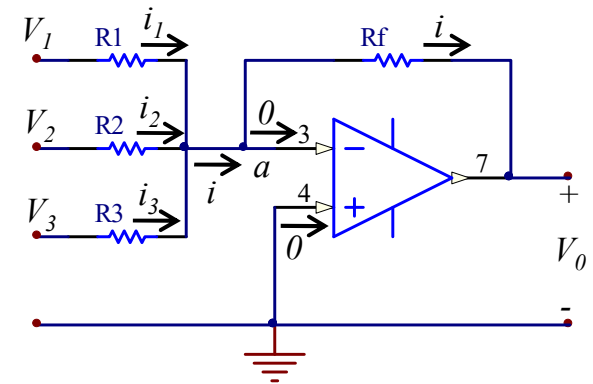
$$\rightarrow V_O = - \left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right)$$



V. Summing amplifier


Ex 5.7: Calculate V_o and i_o in the op amp circuit

- This is a summer with two inputs
- Applying the equation of summing amplifier gives:

$$V_o = -\left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2\right) = -\left(\frac{10}{5} \cdot 2 + \frac{10}{2,5}\right) = -8V$$

- The current i_o is the sum of the currents through the 10-k Ω and 2-k Ω resistor
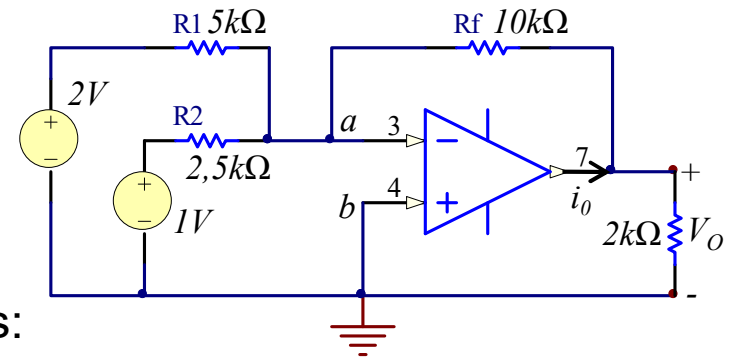
$$i_o = \frac{V_o - V_a}{10} + \frac{V_o - V_b}{2} = \frac{-8}{10} + \frac{-8}{2} = -4,8mA$$



VI. Difference amplifier


- A **difference (differential) amplifier** is a device that amplifies the difference between two inputs but rejects any signals common to the two inputs.

- Applying KCL at node a gives:

$$\frac{V_1 - V_a}{R_1} = \frac{V_a - V_0}{R_2} \rightarrow V_0 = \left(\frac{R_2}{R_1} + 1 \right) V_a - \frac{R_2}{R_1} V_1$$

- Applying KCL at node b gives:
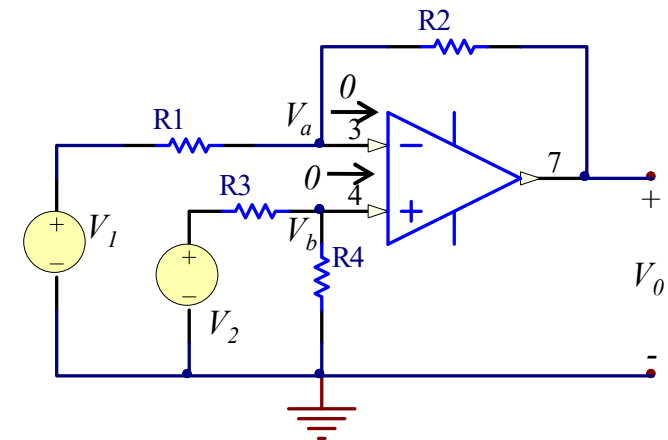
$$\frac{V_2 - V_b}{R_3} = \frac{V_b}{R_4} \rightarrow V_b = \frac{R_4}{R_3 + R_4} V_2$$



- Note that: $V_a = V_b$ (ideal op amp):

$$V_0 = \left(\frac{R_2}{R_1} + 1 \right) \frac{R_3}{R_3 + R_4} V_2 - \frac{R_2}{R_1} V_1 \rightarrow V_0 = \frac{R_2}{R_1} \frac{\left(1 + \frac{R_1}{R_2} \right)}{\left(1 + \frac{R_3}{R_4} \right)} V_2 - \frac{R_2}{R_1} V_1$$


VI. Difference amplifier

- Since a difference amplifier must reject a signal common to the two inputs

$$V_0 = 0 \text{ when } V_1 = V_2$$

- This property exists when: $\frac{R_1}{R_2} = \frac{R_3}{R_4}$
- The op amp circuit is a difference amplifier
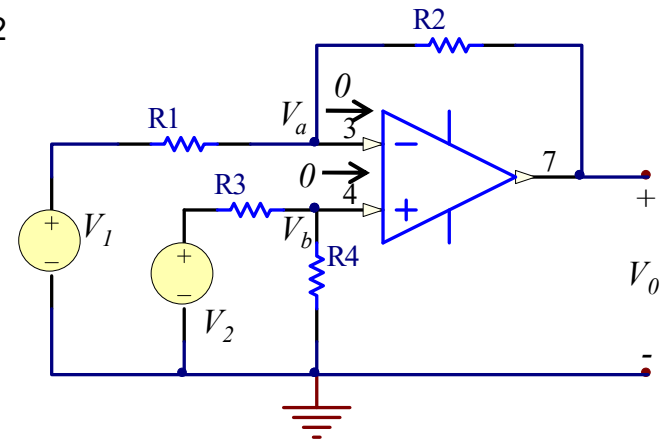
$$\rightarrow V_0 = \frac{R_2}{R_1} (V_2 - V_1)$$



- If $R_2 = R_1$, and $R_3 = R_4$, the difference amplifier becomes a subtractor $V_0 = V_2 - V_1$
- Remarks:
 - ❖ The difference amplifier is also known as the subtractor
 - ❖ The difference amplifier are used in various applications (*instrumentation amplifier*)



Chapter 5: Operational amplifiers



VI. Difference amplifier

Ex 5.8: Design an op amp circuit with inputs V_1 and V_2 such that $V_0 = -5V_1 + 3V_2$

➤ **Solution 1:** Using only one op amp

❖ Rewrite: $V_0 = -5V_1 + 3V_2 = 5\left(\frac{3}{5}V_2 - V_1\right)$

❖ Applying the difference amplifier equation: $V_0 = \frac{R_2}{R_1}(V_2 - V_1) \rightarrow \frac{R_2}{R_1} = 5$

❖ In the other word: $V_0 = \frac{R_2}{R_1} \frac{\left(1 + \frac{R_1}{R_2}\right)}{\left(1 + \frac{R_3}{R_4}\right)} V_2 - \frac{R_2}{R_1} V_1 = 5 \frac{\left(1 + \frac{1}{5}\right)}{\left(1 + \frac{R_3}{R_4}\right)} V_2 - 5V_1$

$$\rightarrow \frac{\left(1 + \frac{1}{5}\right)}{\left(1 + \frac{R_3}{R_4}\right)} = \frac{3}{5} \rightarrow 2 = 1 + \frac{R_3}{R_4} \rightarrow R_3 = R_4$$

❖ Choose:

$$R_1 = 10k\Omega ; R_2 = 50k\Omega$$

$$R_3 = R_4 = 20k\Omega$$

VI. Difference amplifier

Ex 5.8: Design an op amp circuit with inputs V_1 and V_2 such that $V_0 = -5V_1 + 3V_2$


➤ **Solution 2:** Using 02 op amp → inverting amplifier + 2-inputs inverting summer.

❖ For the summer: $V_0 = -V_a - 5V_1$

❖ For the inverter: $V_a = -3V_2$

❖ Combining 02 op amps: $V_0 = 3V_2 - 5V_1$

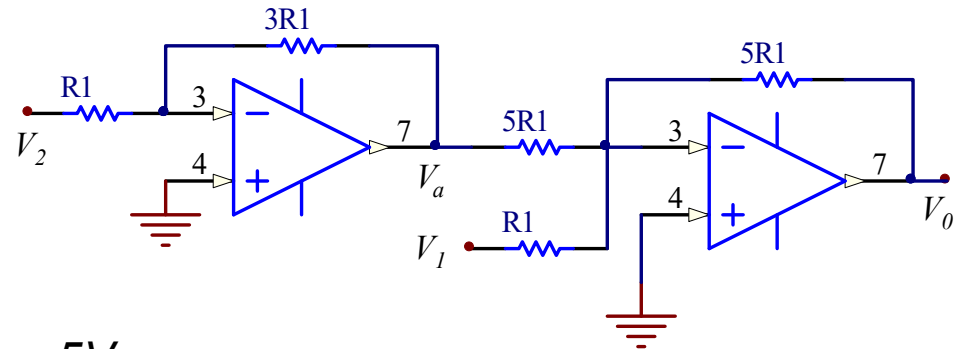❖ Selecte the resistor value: $R_1 = 10k\Omega$;



VI. Difference amplifier


Ex 5.9: Find the relationship between V_o and 02 - inputs of an instrumentation amplifier.

- ❖ There are not current into A_1 , and A_2 , the current i flows through the 3 resistors

$$V_{01} - V_{02} = i(2R_3 + R_4)$$

- ❖ But: $i = \frac{V_a - V_b}{R_4}$; $V_a = V_1$; $V_b = V_2$

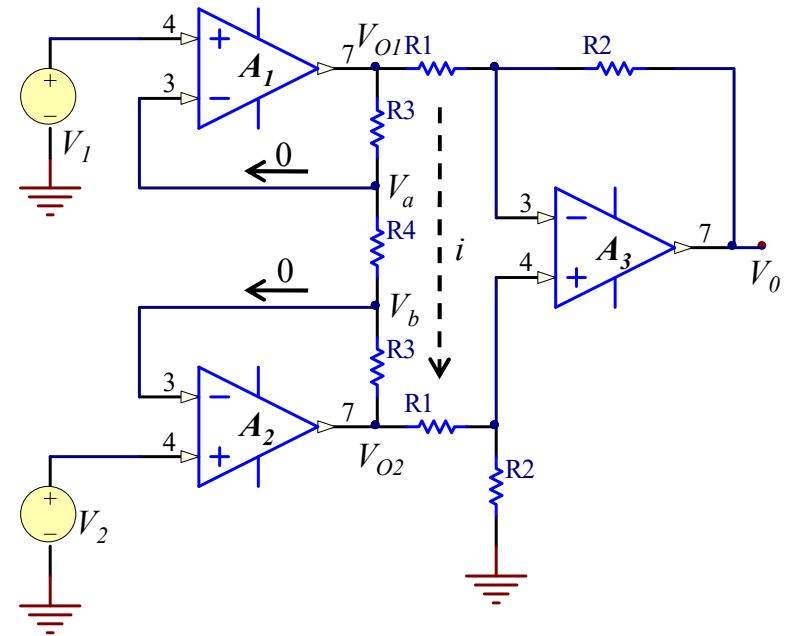- ❖ Therefore: $i = \frac{V_1 - V_2}{R_4}$



- ❖ The relationship between inputs and output of an instrumentation amplifier:

$$V_o = \frac{R_2}{R_1} \left(1 + \frac{2R_3}{R_4} \right) (V_2 - V_1)$$




Chapter 5: Operational amplifiers



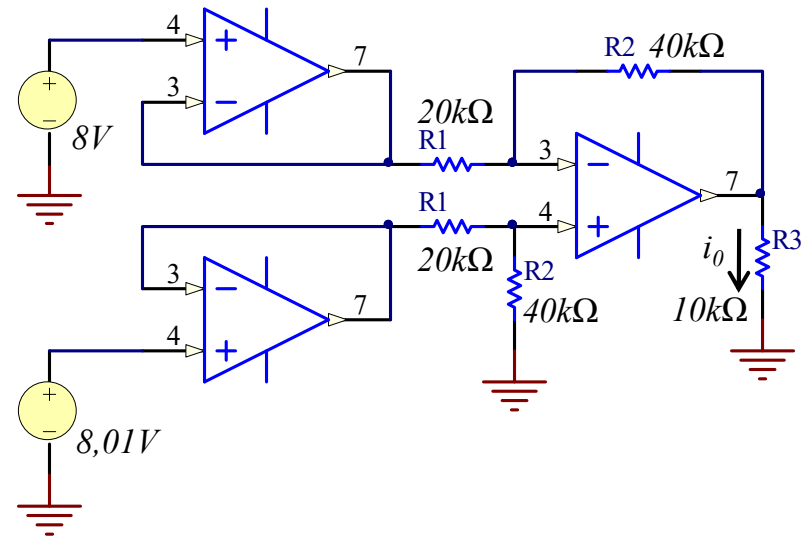
VI. Difference amplifier

Ex 5.10: Obtain i_0 in the instrumentation amplifier circuit.



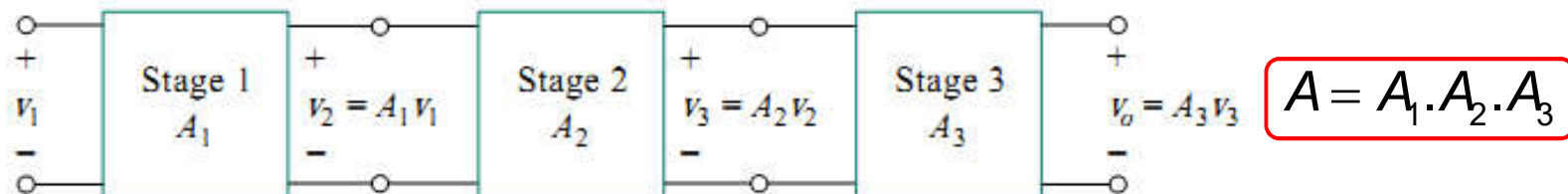VII. Cascaded op amp circuits

- A **cascade connection** is a head-to-tail arrangement of two or more op amp circuits such that the output of one is the input of the next.
- Characteristics:
 - ❖ Each op amp circuit in the string is called a **stage**.
 - ❖ Op amp circuits can be cascaded without changing their input-output relationships because:
 - ❑ Infinite input resistance.
 - ❑ Zero output resistance.
 - ❖ The original input signal is increased by the gain of the individual stage.



VII. Cascaded op amp circuits

Ex. 5.11: Find V_o and i_o in the circuit

- ❖ The circuit consists of two non-inverting amplifiers cascaded


□ At a point:

$$V_a = \left(1 + \frac{R_1}{R_2}\right) 20 = 100mV$$

□ At the output of the second op amp: $V_o = \left(1 + \frac{R_3}{R_4}\right) V_a = 350mV$


- ❖ The current i_o flows through the $10k\Omega$ resistor
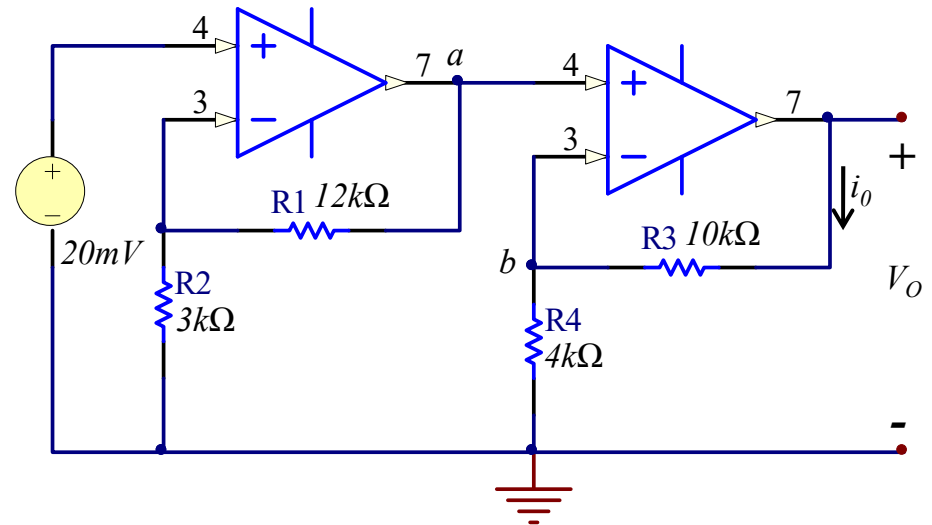
$$i_o = \frac{V_o - V_b}{R_3} \xrightarrow{V_b = V_a} i_o = \frac{(350 - 100) \cdot 10^{-3}}{10 \cdot 10^3} = 25\mu A$$



VII. Cascaded op amp circuits

Ex. 5.12: Find V_o

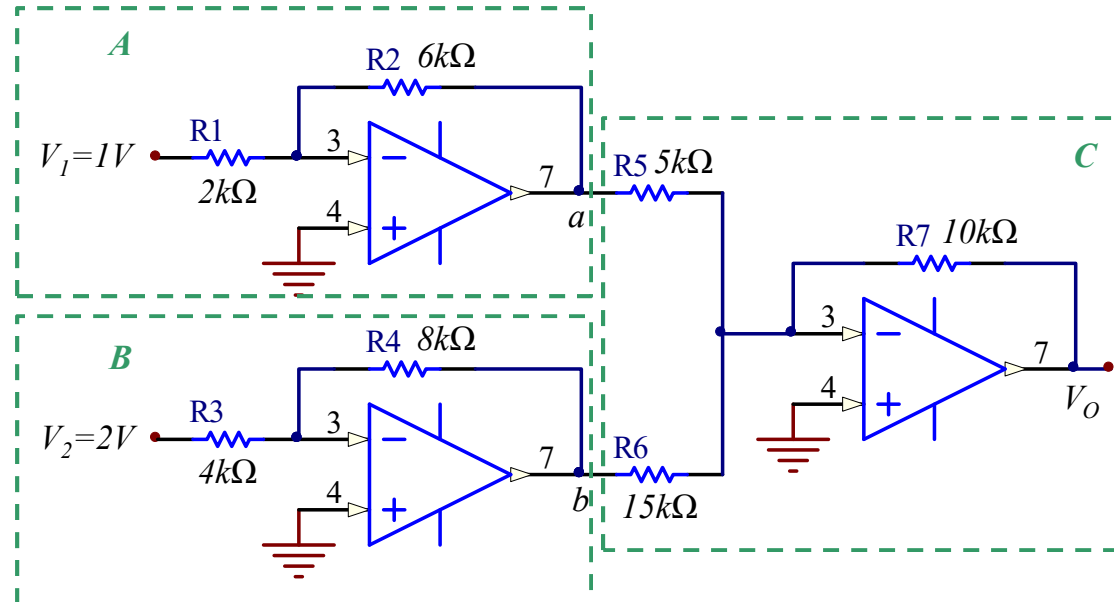

- ❖ The circuit consists of two inverters *A* and *B* and a summer *C*.

$$V_a = -\frac{R_2}{R_1} V_1 = -3V \qquad V_b = -\frac{R_4}{R_3} V_2 = -4V$$

- ❖ These become the inputs to the summer:

$$V_o = -\left(\frac{R_7}{R_5} V_a + \frac{R_7}{R_6} V_b\right) = -\left[2.(-3) + \frac{2}{3}(-4)\right] = 8.333V$$




Chapter 5: Operational amplifiers



VII. Cascaded op amp circuits

Ex. 5.13: Find V_O if $V_1 = 2V$, $V_2 = 1,5V$

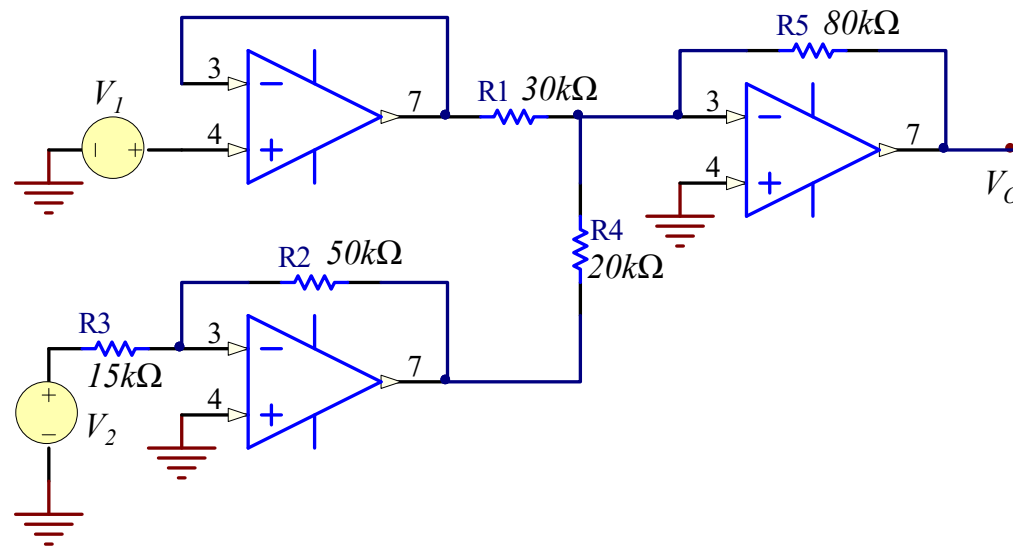



Chapter 5: Operational amplifiers




VIII. Applications

- Op amp has numerous practical applications:
 - ❖ Inverters, summers, integrators, differentiators, subtractors, logarithmic amplifiers
 - ❖ *Instrumentation amplifiers*, calibration circuits
 - ❖ *DAC*, voltage-to-current converters, current-to-voltage converters
 - ❖ Analog computers,
 - ❖ Filters, clippers, rectifier, regulators, level shifters
 - ❖ Comparators, gyrators, oscillators
 - ❖ ...

VIII.1. DAC – Digital-to-Analog Converter

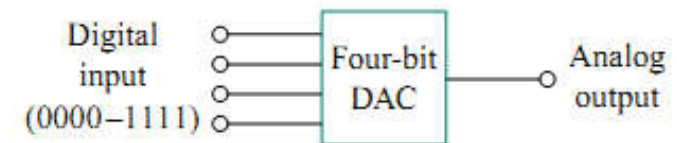
- The *digital-to-analog converter* (DAC) transforms digital signals into analog form.
- A DAC can be realized by using the binary weighted ladder:



A four-bit DAC

- ❖ The bits are weights according to the magnitude of their place value.
- ❖ Their weights decrease value of $R_f/R_n \rightarrow$ each lesser bit has half the weight of the next higher.
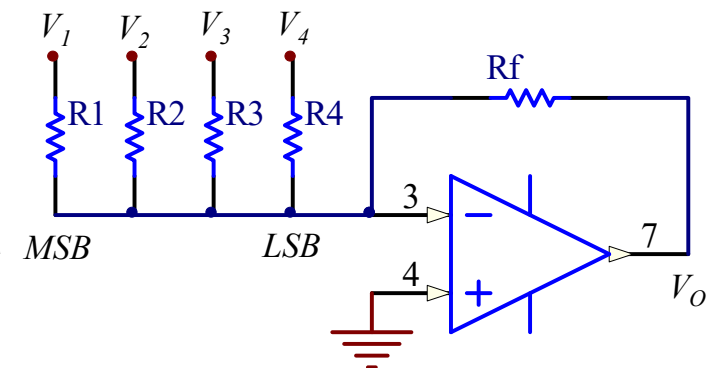
$$-V_O = \frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 + \frac{R_f}{R_4} V_4$$




Binary weighted ladder type

- ❖ V_1, \dots, V_4 can assume only two voltage levels (0, 1) (*binary code*) \rightarrow DAC provides a single output that is proportional to the inputs.

VIII.1. DAC – Digital-to-Analog Converter

Ex 5.14: Obtain the analog output for binary inputs [0000], [0001], [0010], ... [1111].

Inputs [B]	Value [D]	$-V_0$
0000	0	0
0001	1	0.125
0010	2	0.25
0011	3	0.375
0100	4	0.5
0101	5	0.625
0110	6	0.75
0111	7	0.875
1000	8	1.0
1001	9	1.125
...		
1111	15	1.875

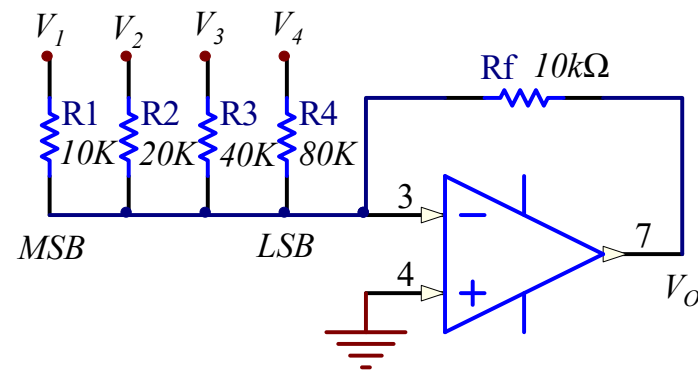

$$-V_0 = \frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 + \frac{R_f}{R_4} V_4$$

$$-V_0 = V_1 + 0,5V_2 + 0,25V_3 + 0,125V_4$$

- Each bit has a value of 0.125V → cannot represent a voltage between 1V → 1.125V (*DAC resolution*).

VIII.2. Instrumentation amplifier (IA)



- Typical applications of IAs include isolation amplifiers, thermocouple amplifiers, and data acquisition systems.

- From the Ex 5.9, we have:

$$V_0 = \left(1 + \frac{2R}{R_G} \right) (V_2 - V_1)$$


- Recall that:

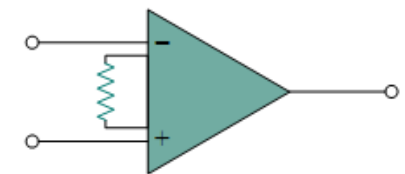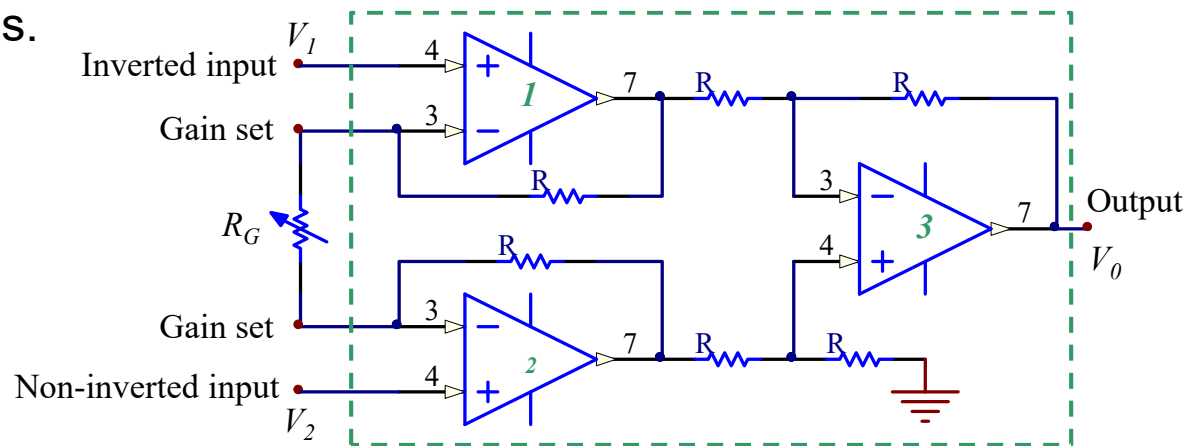- ❖ The IA amplifies small differential signal voltages superimposed on larger common-mode voltages.
- ❖ Since the common-mode voltages are equal, they cancel each other.



Schematic diagram

VIII.2. Instrumentation amplifier (IA)

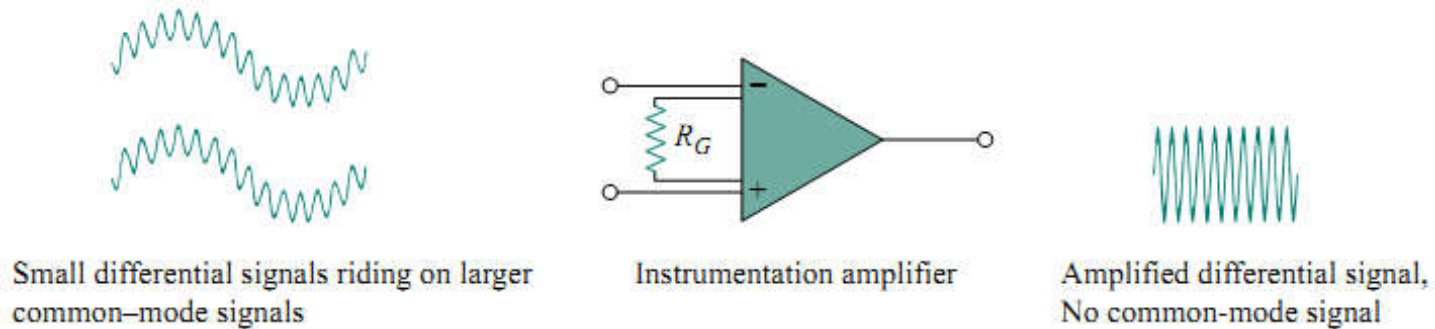

- The IAs have three major characteristics:
- ❖ The *voltage gain is adjusted* by one external resistor R_G
 - ❖ The *input impedance of both inputs is very high* and does *not vary* as the gain is adjusted.
 - ❖ The *output V_O depends on the difference* between the inputs V_1 and V_2 , not on the voltage common to them (common-mode voltage).

VIII.2. Instrumentation amplifier (IA)

Ex: A precision Instrumentation amplifier

Product highlight:


- ❖ Input noise is less than 4 nV/ $\sqrt{\text{Hz}}$ at 1 kHz.
- ❖ Pin programmable gains of 1, 100, 200, 500 and 1000 provided on the chip. Using a single external resistor for other gains.
- ❖ The offset voltage, offset voltage drift, gain accuracy and gain temperature coefficients are guaranteed for all pretrimmed gains.
- ❖ Provides totally independent input and output offset for high precision applications.
- ❖ A sense terminal is provided to enable the user to minimize the errors induced through long leads. A reference terminal is also provided to permit level shifting at the output.

Datasheet:

http://www.analog.com/static/imported-files/data_sheets/AD620.pdf

Fundamentals of Electric Circuits – Viet Son Nguyen - 2013

FUNCTIONAL BLOCK DIAGRAM

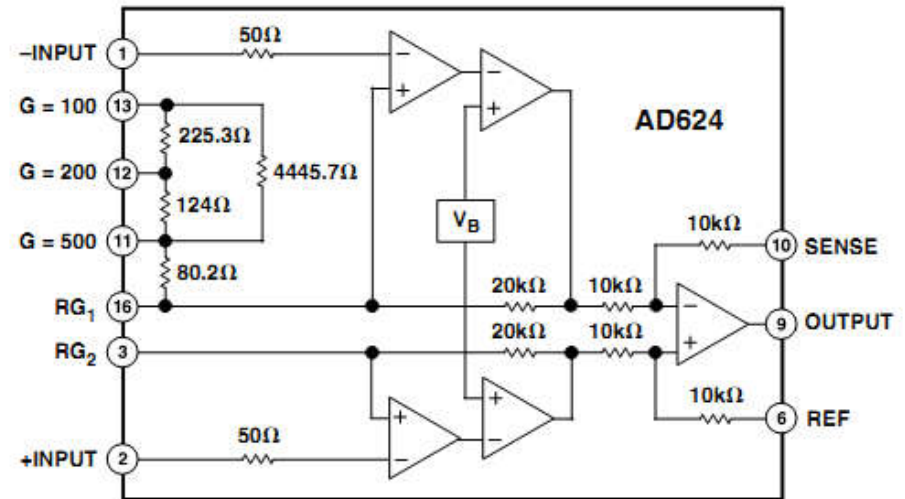


FEATURES

Low Noise: 0.2 μV p-p 0.1 Hz to 10 Hz
 Low Gain TC: 5 ppm max ($G = 1$)
 Low Nonlinearity: 0.001% max ($G = 1$ to 200)
 High CMRR: 130 dB min ($G = 500$ to 1000)
 Low Input Offset Voltage: 25 μV , max
 Low Input Offset Voltage Drift: 0.25 $\mu\text{V}/^\circ\text{C}$ max
 Gain Bandwidth Product: 25 MHz
 Pin Programmable Gains of 1, 100, 200, 500, 1000
 No External Components Required
 Internally Compensated

Price (100 - 499)	Price (1000)
\$4.82	\$4.09

VIII.2. Instrumentation amplifier (IA)

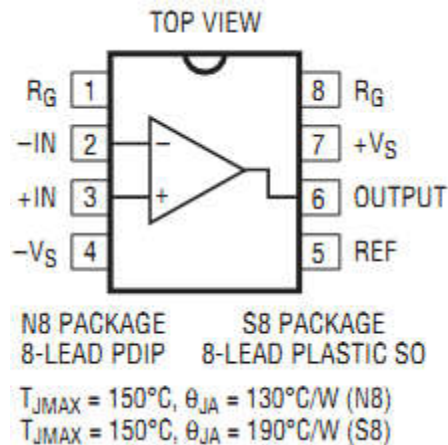Ex: LT167 – Single resistor gain, programmable, precision instrumentation amplifier



APPLICATIONS

- Bridge Amplifiers
- Strain Gauge Amplifiers
- Thermocouple Amplifiers
- Differential to Single-Ended Converters
- Medical Instrumentation

Price (1 - 99)	Price (1000)
\$6.45	\$5.55

FEATURES

- Single Gain Set Resistor: $G = 1$ to 10,000
- Gain Error: $G = 10$, 0.08% Max
- Input Offset Voltage Drift: $0.3\mu\text{V}/^{\circ}\text{C}$ Max
- Meets IEC 1000-4-2 Level 4 ESD Tests with Two External 5k Resistors
- Gain Nonlinearity: $G = 10$, 10ppm Max
- Input Offset Voltage: $G = 10$, $60\mu\text{V}$ Max
- Input Bias Current: 350pA Max
- PSRR at $G = 1$: 105dB Min
- CMRR at $G = 1$: 90dB Min
- Supply Current: 1.3mA Max
- Wide Supply Range: $\pm 2.3\text{V}$ to $\pm 18\text{V}$
- 1kHz Voltage Noise: $7.5\text{nV}/\sqrt{\text{Hz}}$
- 0.1Hz to 10Hz Noise: $0.28\mu\text{V}_{P-P}$
- Available in 8-Pin PDIP and SO Packages

Datasheet: <http://cds.linear.com/docs/Datasheet/1167fc.pdf>